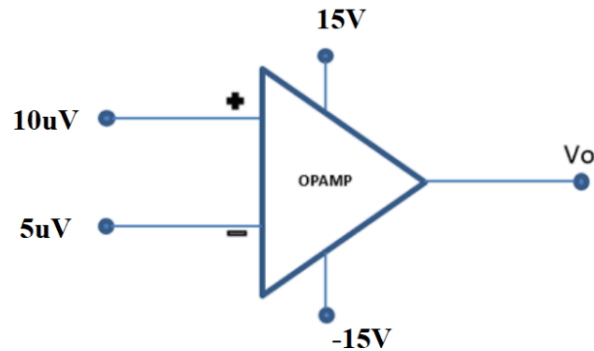


Assignment-1



Op-Amp

1. Observe the following circuit.




Calculate the value of V_o . Repeat the problem with $V_+=1$ mV and $V_-=0.2$ mV. Consider $A=2105$.

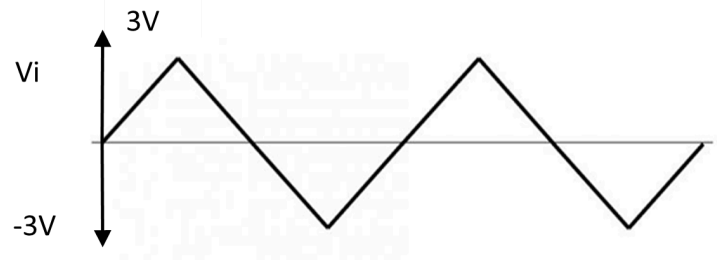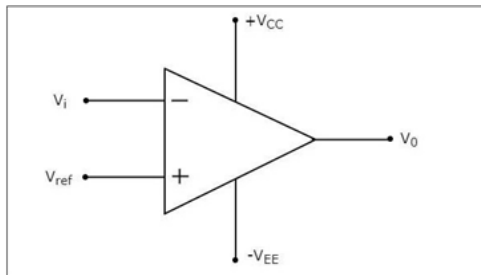2. Draw output V_o for the following op-amp circuit.



$V_{CC} = 15V = -V_{EE}$, $V_{ref} = 1.5V$, V_i is a 6V p-p triangular signal as shown below.

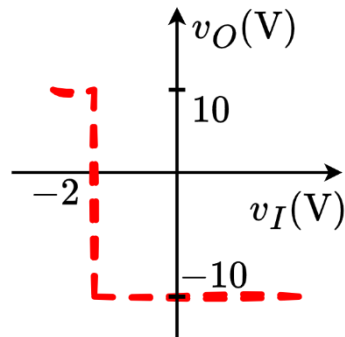3. Design a circuit using **op-amp** that has the voltage transfer characteristics as shown in the figure below. $v_o(V)$ is the **output voltage** and $v_i(V)$ is the **input voltage**.



4.

A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure in a water tank. The valve operates on **ACTIVE LOW** logic. (i.e., the valve is OPENED when given a LOW voltage of 1 V, but remains CLOSED when provided a HIGH voltage of 6 V.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.

At 0.5 atm pressure	At 1 atm pressure	At 1.5 atm pressure
$v_{0.5 atm} = 0.5 V$	$v_{1 atm} = 3 V$	$v_{1.5 atm} = 5.5 V$

The pressure in the water tank can be measured by the formula $P = h\rho g$, where P , (in **Pascals (Pa)** unit) is the water pressure, h is the height of water in the tank (in *metres*), $\rho (= 1000 \text{ kgm}^{-3})$ is the density of water and g is the acceleration due to gravity (in ms^{-2}).

[1 atm = 101325 Pa]

- Design** a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds **10 m**.
- Draw** the voltage transfer characteristics (VTC) of the designed Op-Amp.

5.

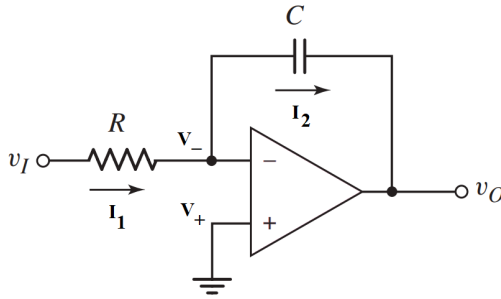


Figure 1 (a)

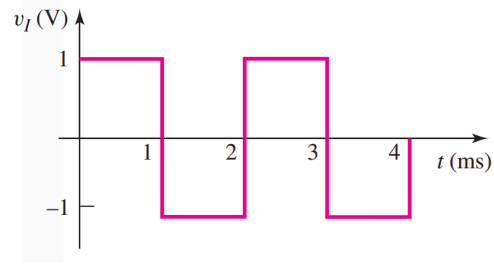


Figure 1 (b)

- (a) **Analyze** the circuit drawn in Fig. 1(a) and **determine** the voltage values at the inverting and non-inverting nodes (V_- and V_+). [0.5+0.5]
- (b) **Identify** the relation between I_1 and I_2 . [1]
- (c) **Analyze** the circuit to derive the expression of output voltage V_O . You have to **show** all the steps. [3]
- (d) Now consider the input wave v_I given in Fig. 1(b). For circuit parameters $R = 10 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$, **determine** the output voltage at $t = 1 \text{ ms}$. [1]
- (e) **Design** a circuit using Op-Amps to implement the following expression: [4]
- $$f = \frac{1}{4}x + 7y - \frac{d}{dt}z$$

6.


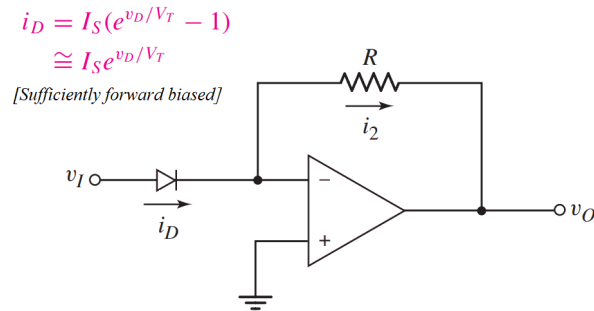


Figure 1

- (a) **Analyze** the circuit drawn in Fig. 1 and **determine** the voltage values at the inverting and non-inverting nodes (V_- and V_+). [0.5+0.5]
- (b) **Identify** and briefly explain the relation between i_2 and i_D . [1.5]
- (c) **Analyze** the circuit to derive the expression of output voltage V_O . You have to **show** all the steps. [3.5]

7.

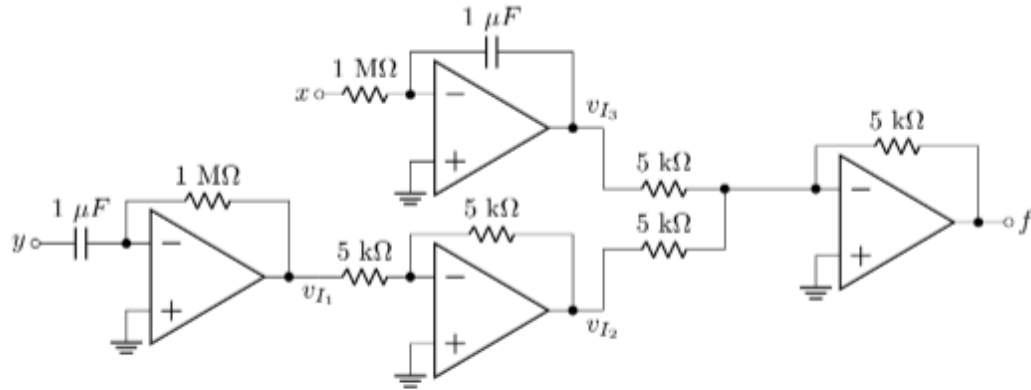

- Analyze** the circuit above to find an expression of f in terms of inputs x and y . Also, **determine** the intermediate outputs v_{I1} , v_{I2} , and v_{I3} as denoted in the circuit. [4]
- Draw the circuit of an inverting amplifier and **design** it in such a way that the voltage gain, $k = -4$. (*i.e.*, find the values of R_1 and R_2). [3]
- Show** the input and output waveforms of the inverting amplifier of part (b) assuming a sinusoidal input of 0.5 V amplitude. **Calculate** the amplitude of the output. [2]
- Consider the inverting amplifier of part (b) again. Assume the input voltage can provide a maximum current of 0.5 μA . **Determine** the design changes required, if any, for the circuit to work. [1]


8.

- Design** a circuit using **Op-Amp comparator** to automatically turn ON (or OFF) the street lights. For this, you have a lux sensor installed on top of the street lights (facing above) that outputs a voltage proportional to amount of natural light, as listed below:


$v_{\text{night}}, 0 \text{ lux} = 1 \text{ V}$	$v_{\text{dusk}}, 20 \text{ lux} = 2 \text{ V}$	$v_{\text{dawn}}, 80 \text{ lux} = 3 \text{ V}$
---	---	---

The lights require 20 V and should be ON if the amount of light goes **below** 20 lux (at dusk). [3]

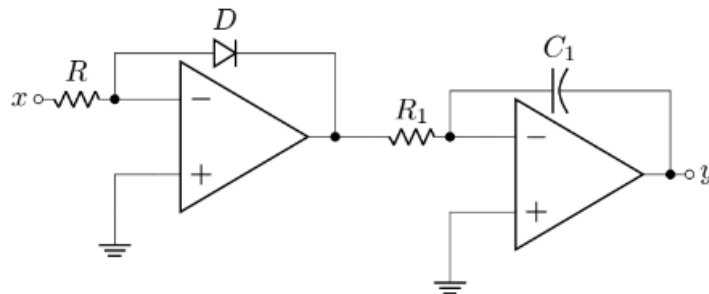- Design** a circuit using Op-Amp to implement the expression: $f = -3\frac{dx}{dt} + 2\exp y + 4z$ [4]
- Analyze** the circuit below to find y as a function of x . For the diode, $I_S R = 1$ and $V_T = 1$. [3]



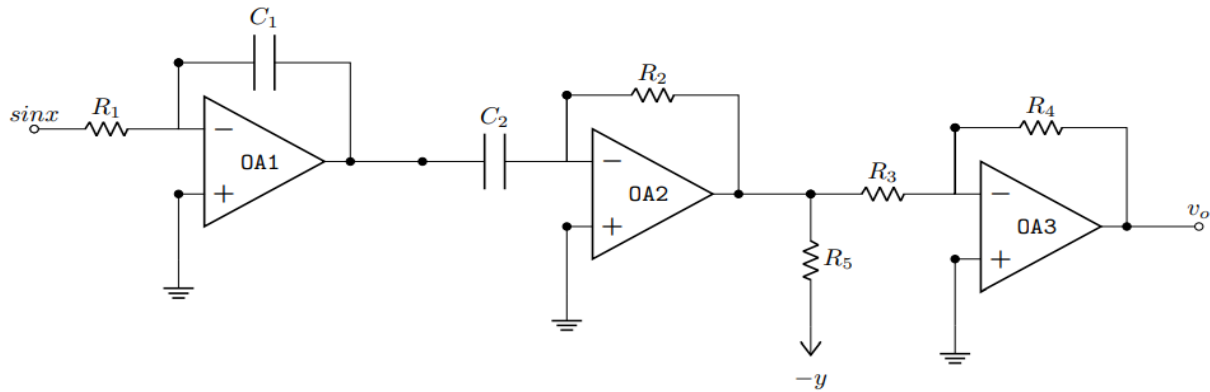
9. Deduce the expression for output, V_o from the circuit above



10. Design a circuit using op-amps to implement $y=7x$ by an


- Inverting amplifier
- Non-inverting amplifier

11.

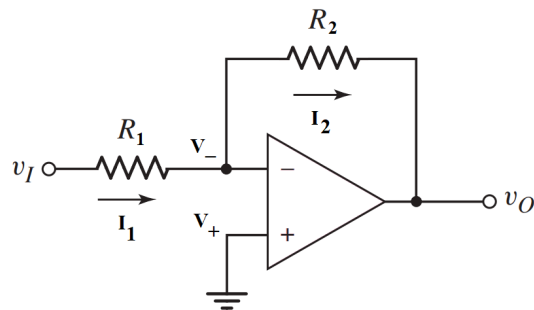


- Design** an inverting amplifier (i.e., find the values of R_1 and R_2 of the circuit shown in the Figure above) in such a way that the voltage gain is **-5**.
- Consider the circuit you drew in (a) again. Assume the input $v_i = 0.1 \sin \omega t$ (V) has a maximum current rating of 5 μA . What design changes, if any, are required for this input, if the voltage gain remains the same?
- Draw** the input and output waveforms of the circuit you designed in (c).

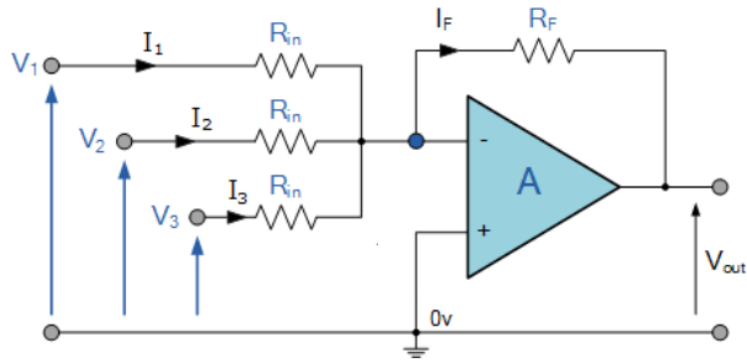- Analyze** the following circuit and derive the expression for the output voltage (V_{out}) in terms of the inputs. If $V_1=1$ V, $V_2=2$ V, and $V_3=1.5$ V, and all the resistors have equal values, calculate V_{out} .



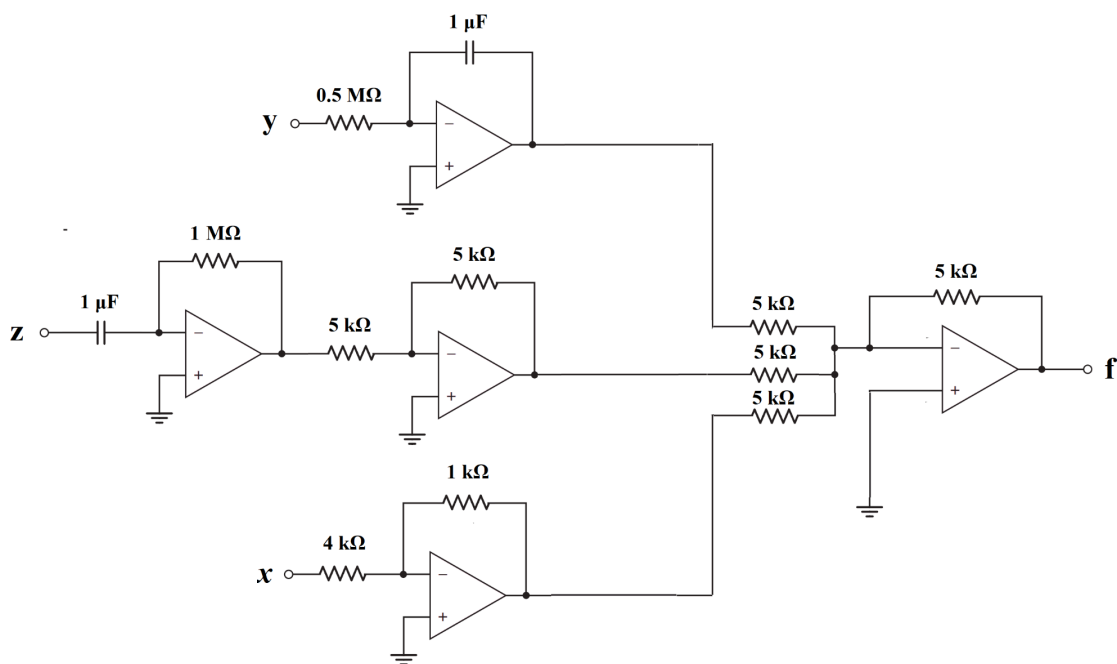12. **Analyze** the following circuit to find an expression of f in terms of x , y , and z .



13. Consider the Ideal Op-Amp and find the value of V_o .

