
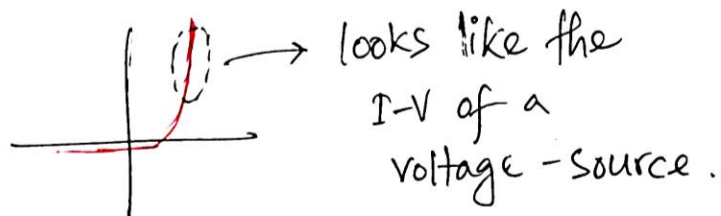


Applications:

2. Voltage Regulation:

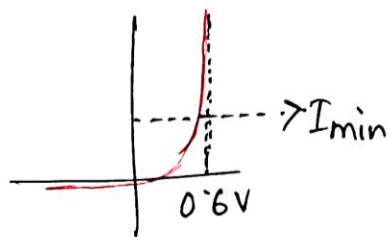


We can use the forward-drop of a non-ideal diode to give a constant voltage at the output.




However, the vertical I-V is maintained only if the diode-current is greater than I_{min} .

Example regulator:

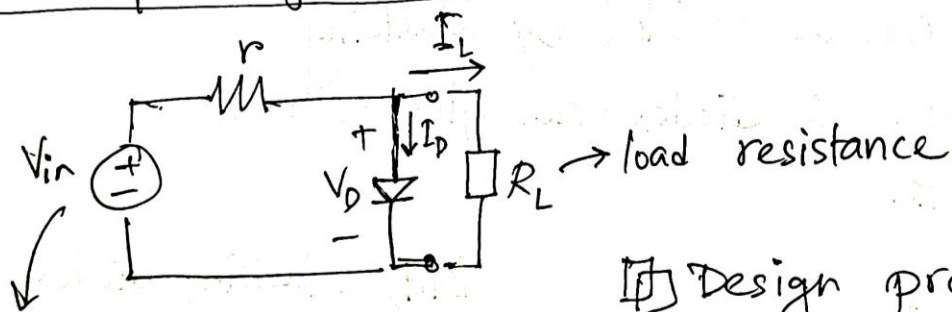

unregulated voltage source

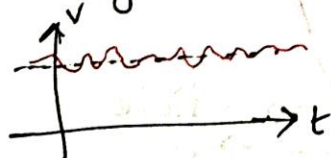

↳ voltage is not perfect DC
- has ripples/
fluctuation

Design problem:

$$V_{in} = 3V \pm 0.1V$$

$$I_{min} = 1mA$$

Load can draw max^m 10 mA current
What will be r for worst-case?
if V_D is to be regulated at 0.6 V?

For worst case,

Load current is max^m, i.e., $I_L = 10mA$

Diode " " min^m, i.e., $I_D = I_{min} = 1mA$

Input voltage " " , i.e., $V_{in} = 3V - 0.1V = 2.9V$

∴ To maintain regulation at worst-case,



$$\frac{V_{in(min)} - 0.6}{r} = I_L + I_D$$

$$\Rightarrow r = \frac{(2.9 - 0.6)V}{10mA + 1mA}$$
$$\cong \cancel{200\Omega} \quad 209\Omega$$

Drawbacks of regulator

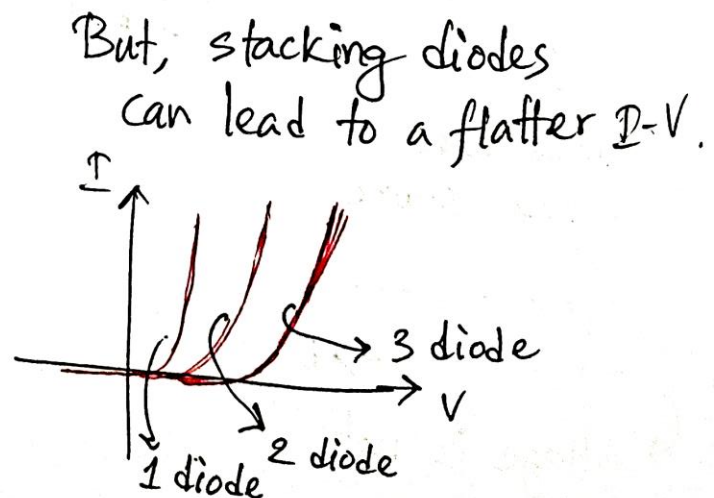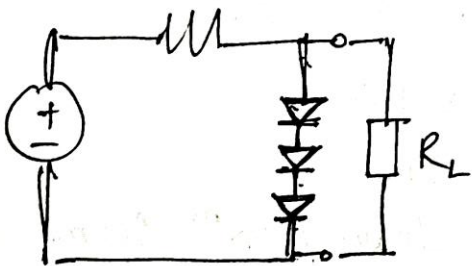1. Regulation voltage is low (only 0.6V!!)
2. I_{min} is relatively high
3. r can become low, and, cause high power loss.

— First drawback can be avoided by stacking diodes in series. 3 diodes can give voltage close to 2 Volts.




★ So, we usually don't stack more than 3 diodes.

- Better solⁿ ???

⇒ Use the reverse-breakdown region of the diode I-V.

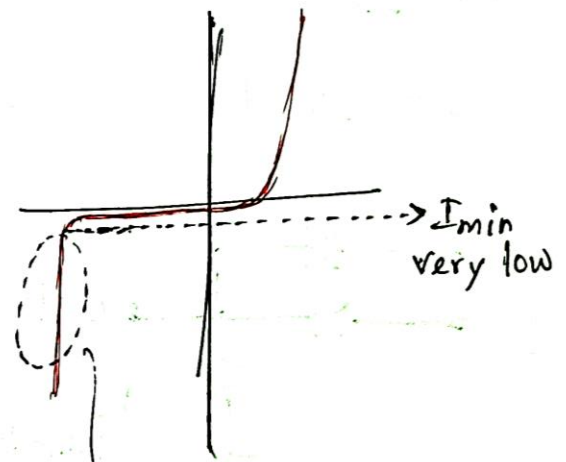- Pros
1. Breakdown voltage can be controlled during fabrication.
 2. I_{min} for reverse-breakdown can be very low.



→ I-V is very vertical during breakdown.

Very good voltage source!!
(☺)

Diodes which are designed/fabricated to operate reliably in breakdown are Zener Diodes.

Symbol:


Practice Problem:

Design a voltage regulator using a 2V-Zener Diode with the constraints of the previous problem.

Find the value of r in this case.

Voltage Regulators with Non-Ideal Zeners

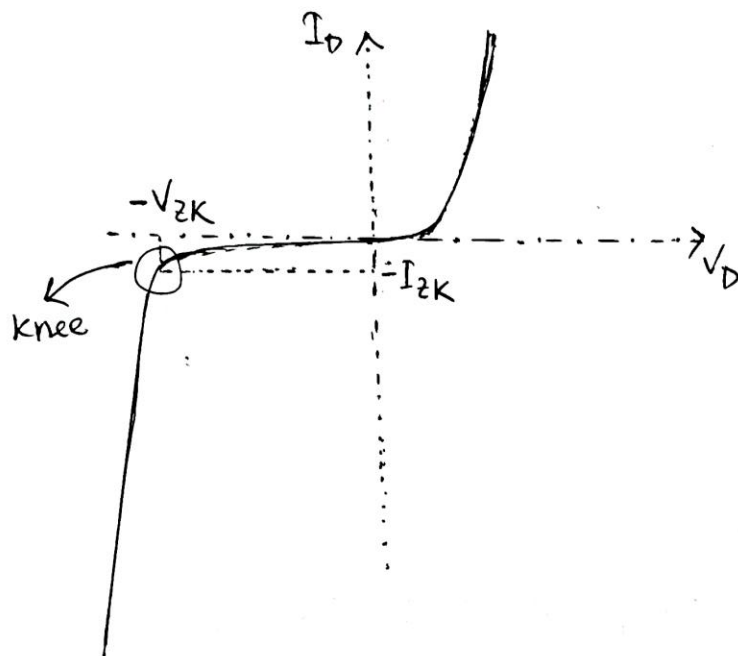Previously, we assumed that, the IV of a zener-diode is completely vertical in breakdown. However, for a real zener diode in breakdown, there is some slope in the IV.



real

So, during reverse breakdown, a ^{*real*} zener-diode may be modelled as a voltage source with a series resistance.


The minimum point upto which the zener can stay in breakdown is called the knee. The voltage and current at that point are the knee-voltage (V_{zk}) and knee-current (I_{zk}).

To stay in break-down, the reverse zener current must be at least, or, more than the knee-current.


* In spite of having a slope in break-down, the IV is almost vertical. So, the series resistance is very small. Usually, it is in the range $10\Omega \sim 50\Omega$.

Characteristics of a Non-ideal Voltage Regulator:

Our basic regulator ckt is this:

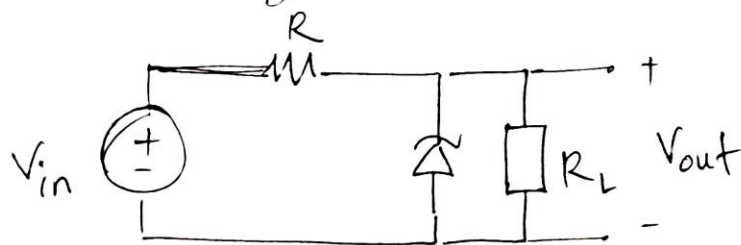

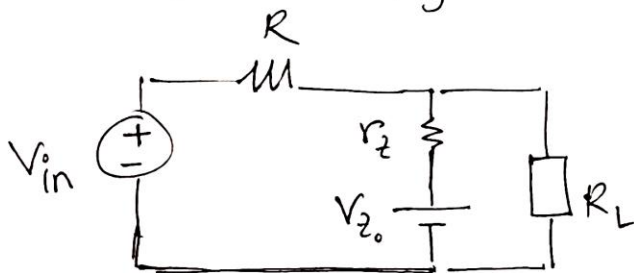When considering a reverse IV with a slope, we can replace it with a Voltage Source and Series resistance.



[Note that... $V_{Z0} \neq V_{ZK}$. Although, they are pretty close.]

For a regulator like this, the output voltage doesn't stay constant if the Input Voltage or the Output Current changes. V_{out} changes. We want to quantify this change.

2 measures of this change are:

(1) Line Regulation:

This is the change in output voltage with respect to the change in line voltage (i.e, Input Voltage). — keeping load resistance fixed.


Mathematically, line regulation = $\frac{dV_{out}}{dV_{in}}$.

(2) Load Regulation:

This is the change in output voltage w.r.t. load current (i.e., output current.) — keeping input voltage fixed.

Mathematically, load regulation = $\frac{dV_{out}}{dI_{out}}$

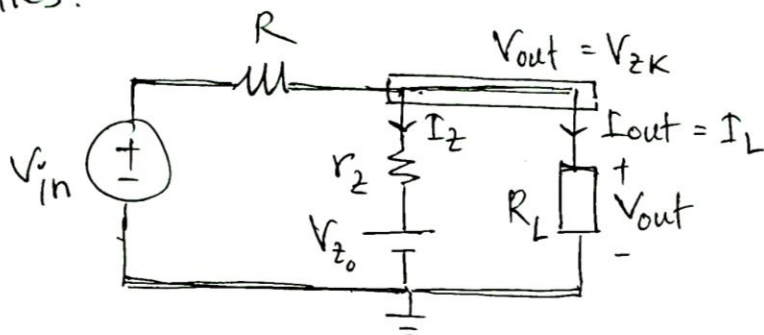For our basic voltage regulator, we will find these 2 quantities.



As before we will proceed from the node equation of V_{out} .

$$\frac{V_{out} - V_{in}}{R} + I_z + I_L = 0 \Rightarrow \frac{V_{out} - V_{in}}{R} + \frac{V_{out} - V_{z0}}{r_z} + I_{out} = 0 \quad \text{--- (1)}$$

For line-regulation, $I_{out} = \frac{V_{out}}{R_L}$.

$$\therefore \frac{V_{out} - V_{in}}{R} + \frac{V_{out} - V_{z0}}{r_z} + \frac{V_{out}}{R_L} = 0.$$

$$\Rightarrow V_{out} \left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) = \frac{1}{R} V_{in} + \frac{1}{r_z} V_{z0}$$

$$\therefore V_{out} = \frac{R \parallel r_z \parallel R_L}{R} \cdot V_{in} + \frac{R \parallel r_z \parallel R_L}{r_z} \cdot V_{z0} \quad \text{--- (11)}$$

Here, $R_p = R \parallel r_z \parallel R_L$ is the parallel combination of R , r_z and R_L .

$$\text{i.e., } \frac{1}{R_p} = \frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L}$$

$$\therefore \text{From (11), } \frac{dV_{out}}{dV_{in}} = \frac{R \parallel r_z \parallel R_L}{R} \quad [\text{Line Regulation}] \quad \text{--- (3)}$$

As a special case, if no load is connected to the output, (i.e., if output is open-circuited or $R_L = \infty$)

$$\frac{dV_{out}}{dV_{in}} = \frac{R \parallel r_z}{R} = \frac{r_z}{r_z + R} \quad \text{--- ()}$$

For load-regulation, we can start directly from eqn (1),

$$\frac{V_{out} - V_{in}}{R} + \frac{V_{out} - V_{z_0}}{r_z} + I_{out} = 0.$$

$$\Rightarrow V_{out} \left(\frac{1}{R} + \frac{1}{r_z} \right) = -I_{out} + \frac{1}{R} V_{in} + \frac{1}{r_z} V_{z_0}.$$

$$\therefore V_{out} = - (R \parallel r_z) \cdot I_{out} + \frac{R \parallel r_z}{R} V_{in} + \frac{R \parallel r_z}{r_z} V_{z_0}.$$

As before, $R_p = R \parallel r_z$ is the parallel combⁿ of R and r_z .

$$\text{i.e., } \frac{1}{R_p} = \frac{1}{R} + \frac{1}{r_z}.$$


$$\therefore \frac{dV_{out}}{dI_{out}} = - R \parallel r_z = - \frac{R \cdot r_z}{R + r_z} \quad [\text{Load Regulation}] \text{ --- (4)}$$

In both cases, eqn (3) and (4), the regulation decreases with r_z . For a Zener with completely vertical IV, $r_z = 0$, and, both $\frac{dV_{out}}{dV_{in}}$ and $\frac{dV_{out}}{dI_{out}}$ will be equal to 0.

Finding corner parameters with r_z :

To find the corner values of different parameters of voltage regulator $[V_{in}(\min), I_L(\max), R_L(\min), R(\max)]$, we use the following node-equation:
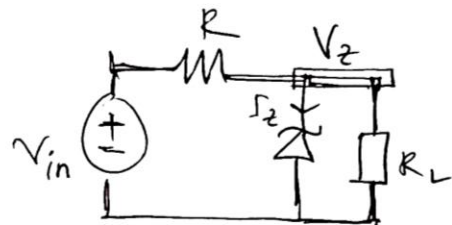
$$\frac{V_z - V_{in}}{R} + I_z + I_L = 0$$



To find the corner values, we always have to set,

$$V_z = V_{zk} \text{ and } I_z = I_{zk}.$$

If one of them is not given, they have to be inferred from other data.

E.g, if V_{z0} , r_z and I_{zk} are given, we can find V_{zk} using,

$$V_{zk} = V_{z0} + I_{zk} \cdot r_z$$

Example:

You are a circuit-engineer who has to design a voltage regulator. The zener diodes you ~~have~~ own have a knee current of 1mA, a series resistance of 25Ω and $V_{z0} = 4V$.

The customer to which you will sell the regulator has a supply of 6V with $\pm 0.2V$ ripple. ~~he~~ The lowest resistance that he will connect to the output of the regulator is $0.5k\Omega$.

Find the value of R such that the regulator will work properly in the worst-case condition.

Here, we will use the ~~the~~ worst-case values for all parameters.

$$I_{ZK} = I_Z = I_{ZK} = 1 \text{ mA}$$

$$\begin{aligned} V_Z &= V_{ZK} = V_{Z_0} + I_{ZK} \times r_Z \\ &= 4 + 1 \times 0.025 \quad [r_Z = 25 \Omega = 0.025 \text{ k}\Omega] \\ &= 4.025 \text{ V} \end{aligned}$$

[Note: If V_{ZK} was given directly in the question, we wouldn't have to do this step].

$$I_L = I_L(\text{max}) = \frac{V_Z}{R_L(\text{min})} = \frac{V_{ZK}}{R_L(\text{min})} = \frac{4.025}{0.5} = 8.05 \text{ mA}$$

$$V_{in} = V_{in}(\text{min}) = 6 \text{ V} - 0.2 \text{ V} = 5.8 \text{ V}.$$

Plugging all these values in the eqn—

$$\frac{V_Z - V_{in}}{R} + I_Z + I_L = 0.$$

$$\text{We get, } R(\text{max}) \approx 0.196 \text{ k}\Omega \approx 200 \Omega.$$

** If V_{ZK} , V_{Z_0} and r_Z ^{are given,} we can calculate I_{ZK} from that.

** If both V_{Z_0} and r_Z are not given, only the zener breakdown voltage is given, we can use $V_{ZK} = V_Z$ (breakdown).

** If none of V_{Z_0} , r_Z , I_{ZK} are given, we can use $I_{ZK} = 0$.