



BRAC University Dept. of Computer Science and Engineering	Assessment: Assignment 2 Due: 11:59 PM 18 February 2024 Full Marks: 40
Semester: Spring 2024 Course Code: CSE251 Section: 10/11 Course Name: Electronic Devices and Circuits	Name: _____ Student ID: _____

- ✓ Write down your student ID on the **top right corner of each of the pages**.
- ✓ Clearly write the solutions, along with the questions, on white paper with black ink (no need to use color pen, don't use pencils).
- ✓ Use **CamScanner**, or **Adobe Scan**, or **Microsoft Office Lens**, or any other software to scan the pages and make a **single PDF file**.
- ✓ After creating the PDF, make sure that (a) there are no pages missing, (b) all of the pages are legible, (c) your student ID on each page are visible.
- ✓ Please note, **collaboration ≠ copying**. You are allowed to discuss the questions and clear confusion you might have, but you have to write your solutions independently and be able to explain your answers during a random viva.
- ✓ **[Very Important]** Rename the PDF in the following format: "**A2_StudentID_FullNameWithoutSpace.pdf**". For example, if my student ID is 12345678 and my name is Shadman Shahid, the filename should be "**A2_12345678_ShadmanShahid.pdf**".
- ✓ **Submission Link:** <https://forms.gle/t3jtDhcubjZVhJs6>

[CO3] Question 1:


20 Marks

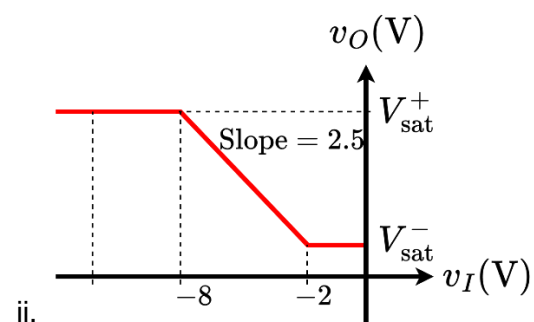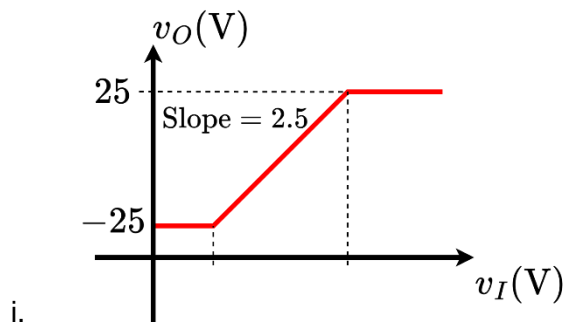- a) Design circuits using **op-amp** that can implement the following functions, where x, y, z indicate input voltages and f indicates the output voltage: **6**
- $f = 3x + 7y$
 - $f = -3 \int x dt + 7y + 5 \frac{dy}{dt}$
 - $f = 4x - 7y + 8z$
- b) Design circuits using **op-amp** to implement the following Voltage transfer characteristics graphs. Clearly show the saturation voltages and any necessary parameters to fully characterize the device. **8**



- c) **Design** the circuit below such that the closed loop voltage gain is $A_{CL} = 18$. The maximum current **in any resistor** is to be limited to $15 \mu A$ with the input voltage in the range $-30 \leq v_I \leq 30 mV$. **6**

- What are the values of R_I and R_f ?
- What is the range of output voltage v_O ?

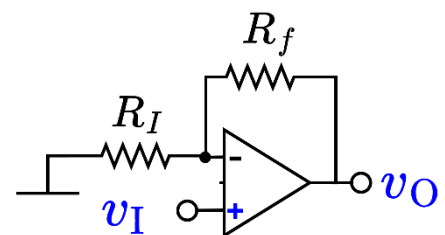


Question 2:

20 Marks

a) Find v_o for the following values of v_i :


- 0.5 V
- 2 V
- 8 V

[CO2] 9

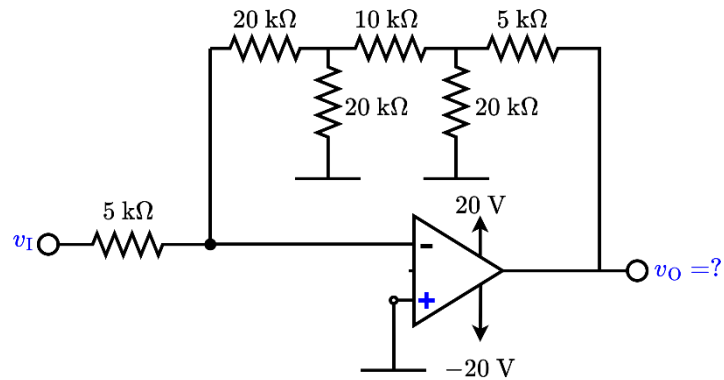

b) Calculate v_o in terms of I_1 , V_1 and V_2 in the adjacent figure. You may assume the operational amplifier has ideal characteristics.

[CO2] 3

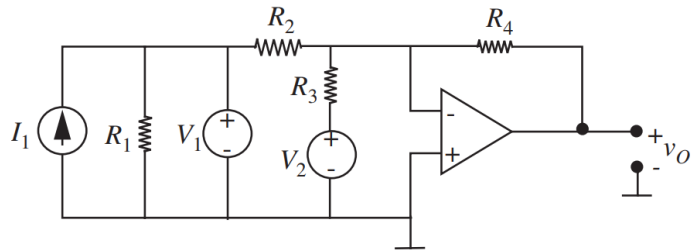

c) Write the node equations for the v_a and the v_- nodes, and enough more independent relations to specify v_o in terms of v_i . Do not solve.

[CO2] 8

