



Semester: Spring 2024
 Course Code: CSE251
 Section: 10 / 11
 Course Name: Electronic Devices and Circuits


Name: _____

Student ID: _____

- ✓ Write down your student ID on the top right corner of each of the pages.
- ✓ Clearly write the solutions, along with the questions, on white paper with black ink (no need to use color pen, don't use pencils).
- ✓ Use CamScanner, or Adobe Scan, or Microsoft Office Lens, or any other software to scan the pages and make a single PDF file.
- ✓ After creating the PDF, make sure that (a) there are no pages missing, (b) all of the pages are legible, (c) your student ID on each page are visible.
- ✓ Please note, **collaboration ≠ copying**. You are allowed to discuss the questions and clear confusion you might have, but you have to write your solutions independently and be able to explain your answers during a random viva.
- ✓ [Very Important] Rename the PDF in the following format: "<Section>_A1_StudentID_FullNameWithoutSpace.pdf". For example, if I am in section 10 and my student ID is 12345678 and my name is Shadman Shahid, the filename should be "10_A1_12345678_ShadmanShahid.pdf".
- ✓ **Submission Link:** <https://forms.gle/DCqCu220xdxKRod96>

Question 1:

10 Marks

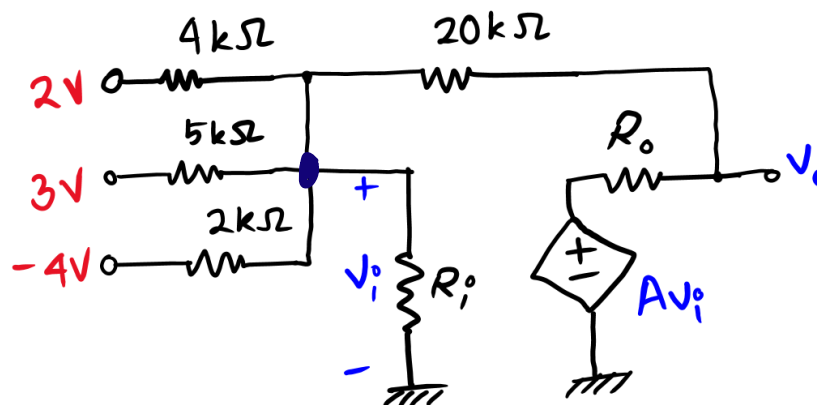

In the above circuit $A = 200$, $R_i = 200 \text{ k}\Omega$ and $R_o = 1 \text{ k}\Omega$. Answer the following questions

- Write the node equations for the nodes indicated by v_i and v_o . [CO1] 4
- Solve the node equations to find the values of v_i and v_o . [CO2] 3
- Can circuit theorems based on linearity principle (such as superposition principle) be applied to the above circuit? Explain in short why or why not. [CO1] 3

Solution:

a) At node v_i :

$$\frac{2-v_i}{4} + \frac{3-v_i}{5} + \frac{-4-v_i}{2} = \frac{v_i-v_o}{20} + \frac{v_i}{200} \quad \dots\dots(i)$$

At node v_o :

$$\frac{v_i-v_o}{20} + \frac{Av_i-v_o}{1} = 0 \quad \dots\dots(ii)$$

b) Simplifying:

(i) becomes:

$$v_i \left(\frac{1}{4} + \frac{1}{5} + \frac{1}{2} + \frac{1}{20} + \frac{1}{200} \right) - v_o \left(\frac{1}{20} \right) = \frac{2}{4} + \frac{3}{5} - \frac{4}{2}$$

$$\therefore 1.005v_i - 0.05v_o = -0.9 \quad \text{--- (iii)}$$

(ii) becomes:

$$v_i \left(-\frac{1}{20} - \frac{200}{1} \right) + v_o \left(1 + \frac{1}{20} \right) = 0$$

$$-200.05v_i + 1.05v_o = 0 \quad \text{--- (iv)}$$

Solving (iii) & (iv) we get:

$$\begin{aligned} v_i &= 0.1056 \text{ V} \\ v_o &= 20.123 \text{ V} \end{aligned}$$

c) Yes! Because all the circuit elements are linear. (Even the voltage dependent voltage source, because the voltage dependence (Av_o) is linear.)

$$v_o = I_L R_L = 0.5 \times 20 = 10 \text{ V}$$

$$I_2 = \frac{v_o - \sqrt{20}}{r_2} = \frac{10 - 2.5}{0.04} =$$

Question 2:

8 Marks


For $R = 200 \Omega$, $R_L = 20 k\Omega$, $r_z = 40 \Omega$, $V_{Z0} = 2.5 V$, and $I_L = 0.5 mA$.

a) Find V_O , I_Z

[CO2] 4

b) Find I , V^+ .

[CO2] 4

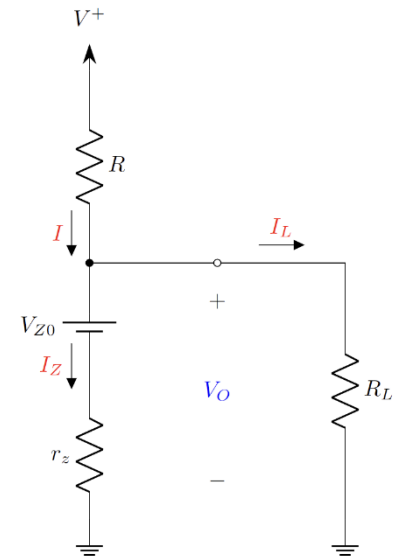

$$a) V_O = I_L R_L = 0.5 \times 20 = 10 V$$

$$I_L = \frac{V_O - V_{Z0}}{r_z} = \frac{10 - 2.5}{0.04} = 187.5 mA$$

$$b) I = I_L + I_Z = (0.5 + 187.5) mA = 188 mA$$

$$V^+ = V_O + I R = (10 + 187.5 \times 0.2) V = 47.6 V$$

Question 3:

10 Marks

In the adjacent circuit $\alpha = 0.95$.

a) Derive an expression of I_E in terms of I_B and α .


[CO1] 3

b) Find the value of the currents I_E , I_B and I_C .

[CO2] 4

c) Find the value of the voltage at the output node v_o .

[CO2] 3

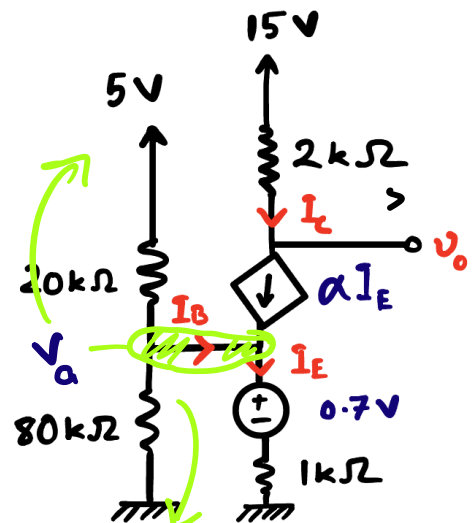

$$a) I_E = I_B + \alpha I_E \quad (\text{From node } v_a)$$

$$I_E (1 - \alpha) = I_B$$

$$I_E = \frac{I_B}{1 - \alpha}$$

$$b) \text{Node analysis at } (v_a): \left(\frac{v_a - 5}{20} + \frac{v_a}{80} + \frac{v_a - 0.7}{1} = \alpha I_E \right)$$

$$V_a \left(\frac{1}{20} + \frac{1}{80} \right) + (V_a - 0.7) \left(\frac{1}{1} \right) - 5 \left(\frac{1}{20} \right) - \alpha I_E = 0$$

$$\therefore V_a \left(\frac{1}{16} \right) + V_a - 0.7 - 0.25 - \alpha (V_a - 0.7) = 0$$

$$V_a \left(\frac{1}{16} + 1 - 0.95 \right) = 0.7 + 0.25 - 0.95 \times 0.7$$

$$\Rightarrow V_a = \frac{0.285}{0.1125} \text{ V} = 2.533 \text{ V}.$$

b (Ans)

$$I_B = \frac{5 - V_a}{20} - \frac{V_a}{80} = \frac{11}{120} \text{ mA} = 0.09166 \text{ mA}$$

$$I_E = \frac{V_a - 0.7}{1} = \frac{11}{6} \text{ mA} = 1.833 \text{ mA}$$


$$I_C = \alpha I_E = 1.7467 \text{ mA}$$

$$(c) \Rightarrow V_o = 15 - I_C \times 2 = 11.5066 \text{ V}$$

Question 4: [CO2]


12 Marks

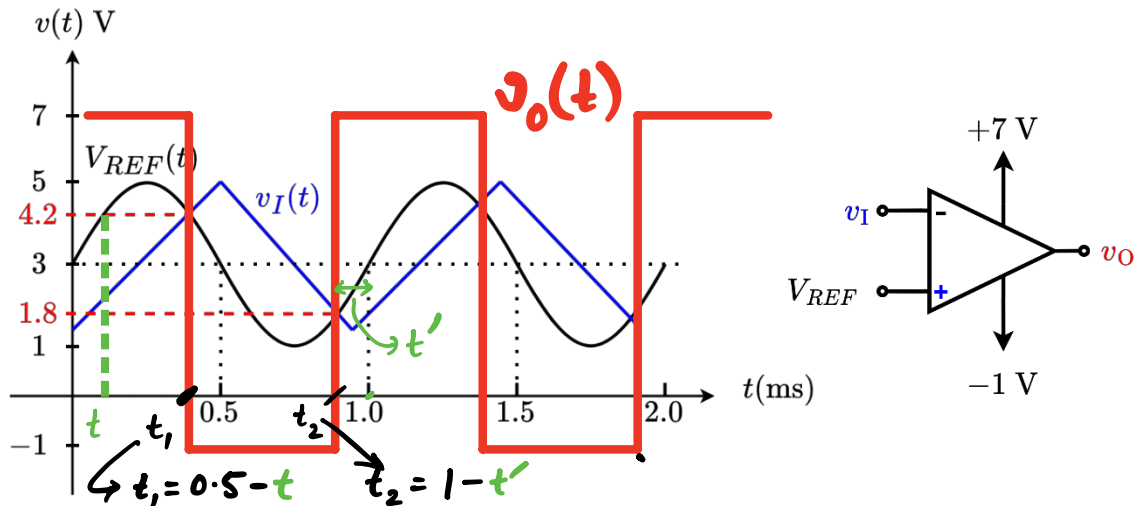- a) Assume that the Op-amp on the right is ideal. The wave shapes of v_I and V_{REF} are shown on the adjacent graph. 6



- Draw the waveshape of the output voltage of the op-amp $v_O(t)$ on the graph provided above. Indicate the time (t) in which switching would occur in $v_O(t)$. (Print this page and draw the graph on the same graph paper)

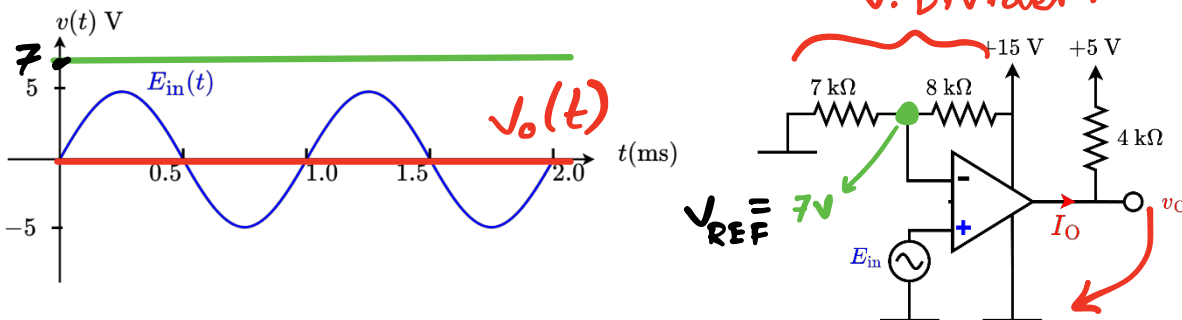- b) Assume that the Op-Amp on the right is ideal. Answer the following questions. 6



- Sketch accurately the graph of V_O vs E_{in} (VTC).
- Sketch accurately the graphs of V_O vs t . Find out the time (t) in which switching would occur in $V_O(t)$.

↓

V_O is 0 V ✓ (The negative saturation)
 as E_{in} is always less than $V_{REF} = 7\text{ V}$.
 So, v_O never switches.

Never

4 (a)

$$2\sin\left(\frac{2\pi}{1}t\right) + 3 = 4.2$$

$$t = 0.102 \text{ ms}.$$

$$\therefore t_1 = \frac{1}{2} \text{ ms} - 0.102 \text{ ms} = 0.398 \text{ ms}$$



$$2\sin\left(\frac{2\pi}{1}t\right) + 3 = 1.8$$

$$t' = -0.102 \text{ ms}$$


$$t_2 = 1 - 0.102 \text{ ms} = 0.898 \text{ ms}.$$

Question 5:

10 Marks

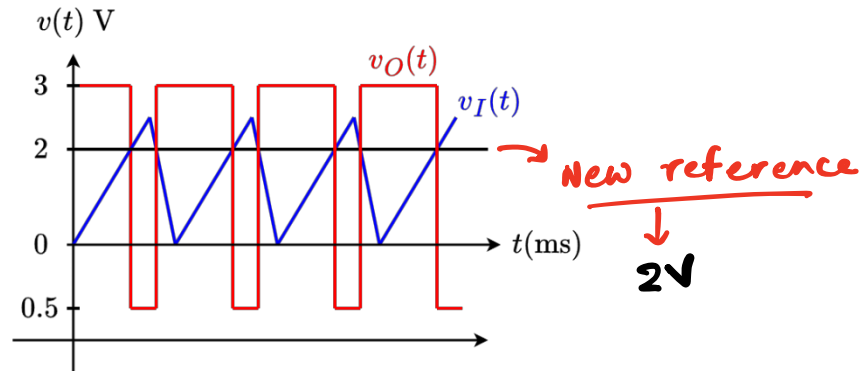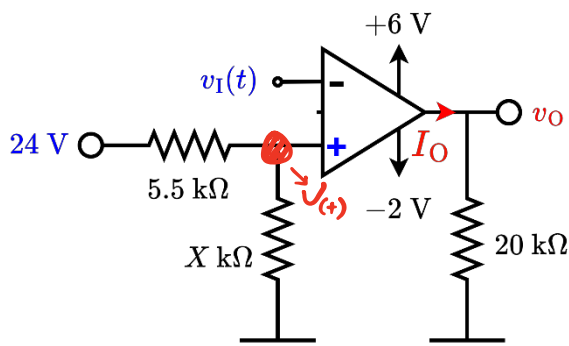

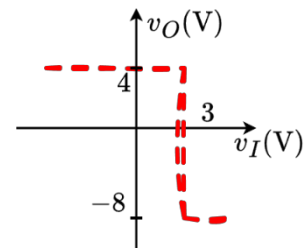- a) For $X = 2.5$, and $v_I = 9\text{ V}$, find v_O and I_O . [CO3] 3
- b) Find the value of X and the new saturation voltages (positive and negative) to implement the waveshape in the right figure. [CO3] 4
- c) Design a circuit using op-amp that has the voltage transfer characteristics as shown in the figure below. v_O (V) is the output voltage and v_I (V) is the input voltage. [CO3] 3



a) $X = 2.5$

$$\therefore v_{(+)} = \frac{2.5}{2.5 + 5.5} \times 24\text{ V} = 7.5\text{ V (Reference)}$$

v. Divider at $v_{(+)}$ node

If $v_I = 9\text{ V} = v_{(-)}$ (input voltage)

$v_I > v_{(+)}$ (Reference) . [Inverting configuration]

So; $v_O = -2\text{ V}$ as $[v_{(+)} - v_{(-)} = (7.5 - 9)\text{ V} = -1.5\text{ V}]$

$\therefore v_{(+)} - v_{(-)} < 0\text{ V}]$

$$I_O = \frac{v_O}{20} = -0.1\text{ mA}$$

$$b) V_{REF} = V_{(+)} = 2V$$

$$V_{(+)} = \frac{X}{X+5.5} \times 24 = 2$$


$$\frac{X}{X+5.5} = \frac{2}{24}$$

$$24X = 2X + 11$$

$$22X = 11$$


$$\boxed{X = 0.5}$$

c)

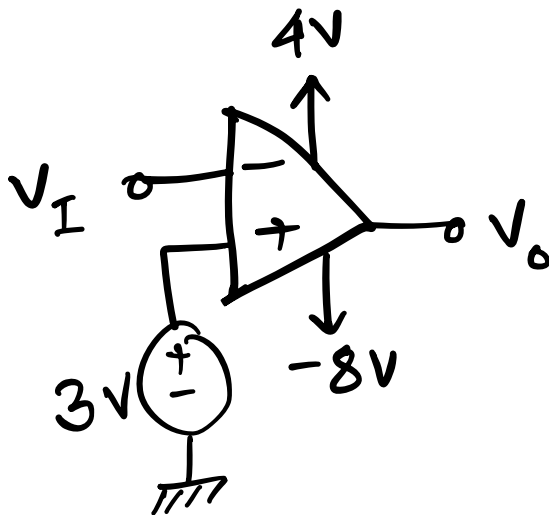


Question 6:

10 Marks

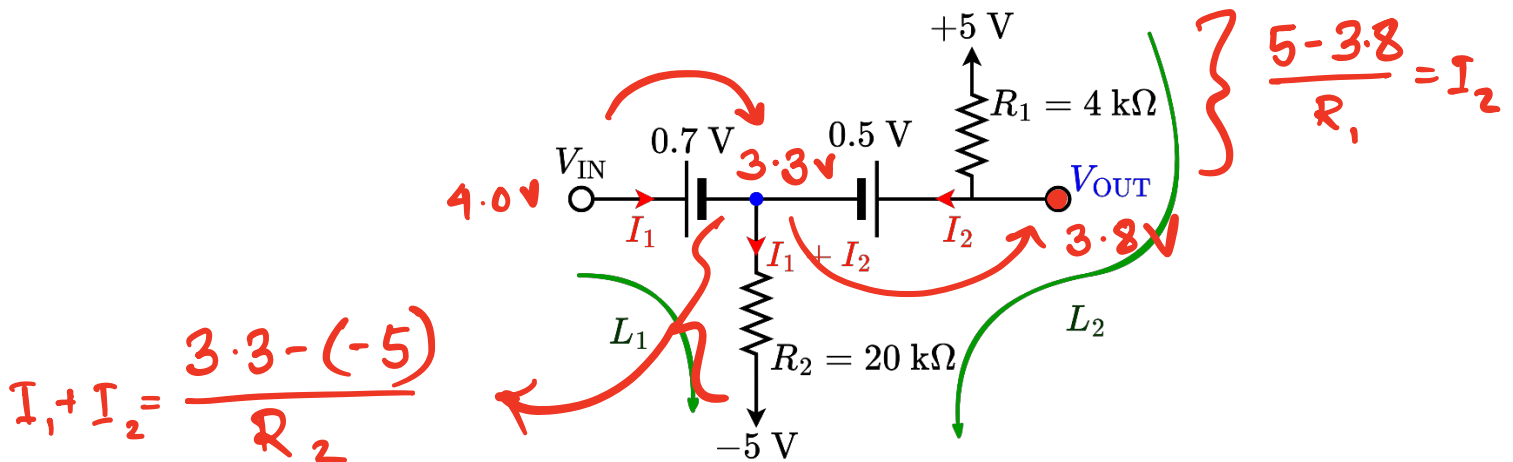

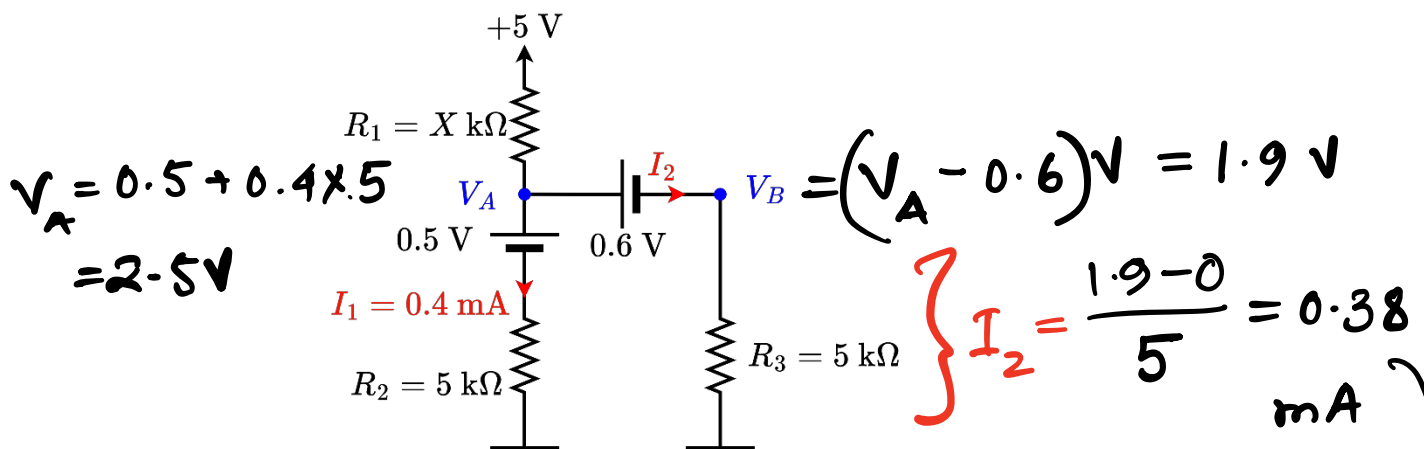- a) $[V_{IN} = 4.0 \text{ V}]$ Write down the two KVL equations for the lines (loops) indicated by the ~~red~~ **green** lines L_1 and L_2 . [CO1] 3
- b) $[V_{IN} = 4.0 \text{ V}]$ Solve the circuit to find V_{OUT} , I_1 and I_2 . You may use either mesh analysis or nodal analysis. [CO2] 4



- c) Design the circuit; i.e., find X to get $I_1 = 0.4 \text{ mA}$. [Use any technique of your choice.] Find V_A , I_2 and V_B . [CO2] 3

c $\therefore I = I_1 + I_2 = 0.4 + 0.38 = 0.78 \text{ mA}$

$\therefore R_1 = \frac{5 - 2.5}{0.78} = X$

$\therefore X = \frac{2.5}{0.78} \text{ V} = 3.205 \text{ V}$

6a. L1: $V_{IN} - 0.7 - R_2(I_1 + I_2) = -5 \quad \text{--- (i)}$
 $(4.0V)$

L2: $5 - R_1 I_2 - 0.5 - R_2(I_1 + I_2) = -5 \quad \text{--- (ii)}$

b. $\frac{3.3 + 5}{20} = I_1 + I_2 = 0.415 \text{ mA}$

$5 - 4.3 + 0.5$

$V_{out} = V_{IN} - 0.7 + 0.5 = 4 - 0.2 \text{ V}$

$V_{out} = 3.8 \text{ V}$

$I_2 = \frac{5 - 3.8}{4} = 0.3 \text{ mA}$

$I_1 = 0.465 - 0.3 \text{ mA} = 0.115 \text{ mA}$

Or;

Solving (i) & (ii)

$I_1 = 0.115 \text{ mA}$

$I_2 = 0.3 \text{ mA}$

$\& V_o = 5 - R_1 I_2 = (5 - 1.2) \text{ V}$