

Brac University

Mid Term Exam

Fall 2023

CSE251


Electronic Devices and Circuits

Date: 04 November 2023

Time: 1 hour 30 minutes (4:30 PM - 6:00 PM)


Marks: 30 (*Answer any 3 out of 4 questions*)

Q1

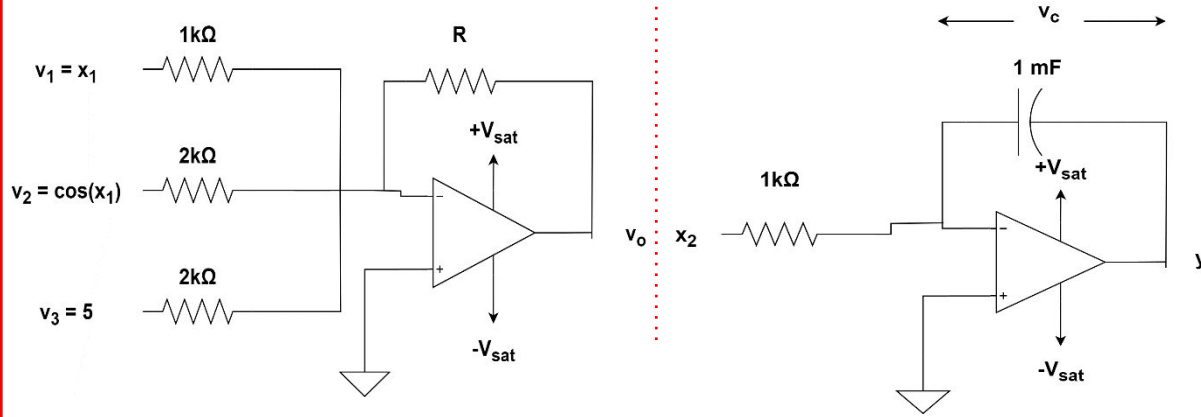

- (a) Determine the expressions for V_o and y . [3+1]
 (b) Assume, $V_o = X_2$, $V_1 = y$. Rewrite the expressions found in part-(a). [1+1]
 (c) Draw the circuit for the expressions found in part-(b). [2]
 (d) Define and explain “virtual ground” in an Ideal Op-Amp. [2]


Q2

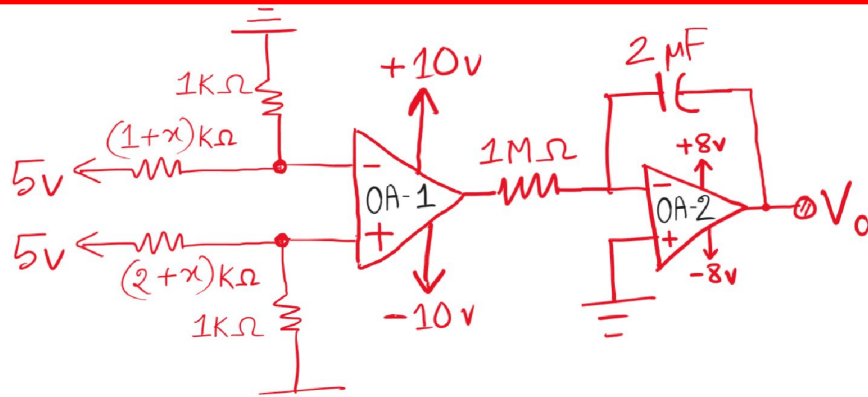

In the circuit given above, x = last digit of your student ID


- (a) Analyze the circuit and determine the voltage at the inverting, non-inverting terminals and the output of OA-1. [2+2+2]
 (b) Determine the highest V_o you can get from this circuit. Explain briefly. [1]
 (c) Analyze the circuit to determine the output voltage, V_o of OA-2 and plot V_o vs. time. Label the plot appropriately. [at $t = 0$, $V_o = 0$] [3]

Q3

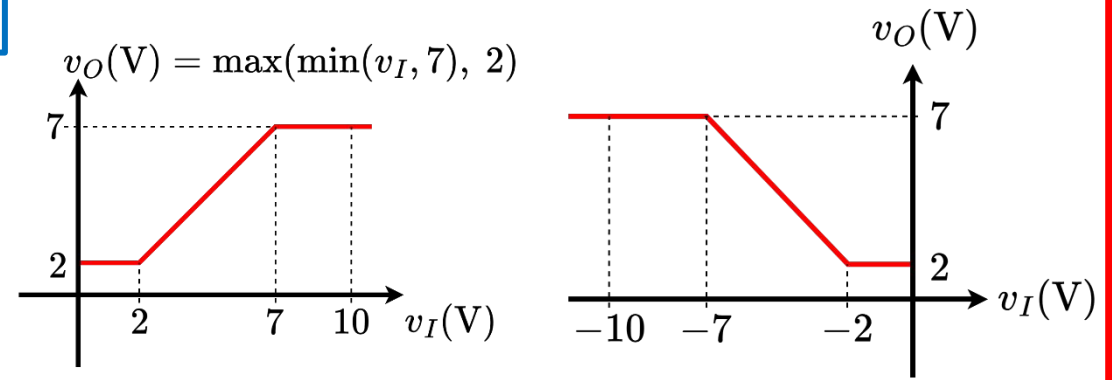

- (a) Design separate circuits, using only diodes, to implement the following functions, $z = \min(v_1, 7)$ and $v_o = \max(z, 2)$. [3+3]
 (b) Design a circuit using Op-Amp to implement the VTC on the right. [3]
 (c) Determine which of the following logic gates can be built with diodes and explain briefly: (i) XOR, (ii) XNOR. [1]


Q4

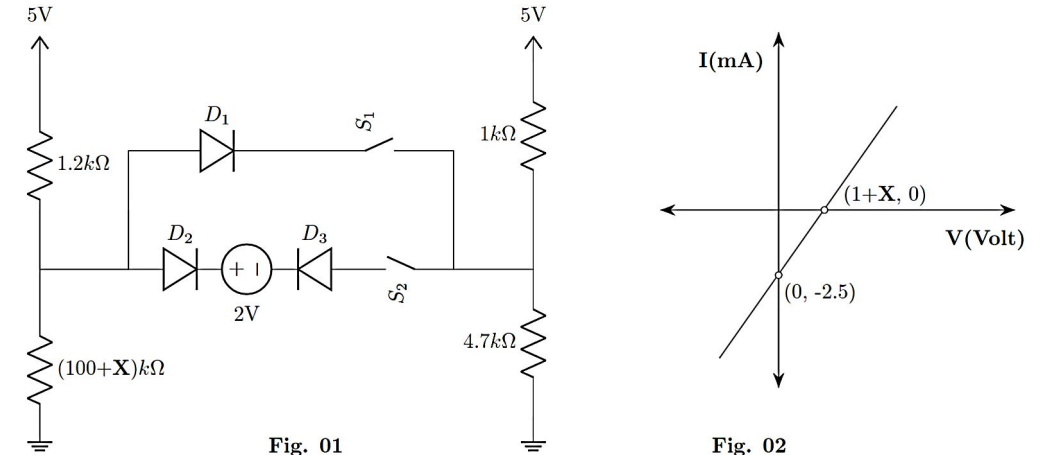

In Fig.01, a circuit is shown with two ‘off’ switches, S_1 and S_2 where $V_{D0} = 0.7V$. Fig.02 represents the IV-curve of an unknown device. Assume, X = Last digit of your Student ID.

- (a) Calculate the current passing through the diode D_1 , if only S_1 is ‘on’. [03]
 (b) Calculate the current passing through the diodes D_2 and D_3 If only S_2 is ‘on’. [04]
 (c) Determine and draw the unknown component of Fig. 02 with parameters. [02+01]

Q1

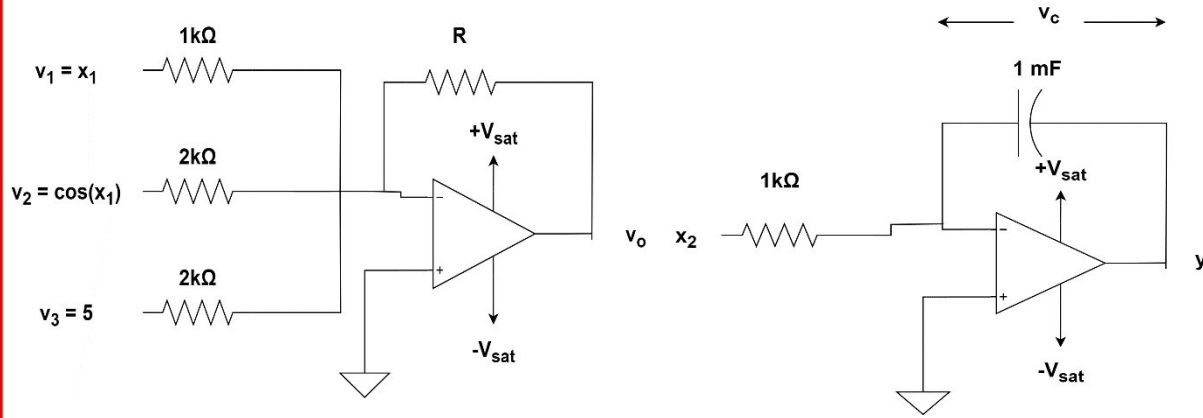

- (a) Determine the expressions for V_o and y . [3+1]
 (b) Assume, $V_o = X_2$, $V_1 = y$. Rewrite the expressions found in part-(a). [1+1]
 (c) Draw the circuit for the expressions found in part-(b). [2]
 (d) Define and explain “virtual ground” in an Ideal Op-Amp. [2]

(a)

$$t_1 = x_1 \sim 10x_1$$

$$t_2 = 0.5 \cos(x_1) \sim 5 \cos(x_1)$$

$$t_3 = 2.5 \sim 25$$

$$V_o = -t_1 - t_2 - t_3$$

$$y = -\int x_2(t) dt$$

(b)

$$y = -\int x_2(t) dt$$

$$y = -\int V_o(t) dt$$

$$V_o(t) = -\frac{dy}{dt}$$

$$\frac{dy}{dt} = y + 0.5 \cos(x_1) + 2.5 \sim \frac{dy}{dt} = 10y + 5 \cos(x_1) + 25$$

$$y = \int (y + 0.5 \cos(x_1) + 2.5) dt$$

$$V_1 = \int (V_1 + 0.5 \cos(x_1) + 2.5) dt$$

$$x_2 = -\int x_2 dt$$


(c)

Just join $V_o - x_2$ and $y - V_1$

(d)

The concept of $V_+ \approx V_-$ in Op-Amp input terminals.

Q2

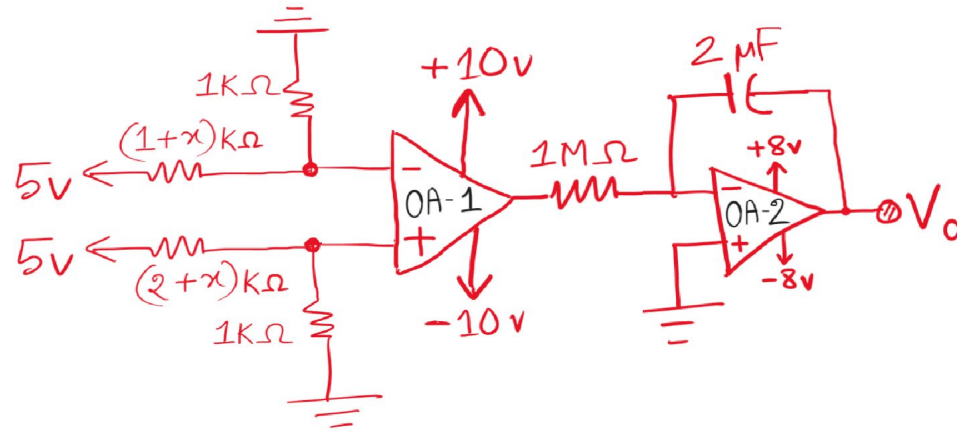

In the circuit given above, $x = \text{last digit of your student ID}$

- (a) **Analyze** the circuit and **determine** the voltage at the inverting, non-inverting terminals and the output of OA-1. [2+2+2]
- (b) **Determine** the highest V_O you can get from this circuit. **Explain** briefly. [1]
- (c) **Analyze** the circuit to **determine** the output voltage, V_O of OA-2 and **plot** V_O vs. time. **Label** the plot appropriately. [at $t = 0, V_O = 0$] [3]

(a)

At OA-1

$$V^+ = 5v \times \frac{1k\Omega}{(1+2+x)k\Omega} = \left(\frac{5}{3+x}\right)v$$

$$V^- = 5v \times \frac{1k\Omega}{(1+1+x)k\Omega} = \left(\frac{5}{2+x}\right)v$$

$$\therefore V^- > V^+$$

$$\therefore \text{The output voltage of OA-1, } V_{O(OA-1)} = -10v$$


- (b) Since, the output voltage of an op-amp cannot exceed its supply voltage,

$$V_O(\text{max}) = 8 \text{ V}$$


(c)

$$V_O = -\frac{-10}{2} \int_0^t dt$$


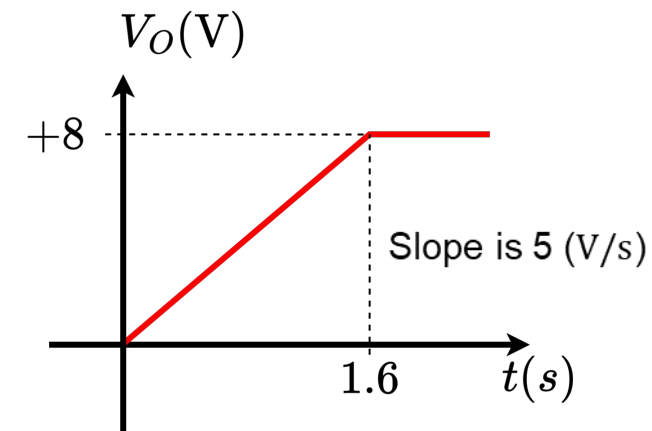
$$V_O = \begin{cases} 5t, & t < \frac{5}{8} \text{ s} \\ 8, & t \geq \frac{5}{8} \text{ s} \end{cases}$$



Q3

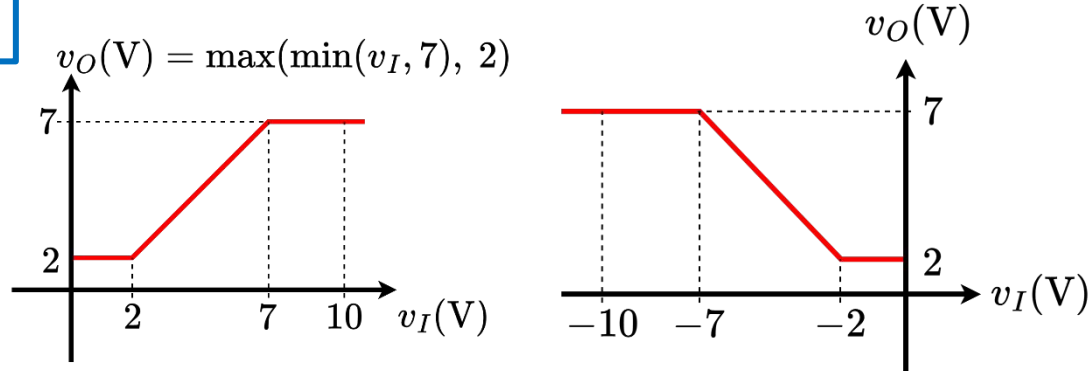

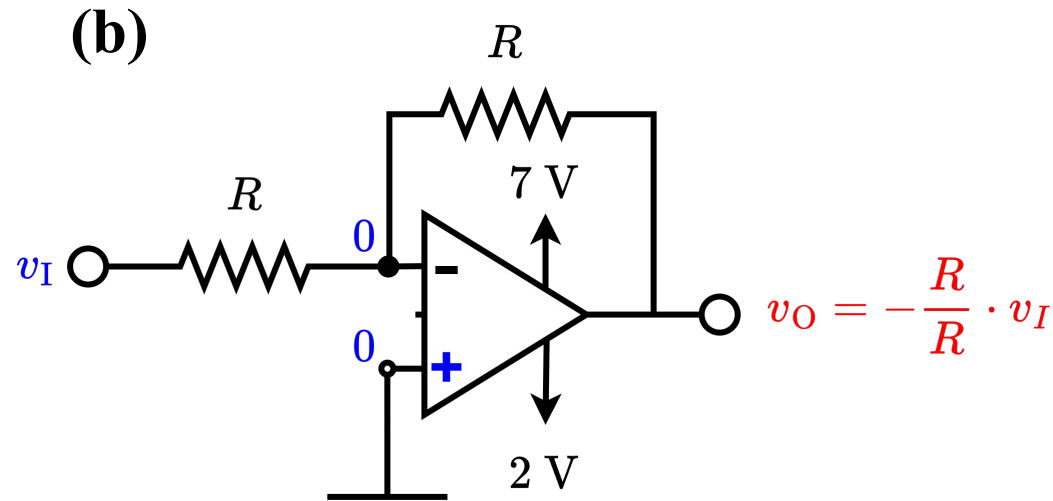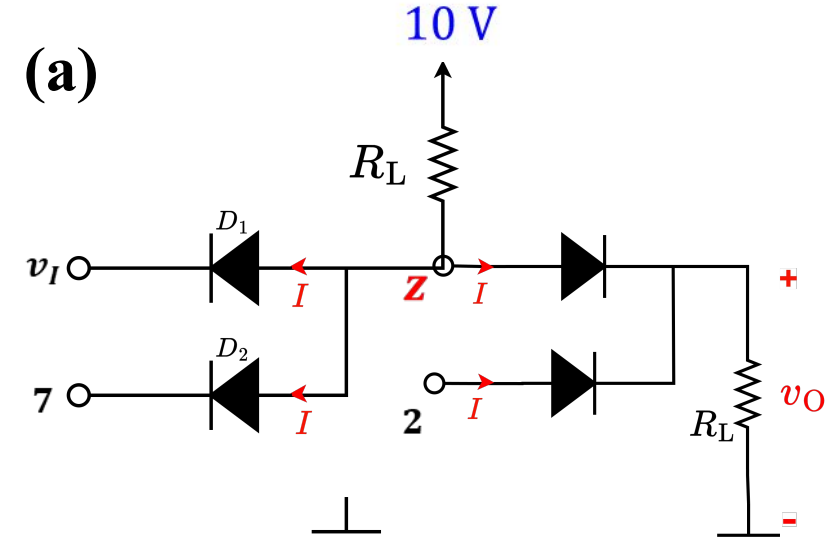- (a) Design separate circuits, using only diodes, to implement the following functions,
 $z = \min(v_I, 7)$ and $v_O = \max(z, 2)$. [3+3]
- (b) Design a circuit using Op-Amp to implement the VTC on the right. [3]
- (c) Determine which of the following logic gates can be built with diodes and explain briefly: (i) XOR, (ii) XNOR. [1]



(c)

None of the logic gates can be build using just diodes, because diodes alone cannot be used for creating the **inverter** logic needed for composing the XOR or XNOR logic function.

Soln: (a) Only S_1 is ON : Assume the diode 'ON', (Nodal Analysis) $V_x = \text{right-side node of the diode}$

$$\Rightarrow v_x = 4.171\text{V} \sim 4.173\text{V} [100\text{k}\Omega \sim 109\text{k}\Omega]$$

$$\Rightarrow I_{D1} (\text{left to right}) = \frac{5 - (v_x + 0.7)}{1.2} + \frac{0 - (v_x + 0.7)}{100 + X} = 0.059 \sim 0.061 \text{ mA} > 0 \text{ mA}$$

\therefore D1 **conducts (short)** current and $I_{D1} = 0.059 \text{ mA} \sim 0.61 \text{ mA} [100\text{k}\Omega \sim 109\text{k}\Omega]$

(b) Only S_2 is ON: Back to back diodes. $I_{D23} = 0 \text{ mA}$

Q4

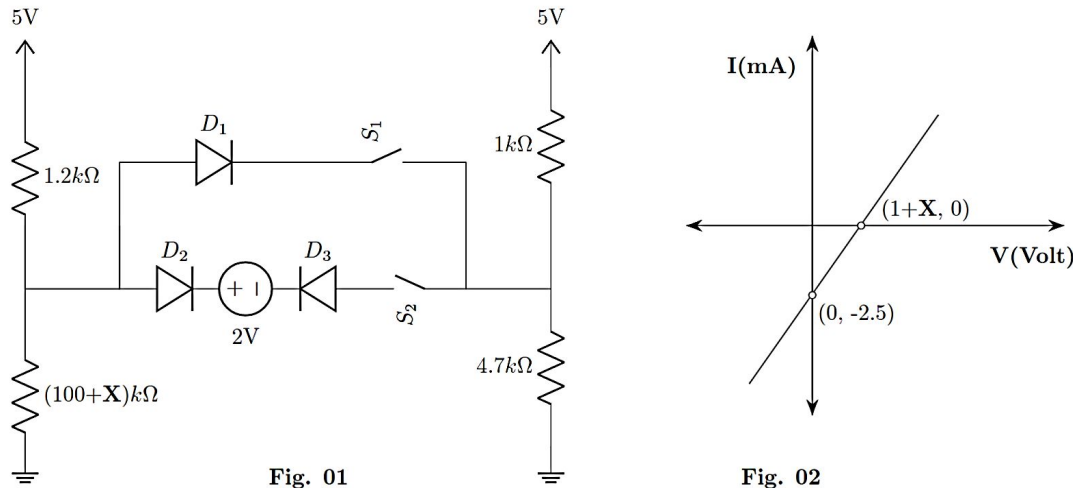


Fig. 01

Fig. 02

In Fig.01, a circuit is shown with two 'off' switches, S_1 and S_2 where $V_{D0} = 0.7\text{V}$.

Fig.02 represents the IV-curve of an unknown device.

Assume, X = Last digit of your Student ID.

(a) Calculate the current passing through the diode D_1 , if only S_1 is 'on'. [03]

(b) Calculate the current passing through the diodes D_2 and D_3 . If only S_2 is 'on'. [04]

(c) Determine and draw the unknown component of Fig. 02 with parameters. [02+01]

(c) Line Equation: $I = 2.5 \text{ V} - 2.5 \sim I = 0.25 \text{ V} - 2.5 [(1,0) \sim (10,0)]$

$$\therefore R = (1/m) \text{ k}\Omega = 0.4 \text{ k}\Omega \sim 4 \text{ k}\Omega [(1,0) \sim (10,0)]$$

\therefore [Either] Series Voltage Source, $V_0 = 2.5 \times R = 1 \text{ V} \sim 10 \text{ V}$

[or] Parallel Current Source, $I_0 = 2.5 \text{ mA}$