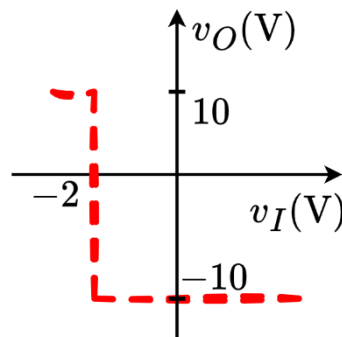


- ✓ Write down your student ID on the **top right corner of each of the pages**.
- ✓ Clearly write the solutions, along with the questions, on white paper with black ink (no need to use color pen, don't use pencils).
- ✓ Use **CamScanner**, or **Adobe Scan**, or **Microsoft Office Lens**, or any other software to scan the pages and make a **single PDF file**.
- ✓ After creating the PDF, make sure that **(a)** there are no pages missing, **(b)** all of the pages are legible, **(c)** your student ID on each page are visible.
- ✓ Please note, **collaboration ≠ copying**. You are allowed to discuss the questions and clear confusion you might have, but you have to write your solutions independently and be able to explain your answers during a random viva.
- ✓ **[Very Important]** Rename the PDF in the following format: "**A1_StudentID_FullNameWithoutSpace.pdf**". For example, if my student ID is 12345678 and my name is Shadman Shahid, the filename should be "**A1_12345678_ShadmanShahid.pdf**".
- ✓ **Submission Link:** <https://forms.gle/j81vXAmKcUwarxZy8>

[CO3] Question 1:

14 Marks

- a) Design a circuit using **op-amp** that has the voltage transfer characteristics as shown in the figure below. 4
 $v_O(\text{V})$ is the **output voltage** and $v_I(\text{V})$ is the **input voltage**.



- b) A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure **10** in a water tank. The valve operates on **ACTIVE LOW** logic. (i.e., the valve is OPENED when given a LOW voltage of **1 V**, but remains CLOSED when provided a HIGH voltage of **6 V**.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.

At 0.5 atm pressure	At 1 atm pressure	At 1.5 atm pressure
$v_{0.5 \text{ atm}} = 0.5 \text{ V}$	$v_{1 \text{ atm}} = 3 \text{ V}$	$v_{\text{low}, 1.5 \text{ atm}} = 5.5 \text{ V}$

The pressure in the water tank can be measured by the formula $P = h\rho g$, where P , (in **Pascals (Pa)** unit) is the water pressure, h is the height of water in the tank (in **metres**), $\rho (= 1000 \text{ kgm}^{-3})$ is the density of water and g is the acceleration due to gravity (in ms^{-2}).


[1 atm = 101325 Pa]

- i. **Design** a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds **10 m**.
- ii. **Draw** the voltage transfer characteristics (VTC) of the designed Op-Amp.

Question 2:


10 Marks

- a) Draw the voltage transfer characteristic (VTC) curve (v_O vs v_I) from the adjacent waveform graph. Also draw the **Op-Amp Circuit** that would give rise to such a VTC.

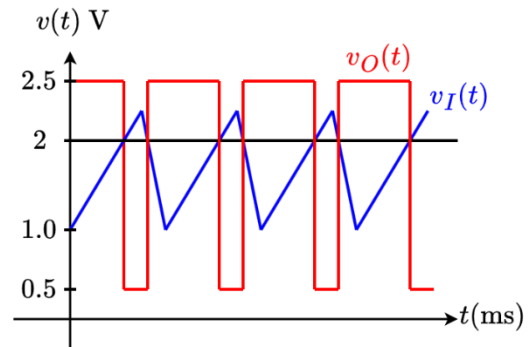

[CO3] 3

- b) Draw the voltage transfer characteristic (VTC) curve (v_O vs v_I) from the adjacent Op-Amp circuit.


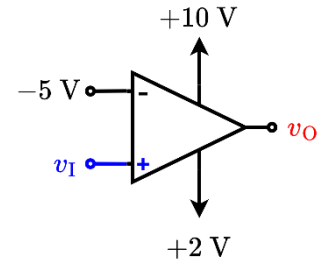


[CO2] 2

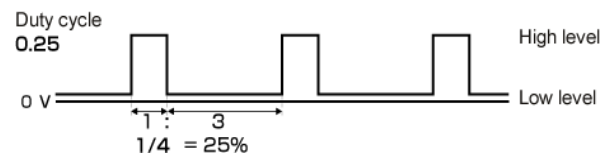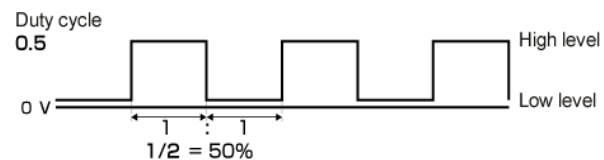- c) **Design** an op-amp circuit to transform the sinusoidal voltage, $v_I = 5 \cdot \sin\left(\frac{2\pi}{5} \cdot t\right)$ (t is in units of **ms**, and time-period T is 5 ms), to:
[You must evaluate V_{REF}]

[CO3] 5

- A square wave with a duty cycle of **50%**.
- A square wave with a duty cycle of **25%**.




[Duty Cycle: Time of positive half cycle \div Time period]

For more information on duty cycle, click [here!](#)

[Hint: If $y = A \cdot \sin(\theta)$ is a sinusoidal function with period of 2π then $\theta = \sin^{-1}\left(\frac{y}{A}\right)$ and $\pi - \sin^{-1}\left(\frac{y}{A}\right)$. So, for 25% duty cycle find the value of y for which $\Delta\theta = \left(\pi - \sin^{-1}\left(\frac{y}{A}\right)\right) - \sin^{-1}\left(\frac{y}{A}\right) = \frac{\text{Time period}}{4} = \frac{\pi}{2}$]

[CO2] Question 3:

10 Marks

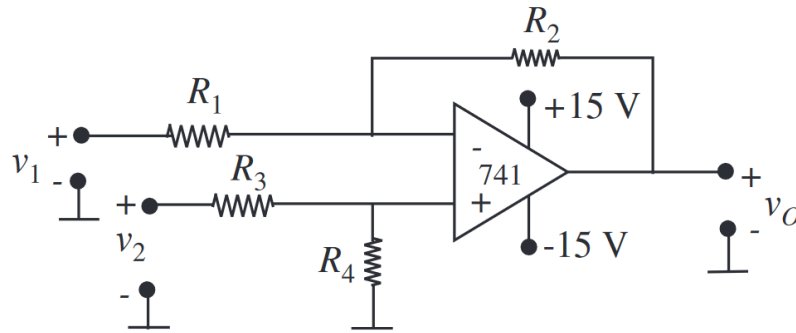


Answer the following questions dealing with the above circuit.

- Using the ideal Op Amp model, derive an expression for the output voltage v_O in terms of v_1 , v_2 , R_1 , R_2 , R_3 , and R_4 . 4
- Does connecting a load resistor R_L between the output and ground change the previous expression for v_O ? Why? 2
- Let $v_1 = v_2$ and $R_1 = 1 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, and $R_3 = 1.5 \text{ k}\Omega$. Find R_4 so that $v_O = 0$. 2
- Let $v_2 = 0$ and $v_1 = 1 \text{ V}$. Using the preceding resistor values (including that computed for R_4), find v_O . 2

[CO3] Question 4:

6 Marks

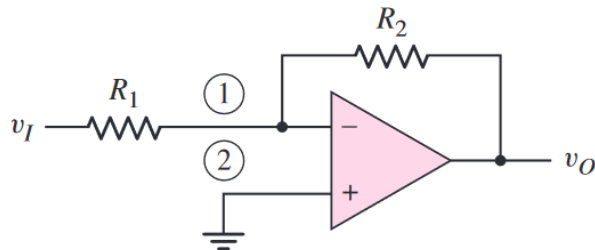Design the circuit below such that the closed loop voltage gain is $A_{CL} = -25$. The maximum current in any resistor is to be limited to $10 \mu\text{A}$ with the input voltage in the range $-25 \leq v_I \leq 25 \text{ mV}$.



- What are the values of R_1 and R_2 ? 4
- What is the range of output voltage v_O ? 2