

**Brac University**
**Set: 01**

Semester: Summer 2023

Course No: CSE251

Course Title: Electronic Devices and Circuits

Section: 1 to 10

Final Exam

Full Marks: 30

Time: 1 hour 30 minutes


Date: 03 September, 2023

 Answer **any 3 out of 4** questions. All the questions carry equal marks.

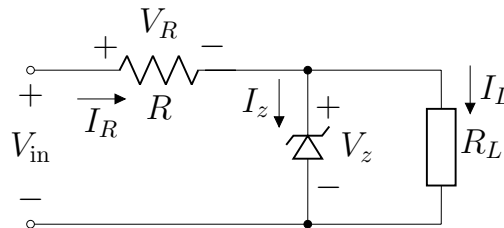**Question 1 [CO3]**

10

A Zener diode voltage regulator has a regulation voltage of 5.1 V when the current through the Zener diode is 50 mA. It is characterized by the parameters,  $r_z = 50 \Omega$ ,  $I_{ZK} = 5 \text{ mA}$ .




- Determine the cut-in voltage,  $V_{Z0}$  of the zener diode. [1.5]
- Assume, the nominal value of the supply voltage,  $V_{in}$  is 15 V and  $R = 200 \Omega$ . Calculate  $I_R$ ,  $R_L$  and  $I_L$  for the worst case scenario. [1+1+1]
- Now, assume,  $R_L$  and  $R$  are both  $100 \Omega$  each. Calculate the minimum value of the supply voltage  $V_{in}$  at the worst case scenario. [3]
- The supply voltage of the regulator is now given as  $15 \pm 1 \text{ V}$ . Design the voltage regulator circuit, i.e., determine the value of  $R$ , such that even in the worst-case scenario, voltage regulation is maintained and the circuit sustains a load current of 80 mA. [2.5]

**Bonus:** Analyze the effect of decreasing the load resistance,  $R_L$  and explain briefly. [2]

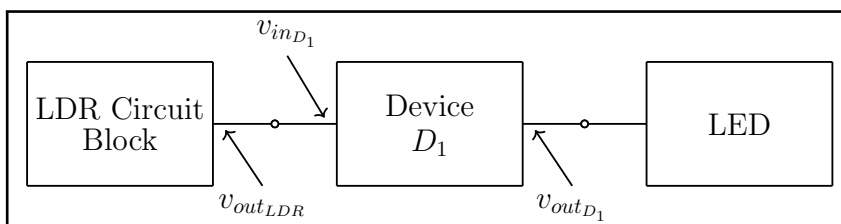**Question 2 [CO1]**

10

Rosa has a switching device,  $D_1$  built with 2 MOSFETs. The MOSFETs have the following parameters,  $k = 1 \text{ mA/V}^2$  and  $V_T = 0.2 \text{ V}$ . The device turns ON an LED light in her dollhouse at night and turns the light OFF during the day. The supply voltage of the device is,  $V_{SS} = 10 \text{ V}$  and the load resistance is  $R_L = 10 \text{ k}\Omega$ . The input voltage of the device,  $v_{inD1}$  is taken from the output voltage of an LDR Circuit Block,  $v_{outLDR}$  as shown in the diagram below. Rosa measured the voltages and made the following table where, **HIGH**  $\equiv 5 \text{ V}$  and **LOW**  $\equiv 1.5 \text{ V}$ .



Time	$v_{outLDR}$	$v_{inD1}$	$v_{outD1}$
Day	LOW	LOW	LOW
Night	HIGH	HIGH	HIGH

- Identify and explain the logical operation of the switching device,  $D_1$ . [1+1]
- Draw the circuit diagram of the device,  $D_1$  with proper labeling. [2]
- Calculate the on-state resistance,  $R_{ON}$  of the 1st MOSFET of the device. [2]
- Draw the Voltage Transfer Characteristic (VTC) of the device with proper labeling. [2+2]

**Bonus:** Determine the  $W/L$  sizing of the 1st MOSFET. [2]

## Equations for MOSFET

**Cut-off:**  $I_D = 0$ , if  $V_{GS} < V_T$

**Triode:**  $I_D = k \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$ , if  $V_{GS} \geq V_T$  and  $V_{DS} < (V_{GS} - V_T)$

**Saturation:**  $I_D = \frac{1}{2} k (V_{GS} - V_T)^2$ , if  $V_{GS} \geq V_T$  and  $V_{DS} \geq (V_{GS} - V_T)$

### Question 3 [CO3]

10

Answer the following questions for **Figure-1** where  $R_1 = 1k\Omega$ ,  $R_2 = 2k\Omega$ ,  $R_3 = 3k\Omega$ ,  $R_4 = 4k\Omega$ .

- Why a MOSFET can be used as a switch? **Explain** briefly. [2]
- Analyze** the circuit in *Figure-1* to **determine** the values of  $I_C$ ,  $I_B$ ,  $I_E$ ,  $v_C$  of  $T_1$ . [3]
- Analyze** the circuit in *Figure-1* to **determine** the value of  $I_{DS2}$ ,  $v_O$  of  $T_2$ . [5]

**Bonus: Design** a circuit with the boolean inputs A, B, C, D using ideal MOSFETs (S-model) to implement the logic function,  $f = \overline{A.C} + B.D$  [2]

### Question 4 [CO1, CO3]

10

- Draw** the I-V characteristic of a BJT. **Indicate** the operating regions with proper labeling. [2]
- A linear amplifier follows the equation,  $V_{out} = -5V_{in}$  where the valid input range is -10V to +10V. **Illustrate** the Voltage Transfer Characteristic (VTC) of the amplifier with proper labels. [2]
- For the BJT CE Amplifier of **Figure-2**,  $v_{IN} = 2 + 0.2 \sin(100\pi t)$  and  $v_O = 4 - 2 \sin(100\pi t)$ . **Design** the Amplifier circuit, i.e., **calculate** the value of  $V_S$ ,  $R_L$  and  $R_i$ . [2+2+2]

**Bonus: Identify** the lowest value of the input voltage for which amplification occurs. **Explain** your reasoning. [2]

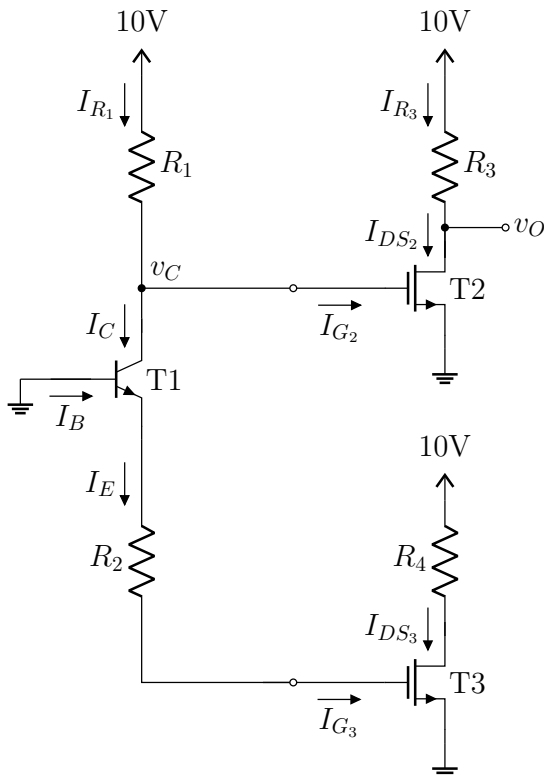


Figure-1

#### for BJT

$\beta = 100$   
 $\alpha = 0.99$   
 $v_{BE(Active)} = 0.7V$   
 $v_{BE(Saturation)} = 0.8V$   
 $v_{CE(Saturation)} = 0.2V$

#### for MOSFET

$V_T = 1V$   
 $k = 5mA/V^2$

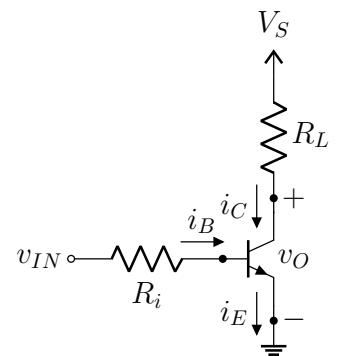


Figure-2