
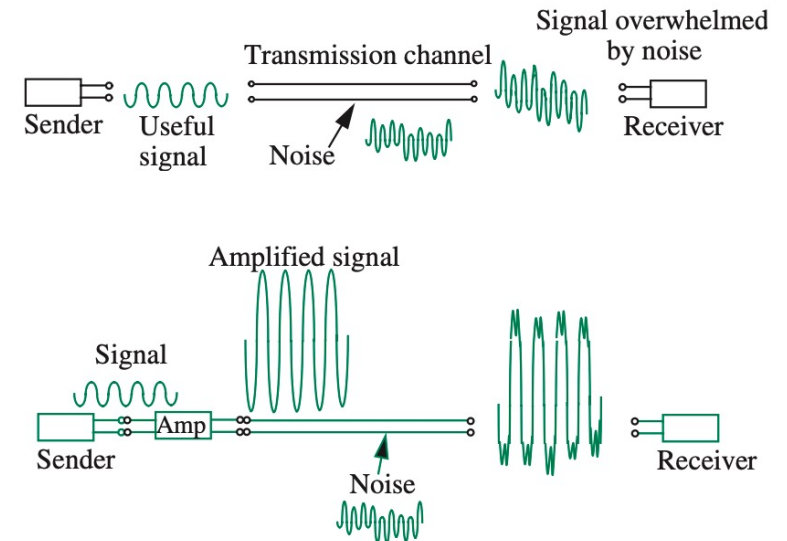


# Lecture 18

Amplifiers Using Transistors

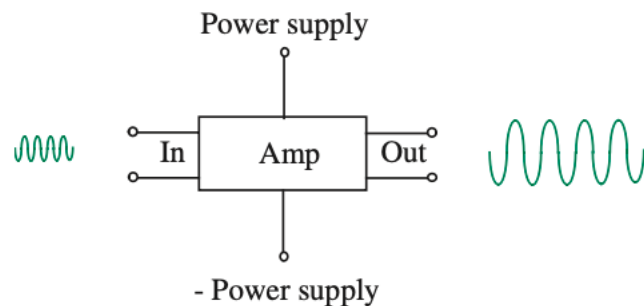
# Amplifier

- Linear amplifier  $\Rightarrow OUT = k \times IN$
- OUT/IN can be voltage or current
- Amplifier must provide power gain ( $P_{OUT} > P_{IN}$ ), hence need power supply
- Usage: during communication





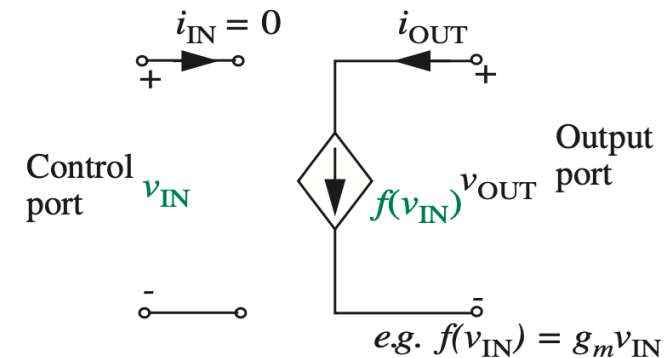
# Types of Amplifier and Circuit Realization

- Depending on input (voltage or current) and output (V or I) – 4 types
  1. Voltage amplifier (In = V, Out = V)
  2. Current amplifier (In = I, Out = I)
  3. Transconductance amplifier (In = V, Out = I)
  4. Transresistance amplifier (In = I, Out = V)
- How to realize (make) amplifiers using circuits? Dependent Source!
- E.g, for transconductance amplifier  $I_{out} = g_M \times V_{in} \Rightarrow$  VCCS (voltage controlled current source)



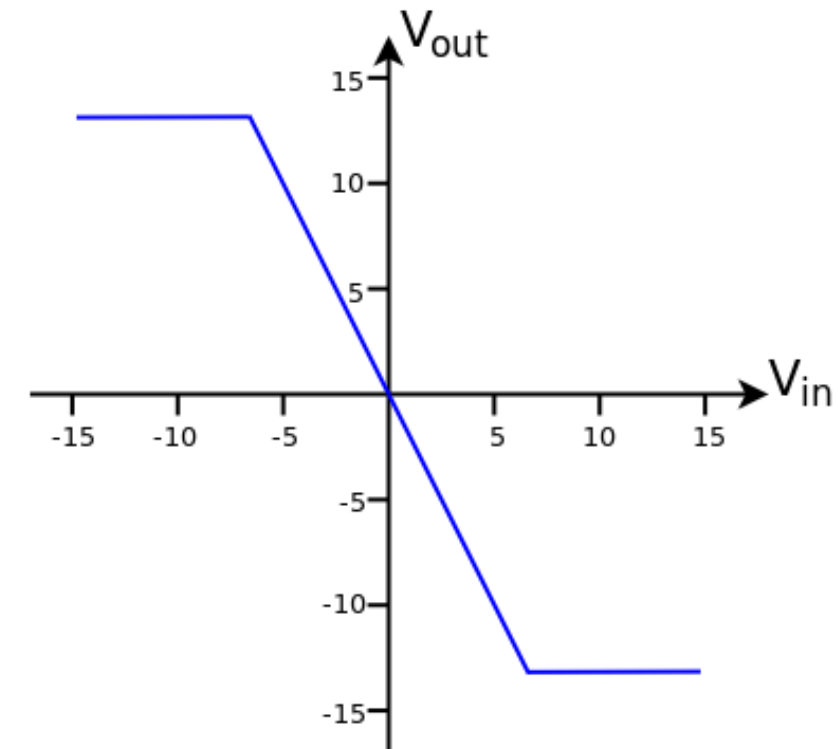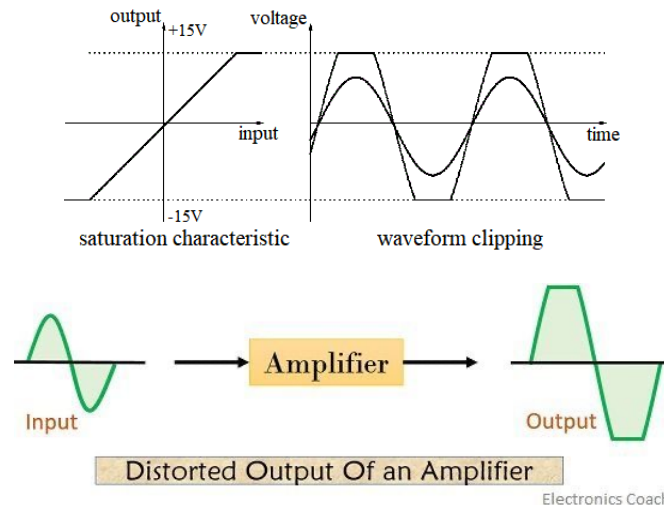
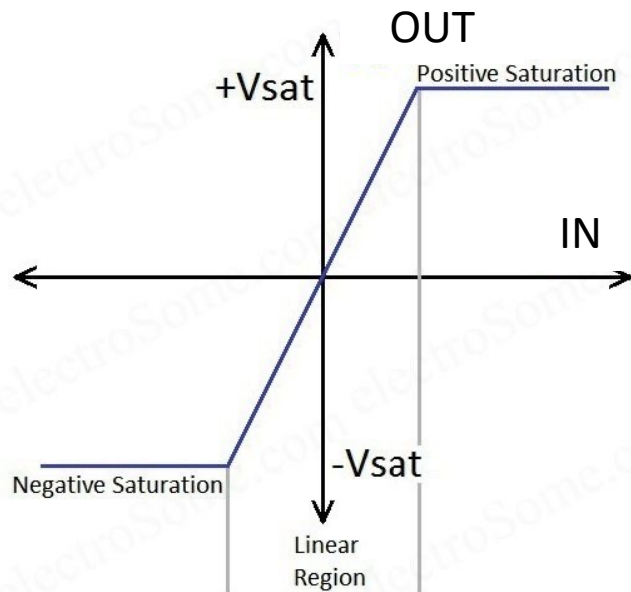
# Amplifier TC

- Saturation due to limited power supply
- Input must be within a **valid input range**, otherwise output will be distorted
- Inverting amplifier, gain = -ve.




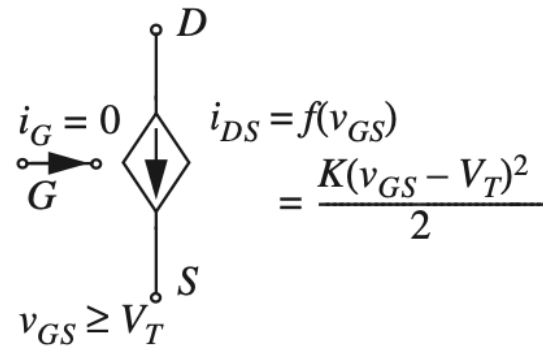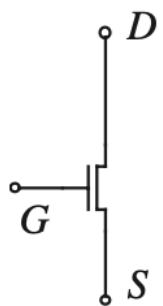
# Making Dependent Sources

- BJT in Active mode acts like a current controlled current source
- MOSFET in Saturation mode acts like a voltage controlled current source
- So, we can use them to make amplifiers!
- BJT in Active is preferable since the relation is linear





Valid when  $v_{DS} \geq v_{GS} - V_T$

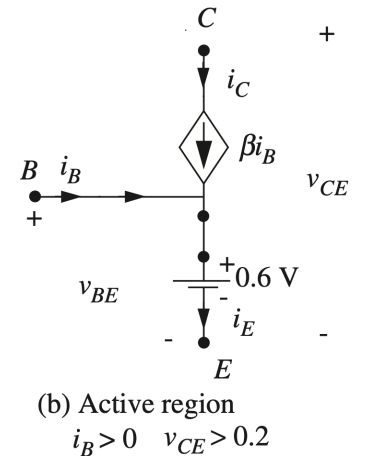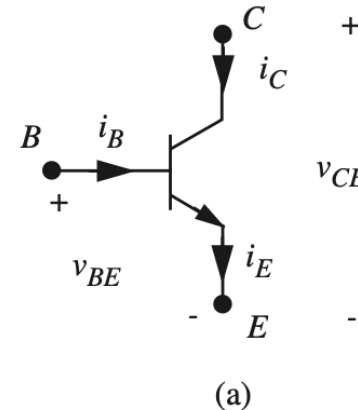

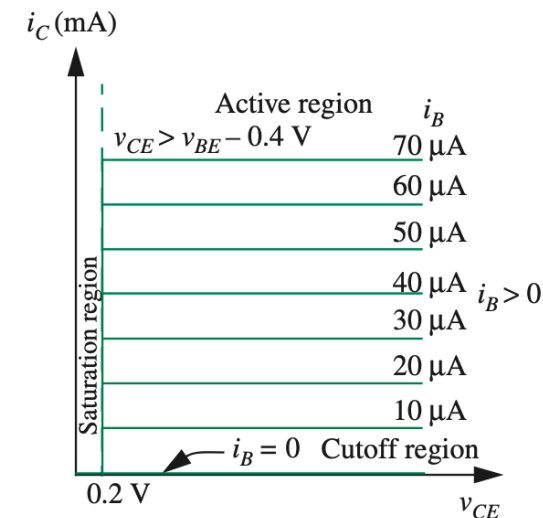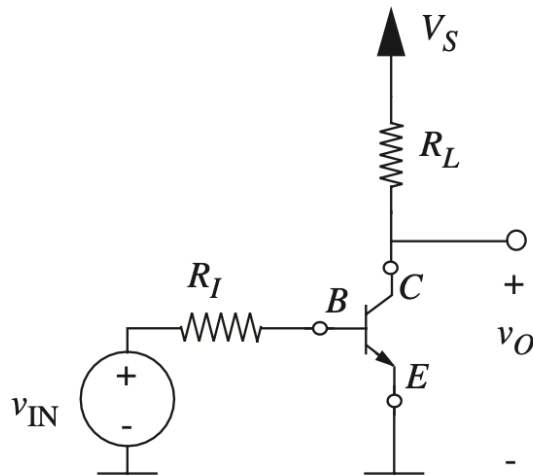
# BJT Common Emitter Amplifier

- When BJT is in active mode,  $I_{out} = \beta I_{in}$  here  $I_{in} = I_B$  and  $I_{out} = I_C$
- $R_I$  converts input voltage ( $v_{IN}$ ) to input current
- $R_L$  converts output current to output voltage ( $v_o$ )
- But how does it work? Need to know relation between  $v_o$  and  $v_{IN}$



# Finding VTC of CE Amplifier

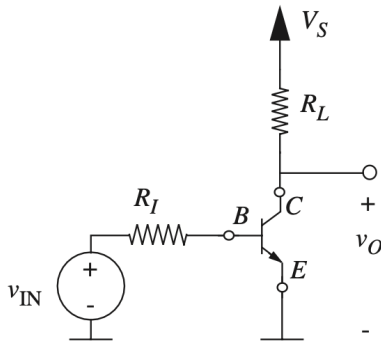

**KVL:**  $v_O = v_{CE} = V_S - I_C \times R_L$  (True for any mode)

**Cutoff:**  $I_B = 0 \Rightarrow v_{BE} \leq 0.7V \Rightarrow v_{IN} \leq 0.7V$

$v_o = V_S - 0 \times R_L = V_S$  (since in cutoff  $I_B = 0$ )

**Active:**  $v_{CE} = v_o > 0.2V$

$$V_S - I_C R_L > 0.2V \Rightarrow I_C < (V_S - 0.2)/R_L$$

$$\text{Since } I_C = \beta I_B \Rightarrow I_B < (V_S - 0.2)/\beta R_L$$



$$\text{Since } v_{in} = I_B R_I + 0.7 \Rightarrow v_{in} < 0.7 + \left( \frac{V_S - 0.2}{\beta R_L} \right) R_I$$

So as long as  $0.7 < v_{IN} < 0.7 + \left( \frac{V_S - 0.2}{\beta R_L} \right) R_I$  BJT will be in Active and

$$\begin{aligned} v_o &= V_S - I_C \times R_L \\ \Rightarrow v_o &= V_S - \frac{\beta(v_{IN} - 0.7)}{R_I} R_L \Rightarrow v_o = \left( V_S + \frac{0.7\beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} v_{IN} \end{aligned}$$

**Saturation:**  $v_{in} > 0.7 + \left( \frac{V_S - 0.2}{\beta R_L} \right) R_I \Rightarrow v_o = v_{CE} = 0.2V$

# VTC of CE Amplifier

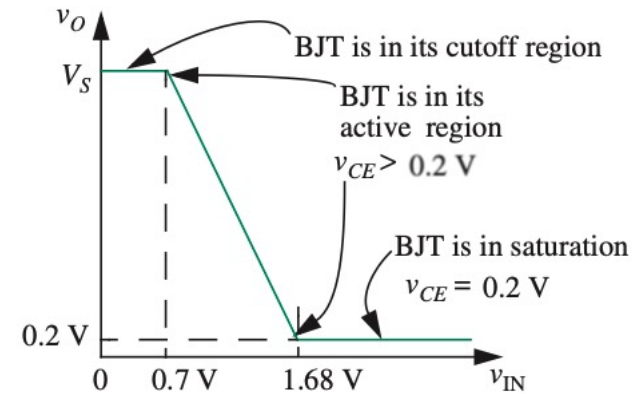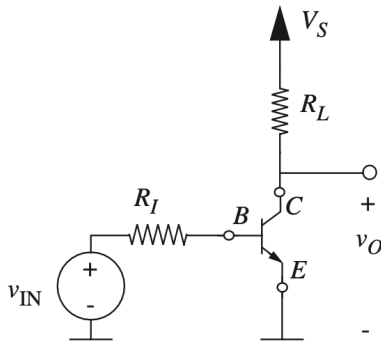


Assume that  $R_I = 100 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  $\beta = 100$ , and  $V_S = 10 \text{ V}$ .

$$\Rightarrow 0.7 + \left( \frac{V_S - 0.2}{\beta R_L} \right) R_I = 0.7 + \left( \frac{10 - 0.2}{100 \times 10 \text{ k}\Omega} \right) 100 \text{ k}\Omega = 1.68 \text{ V}$$

$$\text{And } v_o = \left( V_S + \frac{0.7 \beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} v_{IN} \Rightarrow v_o = 17 - 10v_{IN}$$

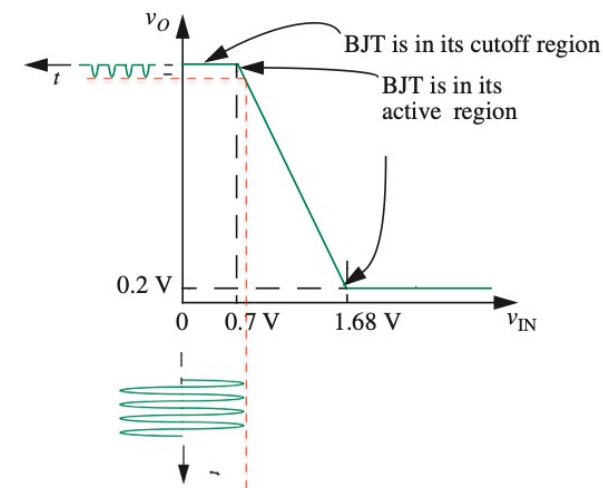But the TC does not look like that of an amplifier!




In fact, if  $v_{IN} = 1 \sin \omega t$ , output will be distorted since for  $v_{IN} \leq 0.7$  in cutoff, and  $0.7 < v_{IN} < 1$  in active. Hence, does not amplify “Large” Signals

$v_{IN} \leq 0.7$	$v_O = 10$	Cutoff mode
$0.7 < v_{IN} < 1.68$	$v_O = 17 - 10v_{IN}$	Active mode
$v_{IN} \geq 1.68$	$v_O = 0.2$	Saturation mode



# Small Signal Amplification


$v_{IN} \leq 0.7$	$v_O = 10$	Cutoff mode
$0.7 < v_{IN} < 1.68$	$v_O = 17 - 10v_{IN}$	Active mode
$v_{IN} \geq 1.68$	$v_O = 0.2$	Saturation mode

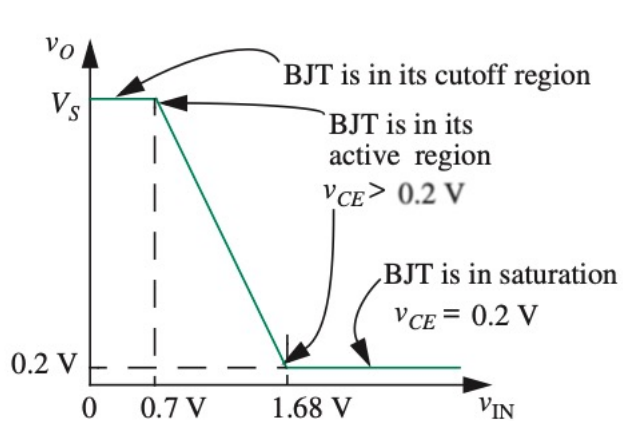

$v_{IN}$	$v_O$
0.5	10
0.7	10
1	7
1.3	4
1.4	3
1.5	2
1.6	1
1.7	0.2
1.8	0.2


- Overall gain,  $1.3\text{V } \Delta$  in inp,  $9.8\text{V } \Delta$  in out
- But non-linear overall
- **Red**: Linear (Active) Region
- $0.1\text{V}$  change in inp  $\Rightarrow 1\text{V}$  change in out
- 10-fold change!  $\Rightarrow$  Amplification!

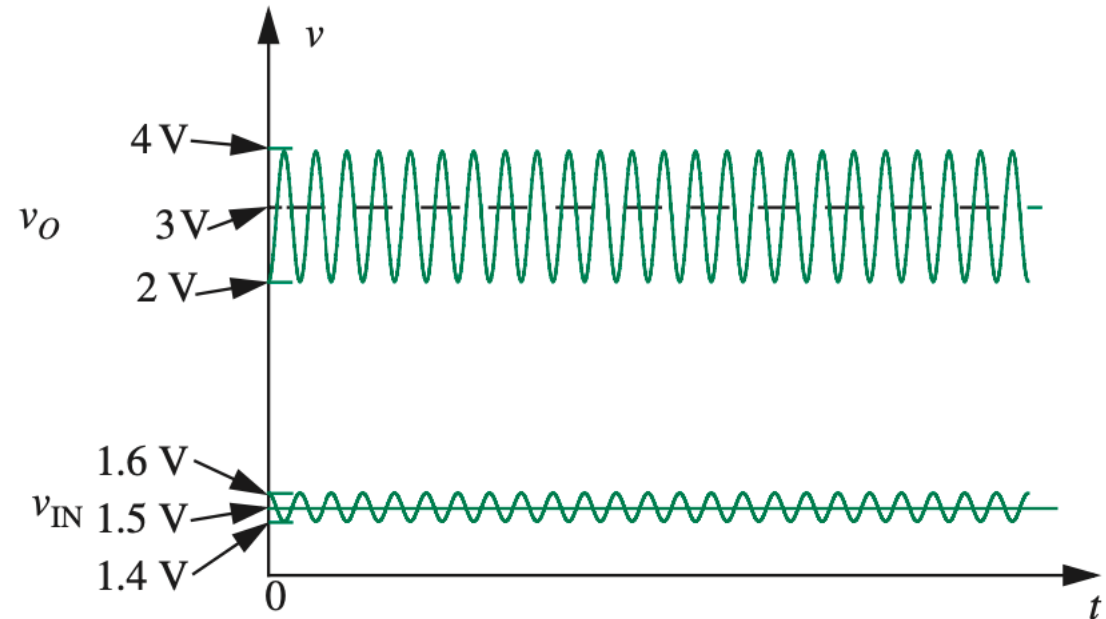- Say  $v_{IN} = 1.5 \pm 0.1\text{V}$ , then  $v_O = 2 \mp 1\text{V}$
- This means a "small" signal of  $0.1\text{V}$  amplitude with **input offset**  $1.5\text{V}$  will have a  $1\text{V}$  amplitude for the small signal output with an **output offset**  $2\text{V}$ , and gain  $k = -10$
- This is called **small signal amplification**



# Small Signal Amplification



$v_{IN} \leq 0.7$	$v_O = 10$	Cutoff mode
$0.7 < v_{IN} < 1.68$	$v_O = 17 - 10v_{IN}$	Active mode
$v_{IN} \geq 1.68$	$v_O = 0.2$	Saturation mode

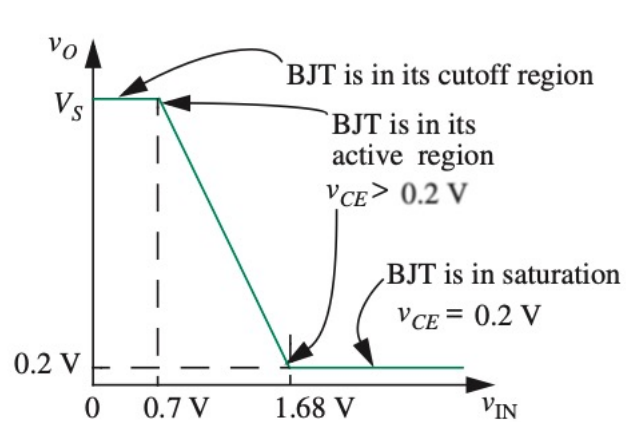


$v_{IN}$	$v_O$
0.5	10
0.7	10
1	7
1.3	4
1.4	3
1.5	2
1.6	1
1.7	0.2
1.8	0.2

- Overall gain, 1.3V  $\Delta$  in inp, 9.8V  $\Delta$  in out
- But non-linear overall
- **Red:** Linear (Active) Region
- 0.1V change in inp  $\Rightarrow$  1V change in out
- **10-fold** change!  $\Rightarrow$  Amplification!

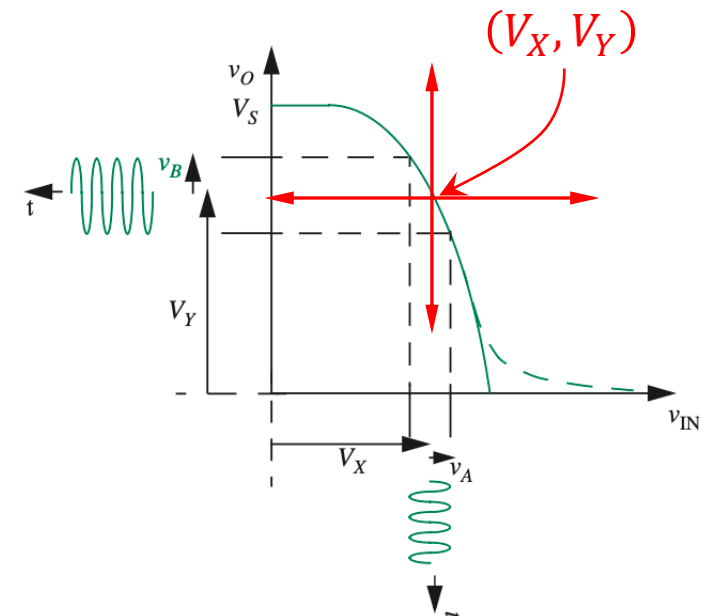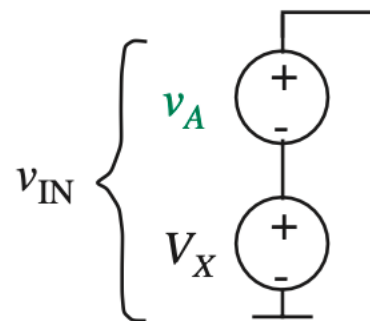- In general,  $v_{IN} = V_X + v_A \Rightarrow v_O = V_Y + v_B$
- Here,  $v_A$  and  $v_B$  are input/output small signals of interest and  $v_B = k \times v_A$ , where gain  $k = -\frac{\beta R_L}{R_I}$
- $V_X$  and  $V_Y$  are input/output biases,  $(V_X, V_Y)$  is called the **Operating point** or **Bias point** or **Q-point**
- **Biasing** is used to ensure BJT stays in Active



# Summary

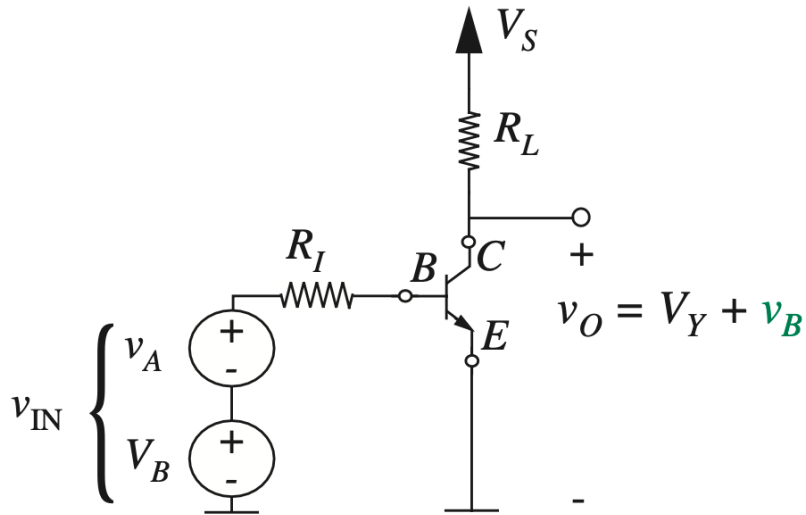


## BJT Common Emitter Amplifier


- Input small signal  $v_A$ , output small signal  $v_B$ . Both are AC signals
- $v_B = k \times v_A$ , where the gain  $k = -\frac{\beta R_L}{R_I}$
- $(V_X, V_Y)$  is called the **Operating point** or **Bias point** or **Q-point**. Both DC Offset
- $V_Y = \left( V_S + \frac{0.7\beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} V_X$

**Valid voltage range** The range of input for which the BJT in the circuit operate in the Active region.

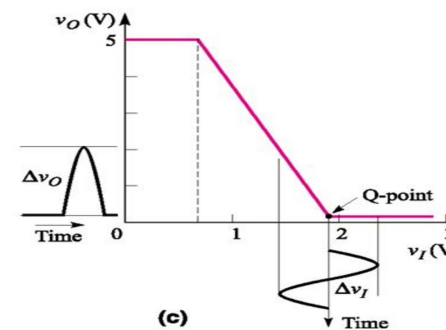If not maintained, output might be distorted



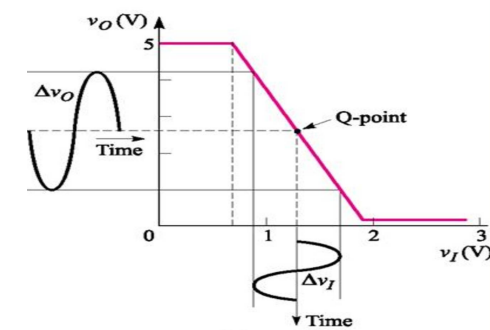Biased, but **Valid voltage range** not maintained



Biased, and **Valid voltage range** maintained

- Need to select Q-point or Bias point in such a way that input is within **Valid voltage range**
- In this case, **Valid voltage range**:  $0.7 < v_{IN} < 0.7 + \left( \frac{V_S - 0.2}{\beta R_L} \right) R_I$
- How to select Q-point? Best option: middle of active region, which will give maximum swing (peak-to-peak) for  $v_A$

# Example 1

Consider the BJT common emitter circuit with  $\beta = 100$ ,  $R_I = 100k\Omega$ ,  $R_L = 10k\Omega$ , and  $V_S = 10V$

We want to set bias the point in such a way that the DC portion of the input, i.e.,  $V_X = 1.2V$ .

Under small signal approximation, if the input  $v_{IN} = V_X + v_i(t)$ , the output will be  $v_O = V_Y + kv_i(t)$ . This means the output will be some DC value  $V_Y$  plus the amplified version of the small signal  $v_i(t)$ .

Here assume that  $v_i = 0.1 \cos \omega t$ .

- What is the value of DC part of the output, i.e.,  $V_Y$ ?
- What will be the value of gain  $k$  under small signal approximation?
- What is amplitude (peak-to-peak) of the input small signal waveform  $v_i(t)$ ?
- What is amplitude (peak-to-peak) of the output small signal waveform?

# Example 1

Consider the BJT common emitter circuit with  $\beta = 100$ ,  $R_I = 100k\Omega$ ,  $R_L = 10k\Omega$ , and  $V_S = 10V$

We want to set bias the point in such a way that the DC portion of the input, i.e.,  $V_X = 1.2V$ .

Under small signal approximation, if the input  $v_{IN} = V_X + v_i(t)$ , the output will be  $v_O = V_Y + kv_i(t)$ . This means the output will be some DC value  $V_Y$  plus the amplified version of the small signal  $v_i(t)$ .

Here assume that  $v_i = 0.1 \cos \omega t$ .

- What is the value of DC part of the output, i.e.,  $V_Y$ ?

$$V_X = 1.2, \text{ therefore } V_Y = \left( V_S + \frac{0.7\beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} V_X = 5$$

- What will be the value of gain  $k$  under small signal approximation?

$$k = -\frac{\beta R_L}{R_I} = -10$$

- What is amplitude (peak-to-peak) of the input small signal waveform  $v_i(t)$ ?


max = 0.1V, min = -0.1V. Therefore, peak-to-peak amplitude = 0.2V

- What is amplitude (peak-to-peak) of the output small signal waveform?

Amplitude of output =  $|k| \times \text{Amplitude of input} \Rightarrow 10 \times 0.2 = 2V$
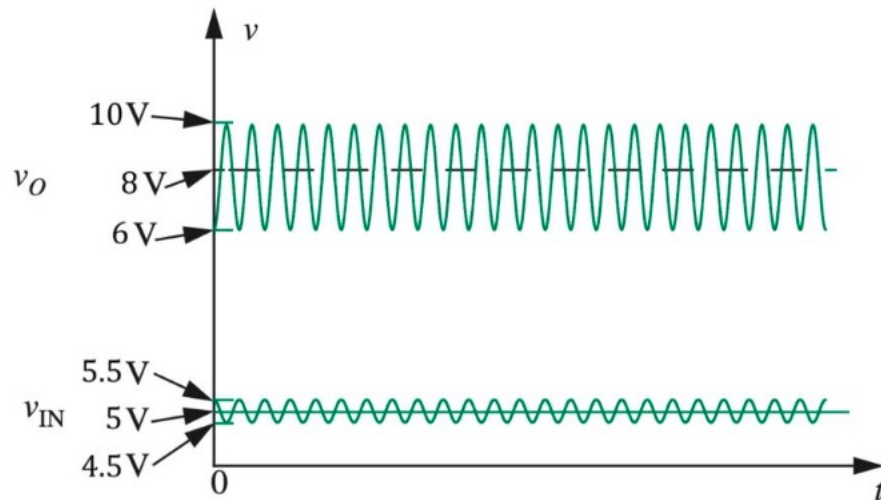
# Example 2


The input voltage of a common source amplifier is given as  $v_{IN} = V_X + v_i(t)$  and the output voltage is given  $v_O = V_Y + kv_i(t)$ . Here,  $v_i(t)$  is a sinusoidal voltage with amplitude  $a$ ,  $V_X$  is the input DC offset voltage,  $V_Y$  is the output DC offset voltage. The input and output waveforms are given below. Notice the output small signal is inverted compared to input small signal. Hence, the small signal gain,  $k$ , will be negative.



- What is the amplitude of the input small signal  $v_i(t)$ ?
- What is the amplitude of the output small signal?
- Hence, what is the small signal gain  $k$ ?
- From the above graph, what is the value of input DC voltage  $V_X$  and the output DC voltage  $V_Y$ ?
- Design the circuit, i.e., find the value of  $V_S$ ,  $R_I$ , and  $R_L$  to achieve given input-output voltage relation. Given  $\beta = 100$
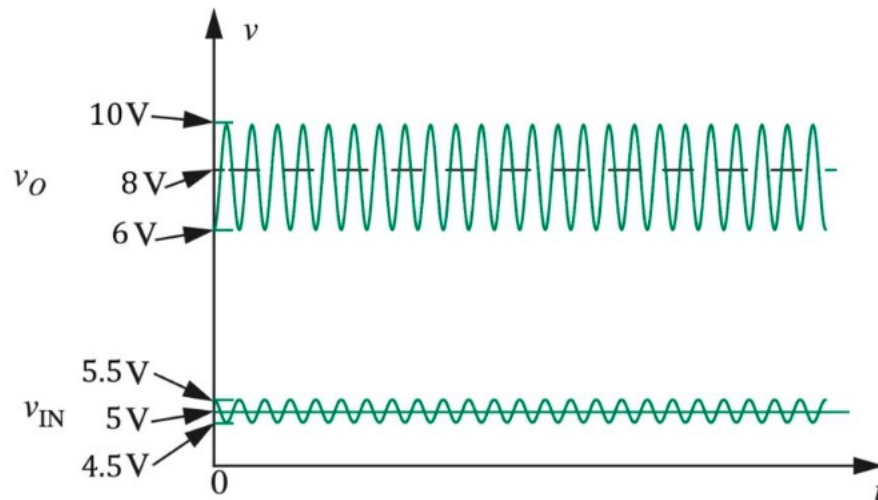
# Example 2


The input voltage of a common source amplifier is given as  $v_{IN} = V_X + v_i(t)$  and the output voltage is given  $v_O = V_Y + kv_i(t)$ . Here,  $v_i(t)$  is a sinusoidal voltage with amplitude  $a$ ,  $V_X$  is the input DC offset voltage,  $V_Y$  is the output DC offset voltage. The input and output waveforms are given below. Notice the output small signal is inverted compared to input small signal. Hence, the small signal gain,  $k$ , will be negative.



- What is the amplitude of the input small signal  $v_i(t)$ ? **0.5 V**
- What is the amplitude of the output small signal? **2 V**
- Hence, what is the small signal gain  $k$ ?  **$k = -\frac{2}{0.5} = -4$**
- From the above graph, what is the value of input DC voltage  $V_X$  and the output DC voltage  $V_Y$ ?  **$V_X = 5, V_Y = 8$**
- Design the circuit, i.e., find the value of  $V_S$ ,  $R_I$ , and  $R_L$  to achieve given input-output voltage relation. Given  $\beta = 100$ .
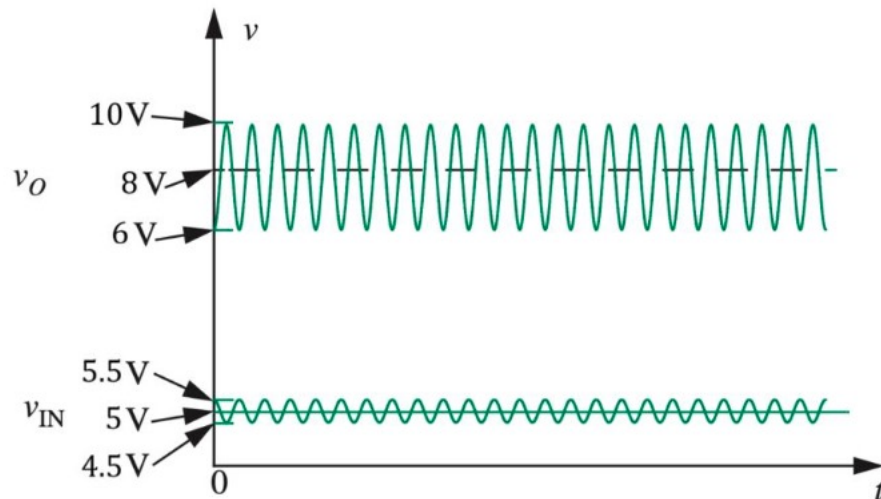
## Example 2

The input voltage of a common source amplifier is given as  $v_{IN} = V_X + v_i(t)$  and the output voltage is given  $v_O = V_Y + kv_i(t)$ . Here,  $v_i(t)$  is a sinusoidal voltage with amplitude  $a$ ,  $V_X$  is the input DC offset voltage,  $V_Y$  is the output DC offset voltage. The input and output waveforms are given below. Notice the output small signal is inverted compared to input small signal. Hence, the small signal gain,  $k$ , will be negative.



- Design the circuit, i.e., find the value of  $V_S$ ,  $R_I$ , and  $R_L$  to achieve given input-output voltage relation. Given  $\beta = 100$ .

$$k = -4 = -\frac{\beta R_L}{R_I} \Rightarrow \frac{\beta R_L}{R_I} = 4 \Rightarrow R_L = 0.04 R_I$$

$$\text{Let } R_I = 100k\Omega \Rightarrow R_L = 4k\Omega$$


$$V_Y = \left( V_S + \frac{0.7\beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} V_X \Rightarrow 8 = (V_S + 0.7 \times 4) - 4 \times 5$$
$$\Rightarrow V_S = 8 + 20 - 2.8 = 25.2 \text{ V}$$


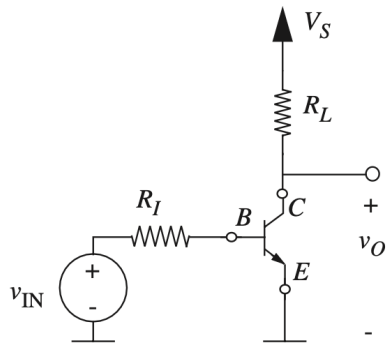
# Example 3

Choose an operating point for the amplifier below to maximize the input voltage swing.


Here  $R_I = 100\text{ k}\Omega$ ,  $R_L = 10\text{ k}\Omega$ ,  $\beta = 100$ ,  $V_S = 10\text{ V}$


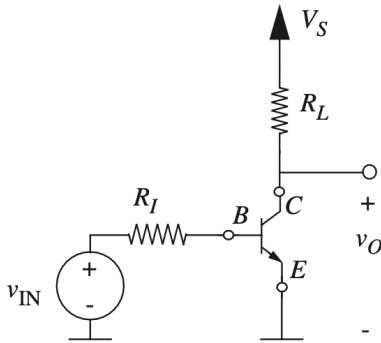
# Example 3

Choose an operating point for the amplifier below to maximize the input voltage swing.

Here  $R_I = 100\text{ k}\Omega$ ,  $R_L = 10\text{ k}\Omega$ ,  $\beta = 100$ ,  $V_S = 10\text{ V}$



**Solution:** BJT will be active for the **valid input range**:  $0.7 < v_{IN} < 0.7 + \left(\frac{V_S - 0.2}{\beta R_L}\right) R_I$

$$\text{Here, } 0.7 + \left(\frac{V_S - 0.2}{\beta R_L}\right) R_I = 0.7 + \left(\frac{10 - 0.2}{100 \times 10}\right) = 0.7 + 0.98 = 1.68\text{ V}$$

Therefore, **valid input range**:  $0.7\text{ V} < v_{IN} < 1.68\text{ V}$

For maximum input swing,  $V_X$  should be midway between the **valid input range**

$$\text{Hence, } V_X = \frac{0.7 + 1.68}{2} = 1.19\text{ V}$$

$$\text{Therefore, } V_Y = \left(V_S + \frac{0.7\beta R_L}{R_I}\right) - \frac{\beta R_L}{R_I} V_X = \left(10 + \frac{0.7 \times 100 \times 10}{100}\right) - \frac{100 \times 10}{100} \times 1.19 = 5.1$$

Therefore, maximum peak-to-peak input swing =  $(1.19 - 0.7) = (1.68 - 1.19) = 0.58\text{ V}$

**Note:**  $V_Y = 5.1$  is midway between the **valid output range**:  $0.2 \leq v_o < 10$