
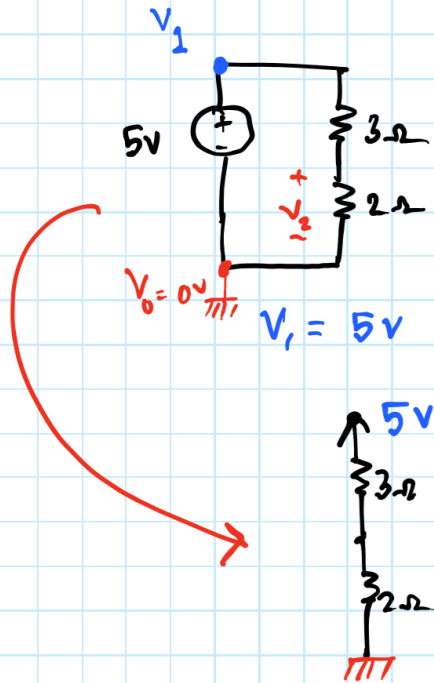


Alternative Circuit Representation

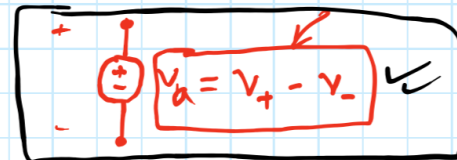


$$V_2 = \frac{2}{2+3} \times 5$$

voltage division




①

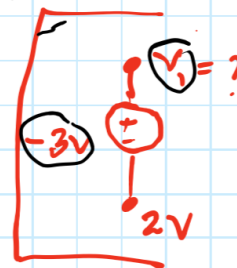

$$-3 = V_1 - 2$$

$$\Rightarrow V_1 = 2 - 3 = -1$$


②

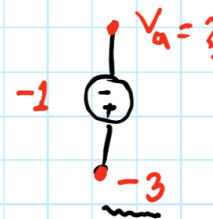

$$-1 = -3 - V_a$$

$$\Rightarrow V_a = -3 + 1 = -2$$



Example-2

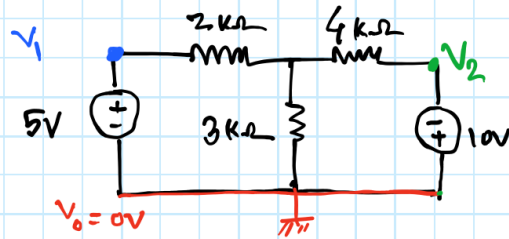



$$V_1 - 0 = 5 \Rightarrow V_1 = 5V$$

$$0 - V_2 = 10 \Rightarrow V_2 = -10V$$

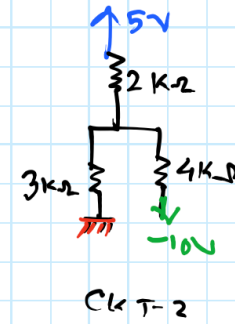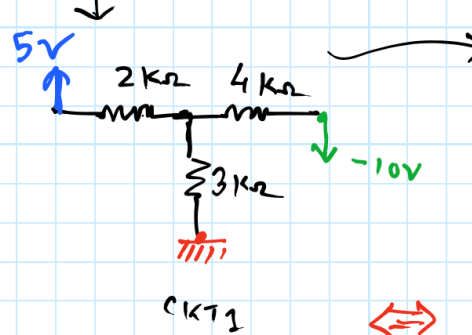Tips: Try to select GND node to reduce # floating voltage sources



Example-3

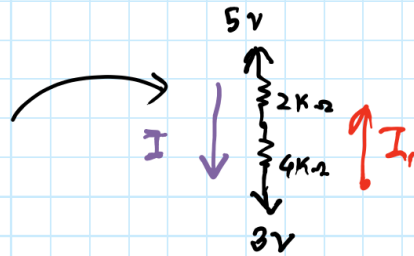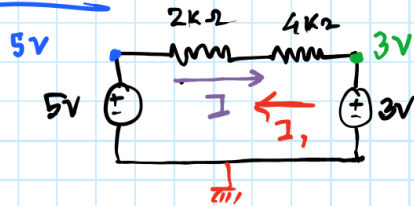

Ohm's law

$$V = iR$$

$$\Rightarrow i = \frac{V}{R}$$

→ voltage diff.
→ total resistance

$$I = \frac{5 - 3}{2 + 4} = \frac{2}{6} = \frac{1}{3} = 0.33 \text{ mA}$$

$$I_1 = \frac{3 - 5}{2 + 4} = \frac{-2}{6} = -\frac{1}{3} = -0.33 \text{ mA}$$



$$\text{mA} \times \text{k}\Omega = \text{V}$$


20301164

20101320



20101439

20101453


Example 4

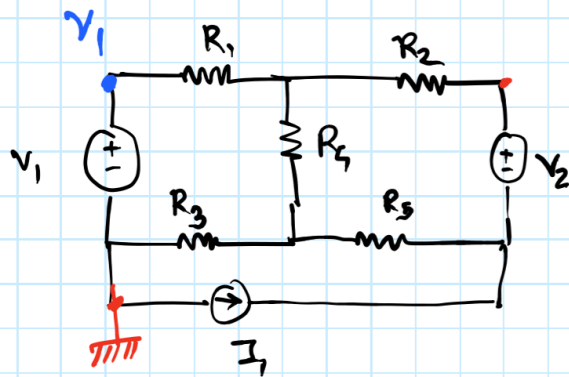

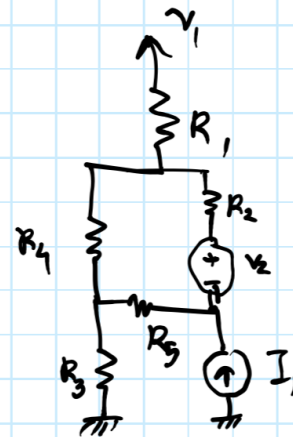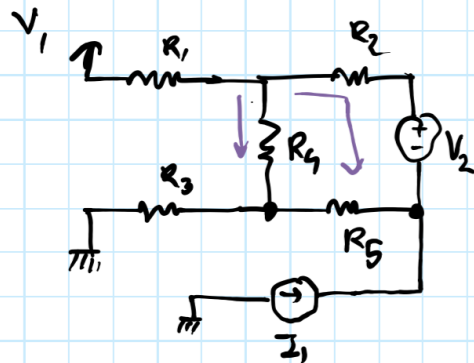floating voltage source [no terminals connected to ground]




KCL in A.R.

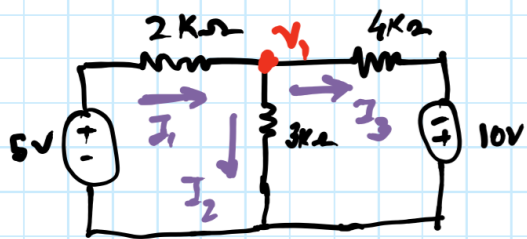

for V_1 node

$$\left. \begin{array}{l} I_1 \rightarrow \text{in} \\ I_2, I_3 \rightarrow \text{out} \end{array} \right\} -I_1 + I_2 + I_3 = 0$$

KCL in A.R.

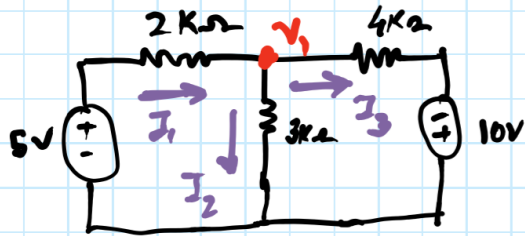


for V_1 node

$$\left. \begin{array}{l} I_1 \rightarrow \text{in} \\ I_2, I_3 \rightarrow \text{out} \end{array} \right\} -I_1 + I_2 + I_3 = 0$$

KCL: $\sum I = 0$
any node


one convention
out = +ve
in = -ve ✓

Exactly the same

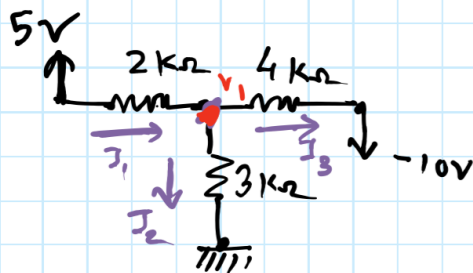


$$\left. \begin{array}{l} I_1 \rightarrow \text{in} \\ I_2, I_3 \rightarrow \text{out} \end{array} \right\} -I_1 + I_2 + I_3 = 0$$

KVL in A.R

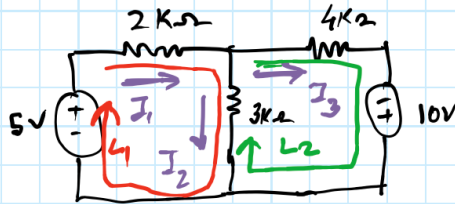

Loop \leftrightarrow Line

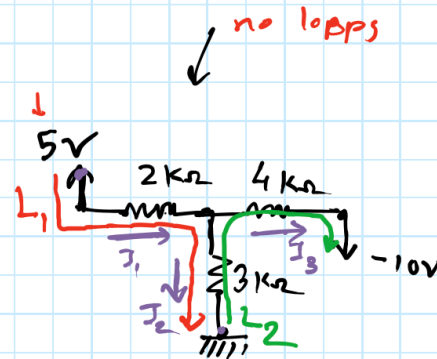

KVL: Loop $\rightarrow \sum v = 0$
along loop

Line $\rightarrow \sum v = V_{\text{start}} - V_{\text{end}}$
along line

$I \rightarrow \text{mA}$
 $\text{mA} \times \text{k}\Omega = \text{Volt}$

we apply KVL along a line.

L1: $2I_1 + 3I_2 - 5V = 0$


L1: $2I_1 + 3I_2 = 5 - 0$
sum of v_s along line
 \uparrow V of start node
 \uparrow V of end node

L2: $4I_3 - 10 - 3I_2 = 0$

$\Rightarrow 2I_1 + 3I_2 - 5 = 0$

L2: $-3I_2 + 4I_3 = 0 - (-10) = 10$
sum of v_s along line
 $\Rightarrow -3I_2 + 4I_3 - 10 = 0$


Example-2

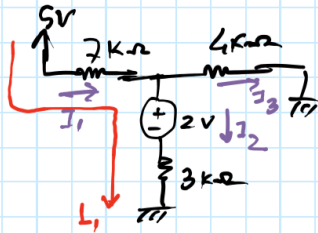

$$\underline{L_1}: \underbrace{7I_1 + 2 + 3I_2}_{\text{Sum of } v_i} = 5 - 0 \quad \begin{matrix} \nearrow \text{start} \\ \nwarrow \text{end} \end{matrix}$$

if current source along line,
we cannot use KVL.

Nodal analysis:

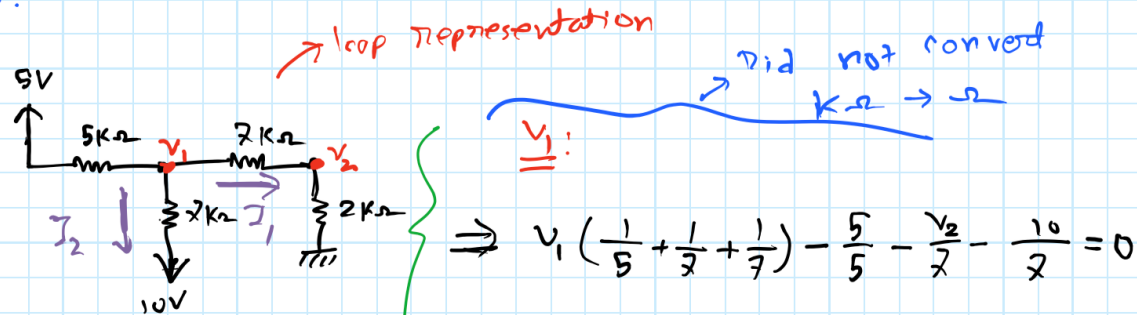

V1:

$$\Rightarrow V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right) - \frac{5}{5} - \frac{V_2}{2} - \frac{10}{2} = 0$$

V2:

$$V_2 \left(\frac{1}{2} + \frac{1}{2} \right) - \frac{0}{2} - \frac{V_1}{2} = 0$$

Solve $\Rightarrow V_1$ and V_2

Exactly same

$$I_1 = \frac{V_1 - V_2}{2}$$

$$I_2 = \frac{V_1 - 10}{2}$$

