


- ✓ Write down your student ID on the **top right corner of each of the pages**.
- ✓ Clearly write the solutions, along with the questions, on white paper with black ink (no need to use color pen, don't use pencils).
- ✓ Use **CamScanner**, or **Adobe Scan**, or **Microsoft Office Lens**, or any other software to scan the pages and make a **single PDF file**.
- ✓ After creating the PDF, make sure that (a) there are no pages missing, (b) all of the pages are legible, (c) your student ID on each page are visible.
- ✓ Please note, **collaboration ≠ copying**. You are allowed to discuss the questions and clear confusion you might have, but you have to write your solutions independently and be able to explain your answers during a random viva.
- ✓ **[Very Important]** Rename the PDF in the following format: "A5_StudentID_FullNameWithoutSpace.pdf". For example, if my student ID is 12345678 and my name is Shadman Shahid, the filename should be "A5_12345678_ShadmanShahid.pdf"
- ✓ **ONE OF THE QUESTIONS IS BONUS (I.E., ONE OF THE QUESTION'S MARKS WON'T BE COUNTED). I WON'T DISCLOSE WHICH ONE. THIS IS JUST SO THAT YOU WOULD NOT BE TENSED ABOUT THIS ASSIGNMENT. DO NOT WORRY ABOUT THE MARKS FOR NOW.**
- ✓ **Submission Link:** Section-15 - <https://forms.gle/6uLBBoCJUbtqITC39>, Section-21 - <https://forms.gle/Kqs1L95qR1hgt4tm6>

Question 1: CO1

10 Marks

- a) Consider an n-channel MOSFET with $k' = 0.2 \text{ mA/V}^2$ and $V_t = 0.7 \text{ V}$ and $\frac{W}{L} = 10$. Find the drain current for the following cases:

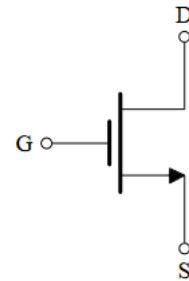
- (a) $v_{GS} = 5 \text{ V}$ and $v_{DS} = 1 \text{ V}$
 (b) $v_{GS} = 2 \text{ V}$ and $v_{DS} = 1.3 \text{ V}$
 (c) $v_{GS} = 5 \text{ V}$ and $v_{DS} = 0.2 \text{ V}$
 (d) $v_{GS} = v_{DS} = 5 \text{ V}$



- b) The table below lists 5 different cases labeled (a) to (e) for operating an NMOS transistor with V_t . In each case the voltages at the source, gate, and drain (relative to the circuit ground) are specified. You are required to complete the table entries. Note that if you encounter a case for which is negative, you should exchange the drain and source before solving the problem. You can do this because the MOSFET is a symmetric device.

Case	Voltage (V)						Region of operation
	V_s	V_g	V_d	V_{GS}	V_{OV}	V_{DS}	
a	+1.0	+1.0	+2.0				
b	+1.0	+2.5	+2.0				
c	+1.0	+2.5	+1.5				
d	+1.0	+1.5	0				
e	0	+2.5	1.0				

- c) The threshold voltage of each transistor in Figure P3.5 is $V_{TN} = 0.4 \text{ V}$. Determine the region of operation of the transistor in each circuit.

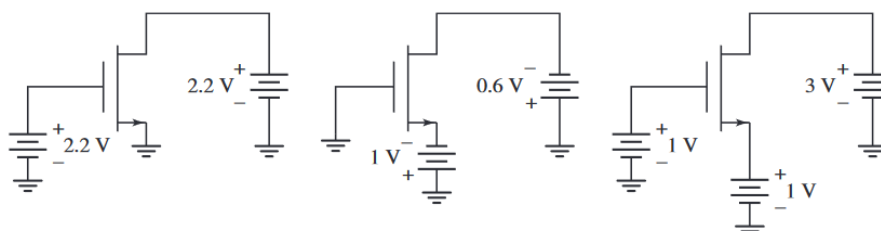


Question 2:

10 Marks

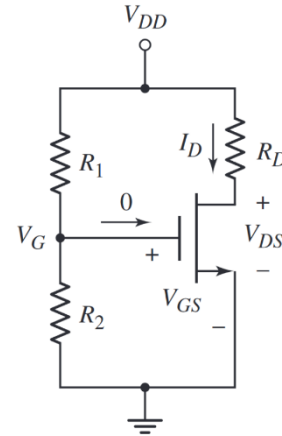- a. Calculate the **drain current** and **drain-to-source voltage** of a common source circuit with an **n-channel** enhancement-mode MOSFET. Find the power dissipated in the transistor. (Power dissipated in the transistor is $P_{NMOS} = I_D \cdot V_{DS}$)

[CO2] 4

For the circuit shown in, assume that $R_1 = 30 \text{ k}\Omega$, $R_2 = R_D = 20 \text{ k}\Omega$, $V_{DD} = 5 \text{ V}$, $V_{TN} = 1 \text{ V}$, and $k_n = 0.1 \text{ mA/V}^2$



- b. Calculate the **drain current** and **drain-to-source voltage** of a common source circuit with an **p-channel** enhancement-mode MOSFET. Find the power dissipated in the transistor. (Power dissipated in the transistor is $P_{PMOS} = I_D \cdot V_{SD}$)

[CO2] 6

For the circuit shown in, assume that $R_1 = R_2 = 50 \text{ k}\Omega$, $R_D = 7.5 \text{ k}\Omega$, $V_{DD} = 5 \text{ V}$, $V_{TP} = -0.8 \text{ V}$, and $k_p = 0.2 \text{ mA/V}^2$

****PS:** For PMOS the current equations are:


PMOS is **NOT** in Cut-off when $V_{GS} < V_{TP}$ or $V_{SG} > |V_{TP}|$.

- i. **Triode mode** ($V_{DS} < V_{GS} - V_{TP}$ or $V_{SD} > V_{SG} + V_{TP}$)

$$I_D = k_p \left(V_{SG} + V_{TP} - \frac{1}{2} V_{SD} \right) V_{SD}$$

- ii. **Saturation mode** ($V_{DS} > V_{GS} - V_{TP}$ or $V_{SD} < V_{SG} + V_{TP}$)

$$I_D = \frac{k_p}{2} (V_{SG} + V_{TP})^2$$

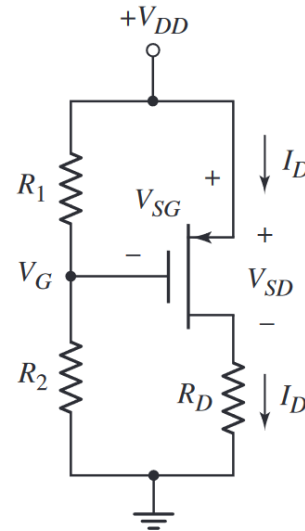


Question 3:

20 Marks

- a) Find the W/L sizing of the MOSFET when $R_D = 10 \text{ k}\Omega$, $I_Q = 250 \text{ }\mu\text{A}$, and $V_D = 2.5 \text{ V}$. Assume that the MOSFET has a threshold voltage of $V_{TN} = 0.8 \text{ V}$ and a transconductance of $k_n = 80 \text{ }\mu\text{A/V}^2$


[CO3] 5

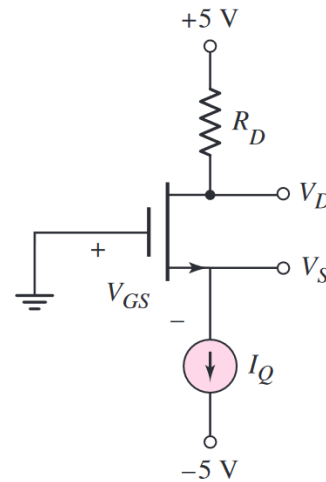

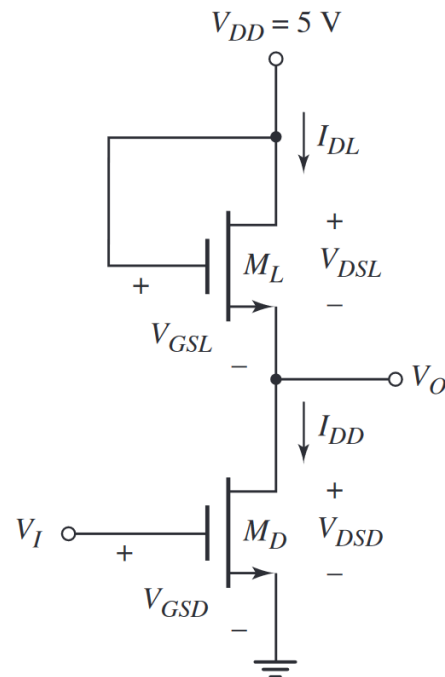- b) Determine the dc transistor currents and voltages in the given circuit. (Determine V_O , I_{DL} and I_{DD} for $V_I = 5 \text{ V}$)


[CO3] 5

For the transistors, $V_{TNL} = V_{TND} = 1 \text{ V}$, $k_{nD} = 50 \text{ }\mu\text{A/V}^2$, $k_{nL} = 10 \text{ }\mu\text{A/V}^2$, $V_{DD} = 5 \text{ V}$, (The subscript D applies to the lower transistor and the subscript L applies to the upper transistor.)



- c) The transistor in the circuit in Figure P3.51 is used to turn the LED on and off. The transistor parameters are $V_{TN} = 0.6 \text{ V}$, $k'_n = 80 \text{ }\mu\text{A/V}^2$, and $\lambda = 0$. The diode cut-in voltage is $V_\gamma = 1.6 \text{ V}$. Design R_D and the transistor width-to-length ratio such that $I_D = 12 \text{ mA}$ for $V_I = 5 \text{ V}$ and $V_{DS} = 0.15 \text{ V}$.


[CO3] 7

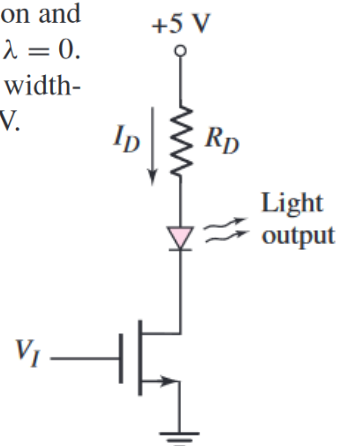

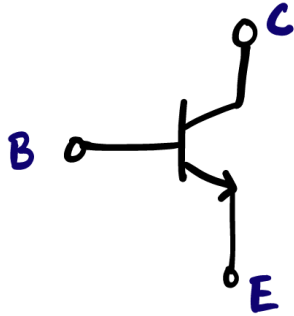Question 4: CO1

8 Marks

The terminal voltages of various npn transistors are measured during operation in their respective circuits with the following results. In this table, where the entries are in volts, 0 indicates the reference voltage. For each case, identify the mode of operation of the transistor.




Case	E	B	C	Mode
1.	0	0.7	0.7	
2.	0	0.8	0.1	
3.	-0.7	0	0.7	
4.	-2.7	-2	0	

Question 5



10 Marks

- a. Design the circuit, i.e., determine the Resistor values, to establish $I_C = 0.1 \text{ mA}$ and $V_C = 0.5 \text{ V}$. The transistor exhibits $v_{BE} = 0.8 \text{ V}$ at $i_c = 1 \text{ mA}$, and $\beta = 100$.

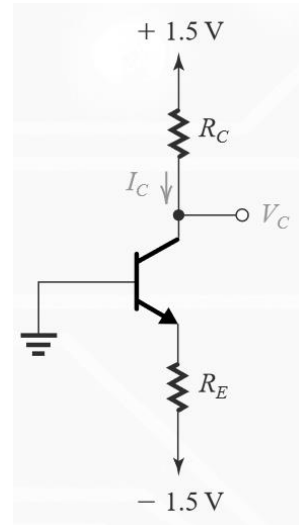

[CO3] 4



- b. For each of the given circuits, find the emitter, base and collector voltages and currents. Use $\beta = 50$ and assume $|V_{BE}| = 0.8 \text{ V}$.

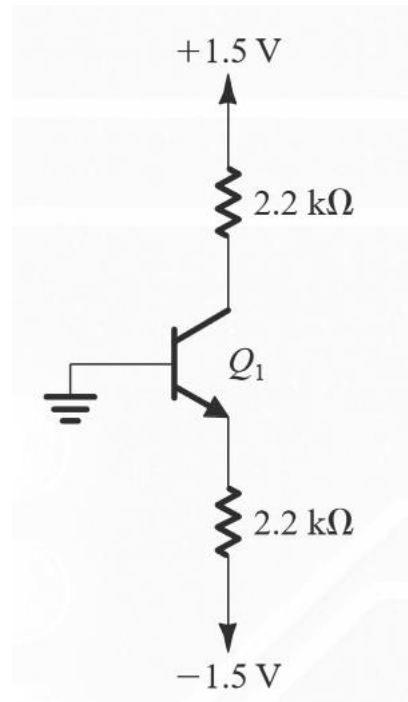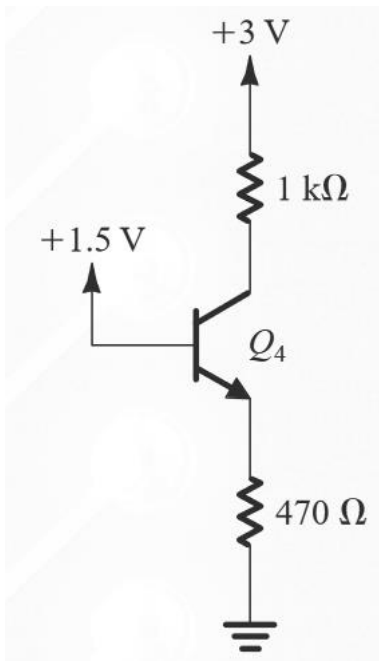

Question 6


10 Marks

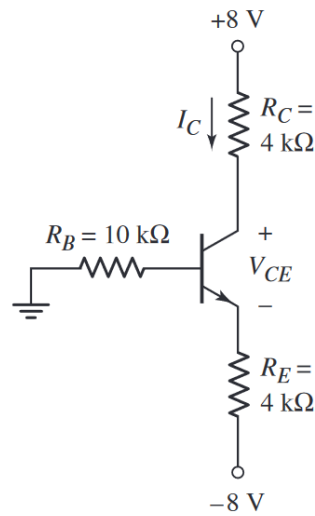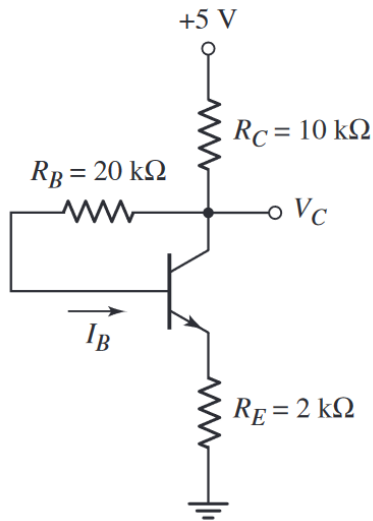- a. For the transistors in the adjacent figure, $\beta = 75$. Find the labelled voltages and currents [CO2] 6
(Assume $V_{BE_0} = 0.7 \text{ V}$, $V_{CE(\text{sat})} = 0.2 \text{ V}$)



- b. In the circuit shown in adjacent figure, the values of measured parameters are shown. Determine β , α , and the other labeled currents and voltages.


[CO2] 4

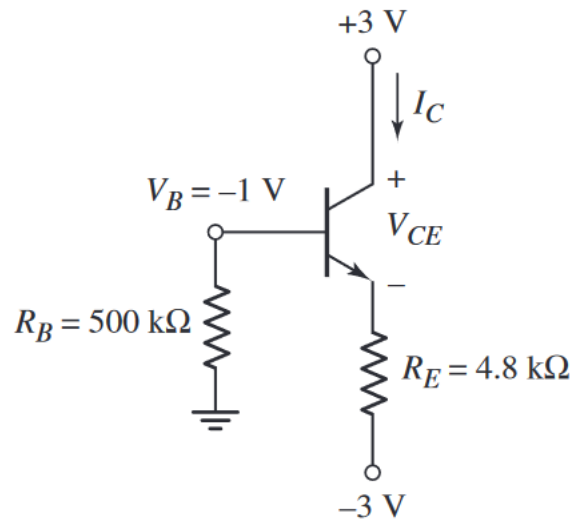

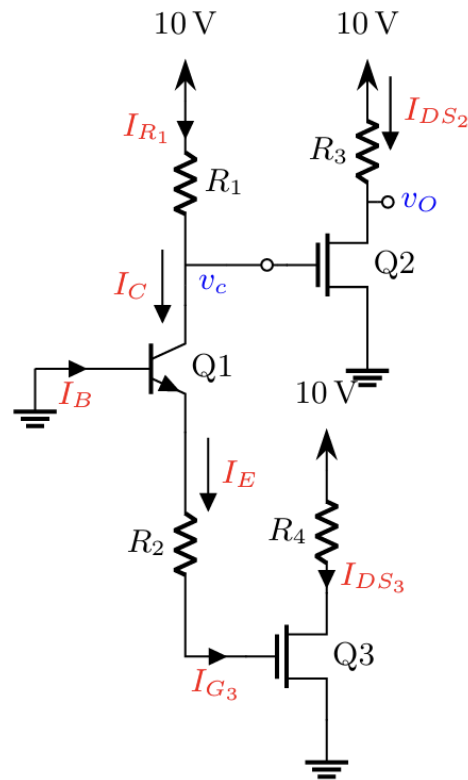Question 7: CO2

12 Marks

For the following circuit, $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$, $R_3 = 3\text{k}\Omega$, $R_4 = 4\text{k}\Omega$



For BJT

$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(\text{Active})} = 0.7\text{ V}$$

$$v_{BE(\text{Saturation})} = 0.8\text{ V}$$

$$v_{CE(\text{Saturation})} = 0.2\text{ V}$$

for MOSFETs

$$V_T = 1\text{ V}$$

$$k = 5\text{ mA/V}^2$$

- (a) [5 marks] **Analyze** the circuit to **determine** the values of I_C , I_B , I_E , v_c .
- (b) [5 marks] **Analyze** the circuit to determine the value of I_{DS_2} , v_O .