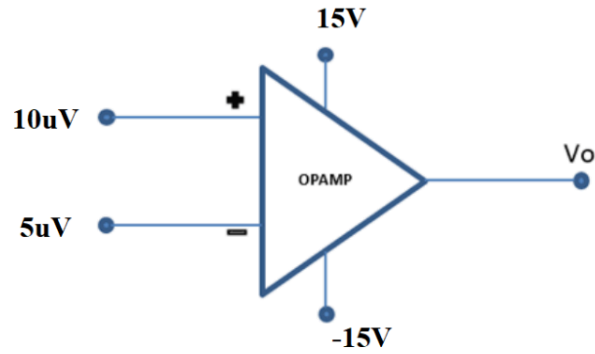




## Op-Amp

1. Observe the following circuit.




Calculate the value of  $V_o$ . Repeat the problem with  $V_+ = 1 \text{ mV}$  and  $V_- = 0.2 \text{ mV}$ . Consider  $A = 2105$ .

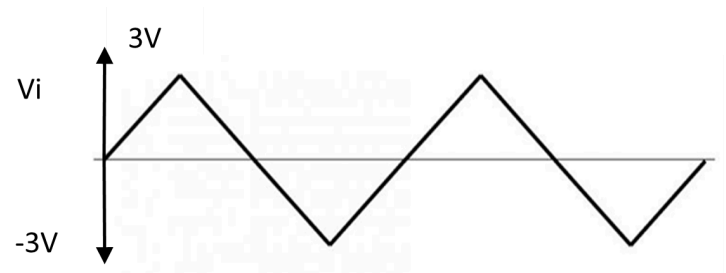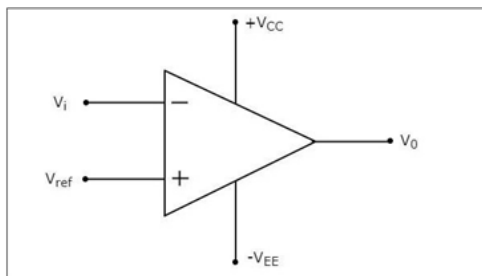2. Draw output  $V_o$  for the following op-amp circuit.



$V_{CC} = 15V = -V_{EE}$ ,  $V_{ref} = 1.5V$ ,  $V_i$  is a 6V p-p triangular signal as shown below.

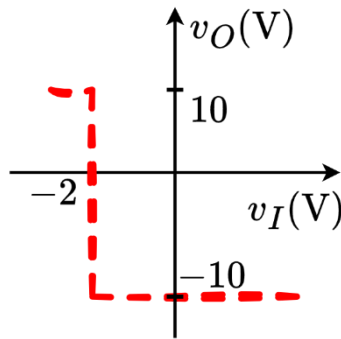3. Design a circuit using **op-amp** that has the voltage transfer characteristics as shown in the figure below.  $v_o(V)$  is the **output voltage** and  $v_i(V)$  is the **input voltage**.



5.

A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure in a water tank. The valve operates on **ACTIVE LOW** logic. (i.e., the valve is OPENED when given a LOW voltage of 1 V, but remains CLOSED when provided a HIGH voltage of 6 V.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.

At 0.5 atm pressure	At 1 atm pressure	At 1.5 atm pressure
$v_{0.5 \text{ atm}} = 0.5 \text{ V}$	$v_{1 \text{ atm}} = 3 \text{ V}$	$v_{1.5 \text{ atm}} = 5.5 \text{ V}$

The pressure in the water tank can be measured by the formula  $P = h\rho g$ , where  $P$ , (in **Pascals (Pa)** unit) is the water pressure,  $h$  is the height of water in the tank (in *metres*),  $\rho (= 1000 \text{ kgm}^{-3})$  is the density of water and  $g$  is the acceleration due to gravity (in  $\text{ms}^{-2}$ ).

[1 atm = 101325 Pa]

- Design a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds **10 m**.
- Draw the voltage transfer characteristics (VTC) of the designed Op-Amp.

6.

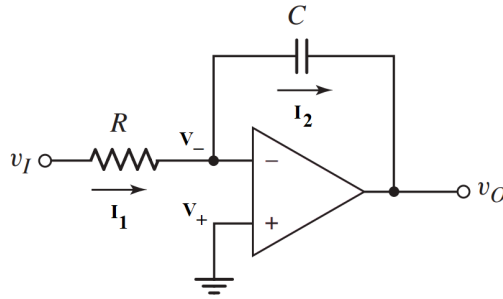


Figure 1 (a)

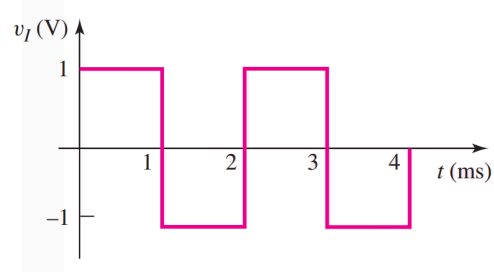


Figure 1 (b)

- (a) **Analyze** the circuit drawn in Fig. 1(a) and **determine** the voltage values at the inverting and non-inverting nodes ( $V_-$  and  $V_+$ ). [0.5+0.5]
- (b) **Identify** the relation between  $I_1$  and  $I_2$ . [1]
- (c) **Analyze** the circuit to derive the expression of output voltage  $V_O$ . You have to **show** all the steps. [3]
- (d) Now consider the input wave  $v_I$  given in Fig. 1(b). For circuit parameters  $R = 10 \text{ k}\Omega$  and  $C = 0.1 \mu\text{F}$ , **determine** the output voltage at  $t = 1 \text{ ms}$ . [1]
- (e) **Design** a circuit using Op-Amps to implement the following expression: [4]  

$$f = \frac{1}{4}x + 7y - \frac{d}{dt}z$$

7.


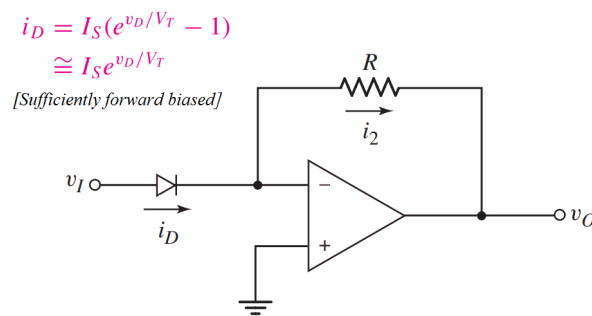


Figure 1

- (a) **Analyze** the circuit drawn in Fig. 1 and **determine** the voltage values at the inverting and non-inverting nodes ( $V_-$  and  $V_+$ ). [0.5+0.5]
- (b) **Identify** and briefly explain the relation between  $i_2$  and  $i_D$ . [1.5]
- (c) **Analyze** the circuit to derive the expression of output voltage  $V_O$ . You have to **show** all the steps. [3.5]
- (d) **Design** a circuit using Op-Amps to implement the following expression: [4]

8.

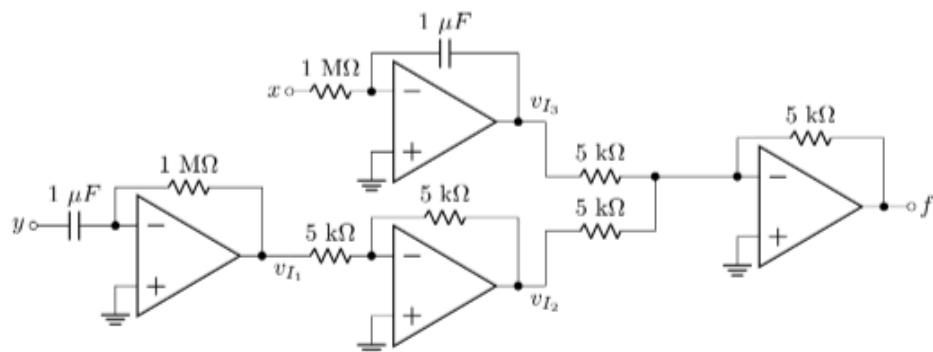

- (a) **Analyze** the circuit above to find an expression of  $f$  in terms of inputs  $x$  and  $y$ . Also, **determine** the intermediate outputs  $v_{I1}$ ,  $v_{I2}$ , and  $v_{I3}$  as denoted in the circuit. [4]
- (b) Draw the circuit of an **inverting amplifier** and **design** it in such a way that the voltage gain,  $k = -4$ . (*i.e.*, find the values of  $R_1$  and  $R_2$ ). [3]
- (c) **Show** the input and output waveforms of the inverting amplifier of part (b) assuming a sinusoidal input of 0.5 V amplitude. **Calculate** the amplitude of the output. [2]
- (d) Consider the inverting amplifier of part (b) again. Assume the input voltage can provide a maximum current of  $0.5 \mu\text{A}$ . **Determine** the design changes required, if any, for the circuit to work. [1]

9.


- (a) **Design** a circuit using **Op-Amp comparator** to automatically turn ON (or OFF) the street lights. For this, you have a lux sensor installed on top of the street lights (facing above) that outputs a voltage proportional to amount of natural light, as listed below:

$v_{\text{night}}, 0 \text{ lux} = 1 \text{ V}$	$v_{\text{dusk}}, 20 \text{ lux} = 2 \text{ V}$	$v_{\text{dawn}}, 80 \text{ lux} = 3 \text{ V}$
---	---	---


The lights require 20 V and should be ON if the amount of light goes **below** 20 lux (at dusk). [3]

- (b) **Design** a circuit using Op-Amp to implement the expression:  $f = -3\frac{dx}{dt} + 2\exp y + 4z$  [4]

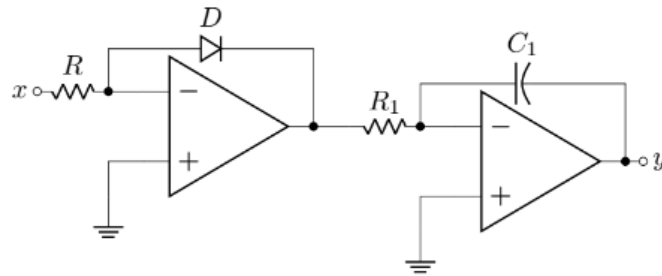- (c) **Analyze** the circuit below to find  $y$  as a function of  $x$ . For the diode,  $I_S R = 1$  and  $V_T = 1$ . [3]



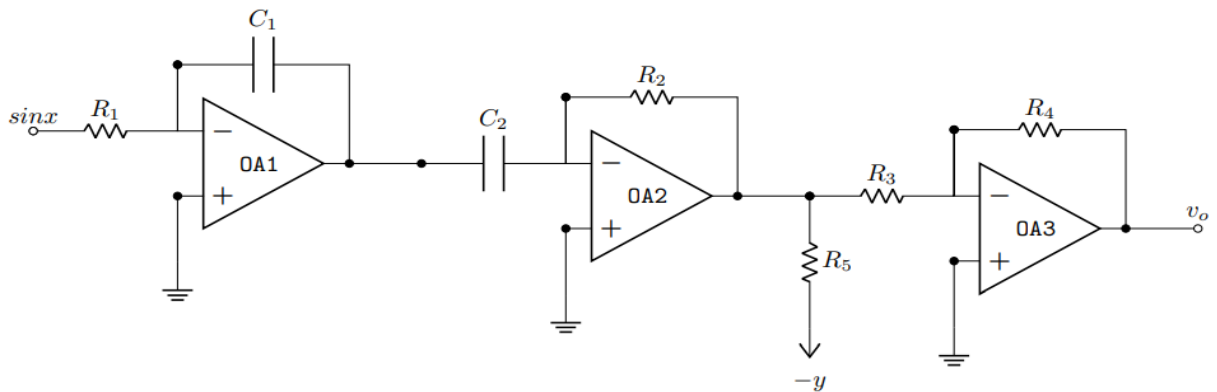
10. **Deduce** the expression for output,  $V_o$  from the circuit above



11. Design a circuit using op-amps to implement  $y=7x$  by an


- (a) Inverting amplifier
- (b) Non-inverting amplifier

12.

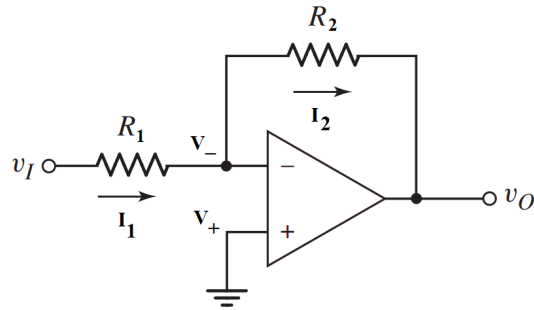


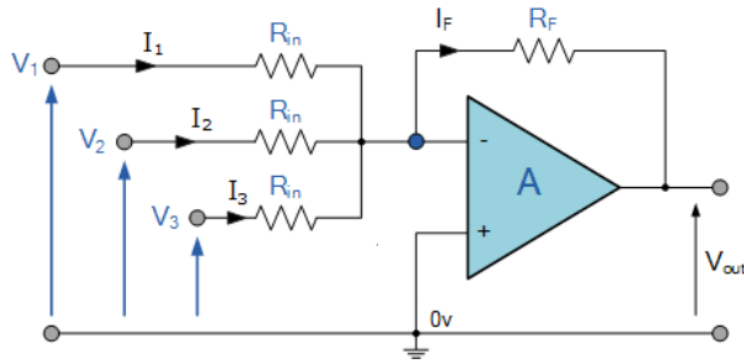- (a) **Design** an inverting amplifier (i.e., find the values of  $R_1$  and  $R_2$  of the circuit shown in the Figure above) in such a way that the voltage gain is  $-5$ .
- (b) Consider the circuit you drew in (a) again. Assume the input  $v_i = 0.1 \sin \omega t$  (V) has a maximum current rating of  $5 \mu\text{A}$ . What design changes, if any, are required for this input, if the voltage gain remains the same?
- (c) **Draw** the input and output waveforms of the circuit you designed in (c).


- **Analyze** the following circuit and derive the expression for the output voltage ( $V_{\text{out}}$ ) in terms of the inputs. If  $V_1 = 1$  V,  $V_2 = 2$  V, and  $V_3 = 1.5$  V, and all the resistors have equal values, calculate  $V_{\text{out}}$ .



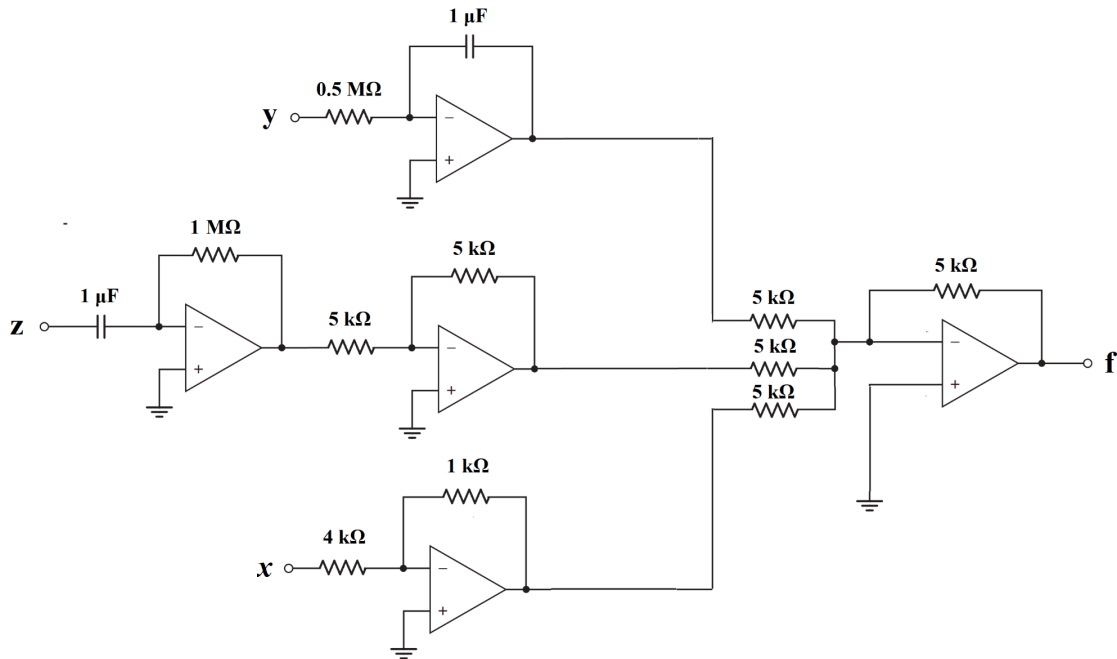13. **Analyze** the following circuit to find an expression of  $f$  in terms of  $x$ ,  $y$ , and  $z$ .



14. Consider the Ideal Op-Amp and find the value of  $V_o$ .

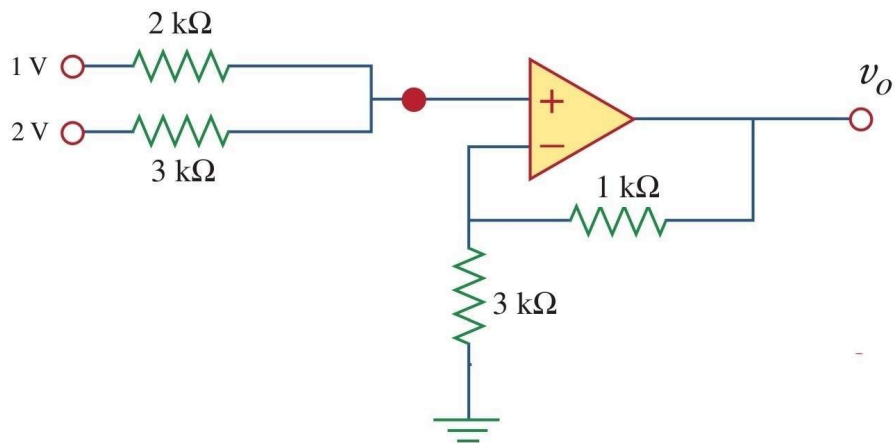

**Figure 3(b)**

- (a) **Analyze** the circuit in Fig 3(a) to find an expression of  $f$  in terms of  $x$ ,  $y$ , and  $z$ .  
[4]
- (b) **Design** an inverting amplifier (i.e., find the values of  $R_1$  and  $R_2$  of the circuit shown in Fig. 3(b)) in such a way that the voltage gain is **-4**.  
[3]
- (c) **Draw** the input and output waveforms of the circuit you designed in (b).  
[2]
- (d) Consider the circuit in Figure 3(b) again. Assume the input  $v_i = 0.1 \sin \omega t$  (V) has a maximum current rating of  $4 \mu\text{A}$ . What design changes, if any, is required for this input, if the voltage gain remains the same?