

Name:	ID:
-------	-----



Brac University

Set - B

Semester: Fall 2023

Course No: CSE251

Course Title: Electronic Devices and Circuits

Sections: 1 to 24

Final Examination


Full Marks: 30

Time: 1.5 hours

Date: Dec 15, 2023

Answer any 3 questions. All the questions carry equal marks.


Question 1

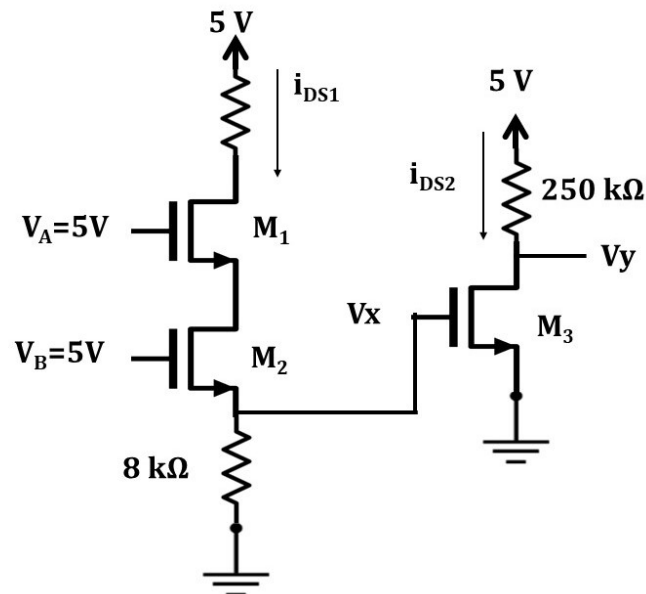

For the following circuit with MOSFETs, assume that $V_T = 1\text{ V}$, $k_n' = 20\text{ }\mu\text{A/V}^2$ and the aspect ratio W/L is 1 for all the MOSFETs.

- If the gate voltage to **M3** MOSFET, $V_x = 0.492\text{ V}$, and MOSFET **M2** is in triode mode, find the voltage V_1 . Verify the modes for both **M1** and **M2** [3]
- Find V_y . [2]
- If $W/L=4$, then $V_1 = 2.04\text{ V}$. Find V_x for this case. [2]
- Can you explain, whether there will be any changes in the output voltage at V_y for $W/L = 4$ from that in 'b'. Also, comment on whether a larger or smaller value of W/L ratio is preferred in this case. [2+1]

Question 2

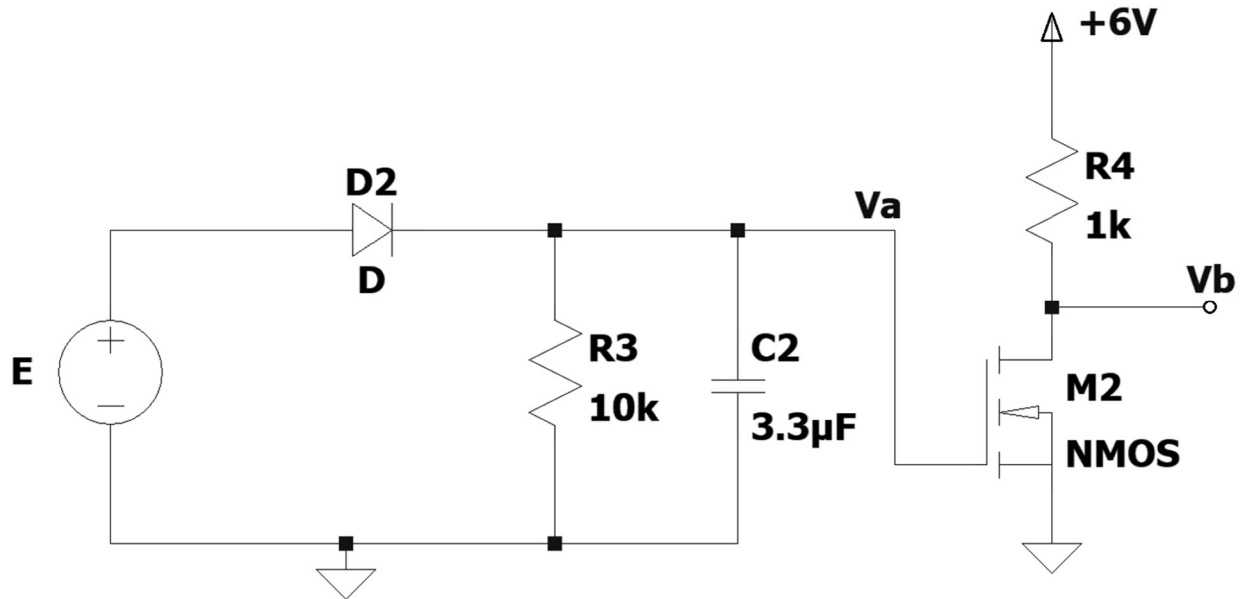


The Half-wave rectifier circuit has been cascaded with an inverter. You are given the following information about the circuit: [For HW: $V_o = V_{dc} \pm V_{ripple}/2$]

$E = 6 \sin(400\pi t) V$	$K_n = 2 mA/V^2$	$V_T = 1 V$	$V_{Do} = 0.7 V$
--------------------------	------------------	-------------	------------------

- Determine** the peak-to-peak ripple value of the half-wave rectifier output, V_a . What is the lowest value of V_a ? [3+1]
- At the lowest value of V_a , **determine** the output V_b of the inverter. [4]
- Now disconnect the capacitor. In this case, **find out** the voltage V_b for the lowest value of V_a . [2]
- [BONUS]** Draw an approximate plot of V_b without the capacitor connection. [2]



Question 3

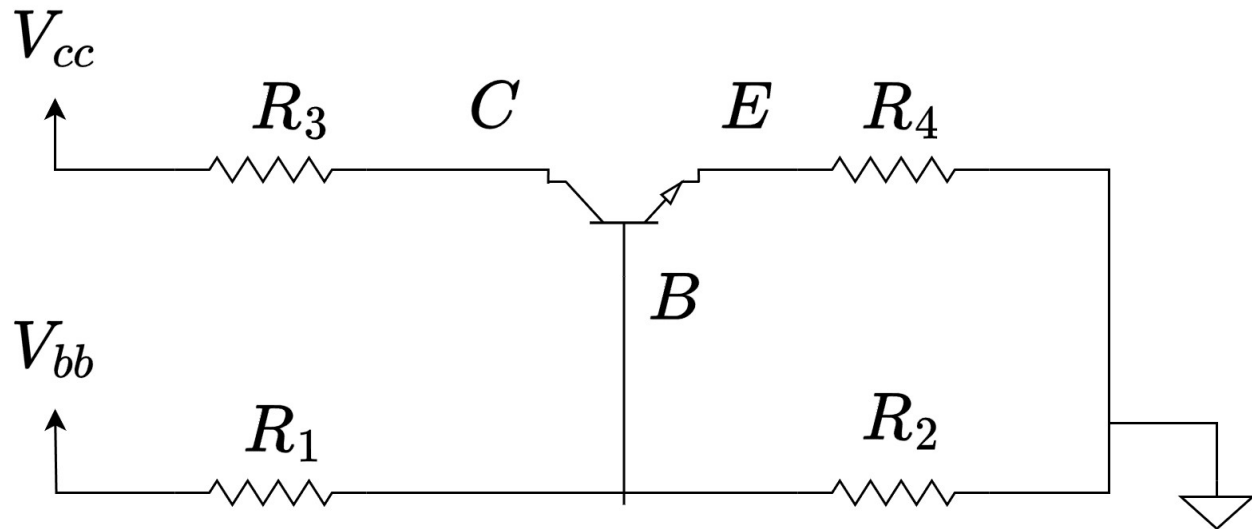

In the circuit above, $V_{bb} = 5\text{ V}$, $V_{cc} = 15\text{ V}$, $R_1 = 40\text{ k}\Omega$, $R_2 = 60\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$ and $R_4 = 1\text{ k}\Omega$. Also, the current gain, $I_C/I_B = 100$.

- Draw** the equivalent circuit of BJT during saturation and active modes. [1]
- Analyze** the following circuit to **calculate** the values of I_b , I_C , I_E , V_{CE} and V_C using the method of assumed states. You must validate your assumptions. [Hint: try to find the Thevenin equivalent of the bottom circuit from the B terminal and ground] [6]
- Assume, V_{bb} is changed **from 5V to 5.1V**, what happens to the outputs of the circuits? Calculate I_b , I_C , I_E , V_{CE} and V_C again. Now for a 0.1V increase in input V_{bb} , what is the change of I_C ? Use $\Delta I_C = I_{C(NEW)} - I_{C(OLD)}$ [3]
- [BONUS]** Explain any use case of the differences in voltage increase between input and output. What could the use case be to such a phenomenon? [1]

Question 4

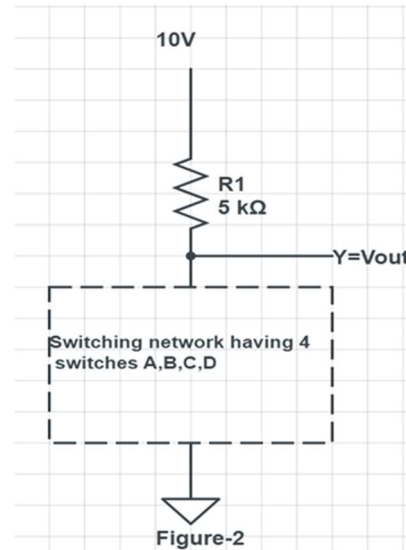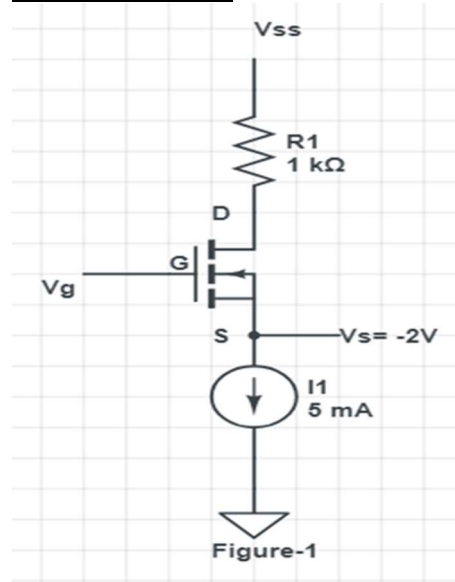


- For the MOSFET in Figure-1, $V_T = 1\text{ V}$ and $k_n' = 2\text{ mA/V}^2$. Assume that the MOSFET is in **Saturation mode**. Determine the gate voltage, V_g and the minimum supply voltage, V_{ss} to operate the device in this condition. [Hint: $V_{OV} = V_{DS}$] [3+2]
- In Figure-2, the MOSFET switching network turns ON the following conditions MUST be fulfilled -
 - 'A' MUST be ON
 - 'B' and 'C' MUST be ON or 'D' MUST be ON

Deduce the logic function, F, using Boolean variables A, B, C, and D to implement these conditions. [2]

- Assume, only A and D switches are ON in the switching network of Figure-2. **Find out** the output voltage, V_{out} . Let, $R_{ON} = 0.1\text{ k}\Omega$ and use the SR model. [3]
- [BONUS]** In Figure-2, assume the input on a NOT gate is connected to V_{out} . **Explain** mathematically whether it will be possible to turn OFF the NOT gate when V_{out} is LOW. Assume, $V_T = 0.5\text{ V}$, $V_{out} = V_{out(LOW)}$ of question(b). [2]

Question 5

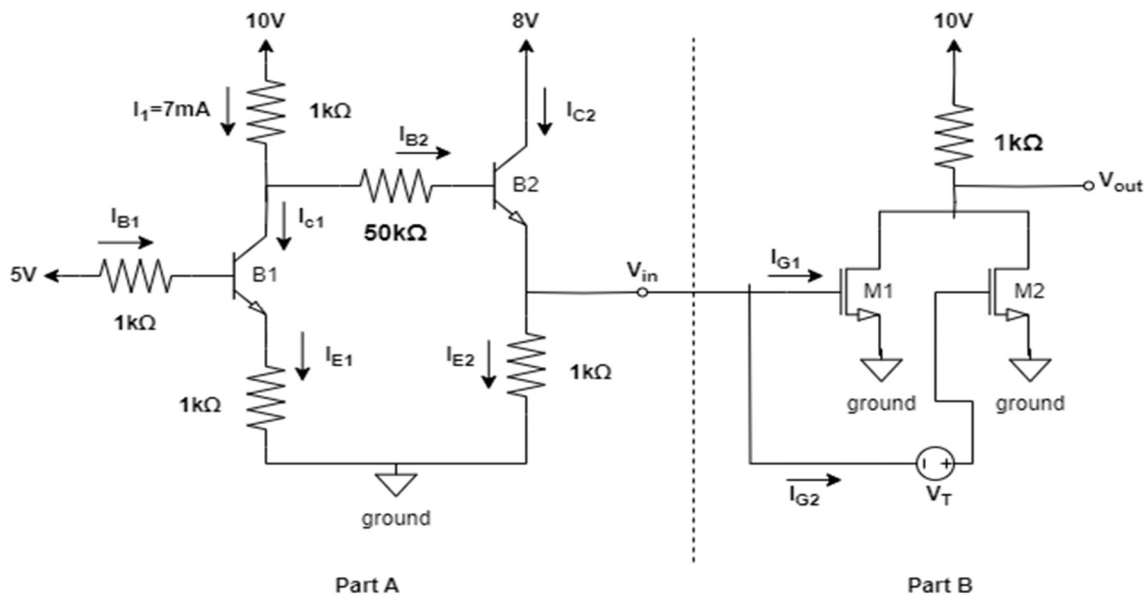

In the circuit above, the BJTs have the following specification: $\beta=100$, Forward Active Region: $V_{BE} = 0.7\text{ V}$, $I_C = \beta I_B$, Saturation Region: $V_{BE} = 0.8\text{ V}$, $V_{CE} = 0.2\text{ V}$, or the MOSFETs: $V_T =$ Threshold Voltage of M1 and M2.

- Determine i_{g1} and i_{g2} . [1]
- The SR model of MOSFET is more efficient than the S model- Justify this statement. [1]
- Assume, B1 and B2 are in the **Saturation region**. Calculate i_{c2} . [2]
- Assume, B1 is in the **Forward Active region**. Calculate V_{in} . [4]
- Draw the VTC of Part- B assuming, $V_T = 8\text{ V}$. [Use S model of MOSFETs]. [2]

Equations for MOSFET

$$I_D = 0, \text{ if } V_{GS} < V_T$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right], \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2, \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$