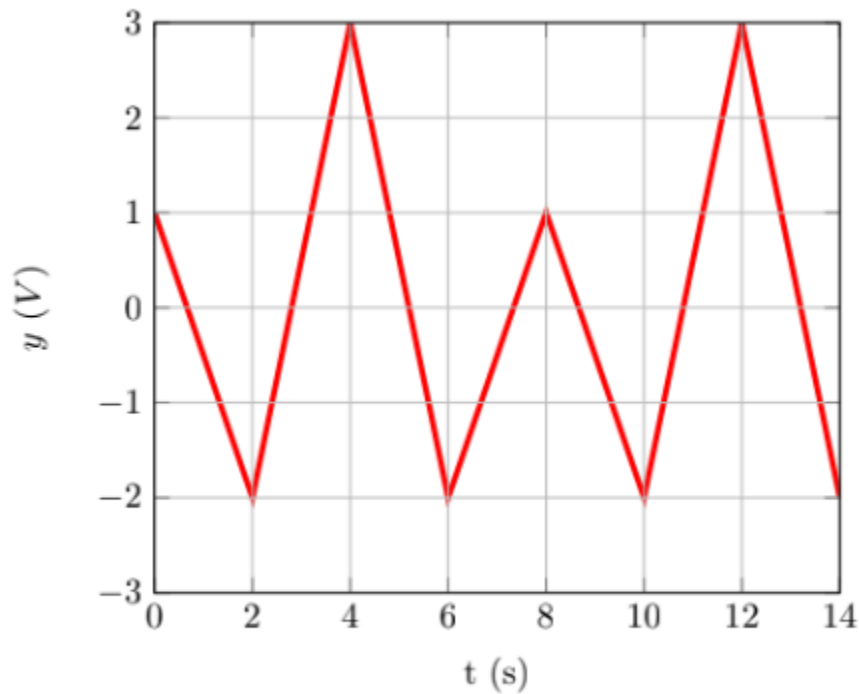


## Assignment-2

### Rectifiers

1. The input of a full-wave rectifier is a cosine voltage with peak  $V_M = 5$  V and frequency 60 Hz, and output load resistance is  $R = 2$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
  - (a) Briefly explain the purpose of a rectifier and describe its operation. [1]
  - (b) Show the input and output waveforms. [2]
  - (c) Calculate the DC value of the output voltage. [1]Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage  **$V_{out} = V_{DC} \pm 0.2$  V**
  - (d) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor. [2]
  - (e) Calculate the average of the output voltage  $V_{DC}$  after connecting the capacitor. Compare this with the DC value determined in 'c' and comment on the difference between these two. [2]
2. The input of a **Half-wave rectifier** is a sine voltage with peak  $V_M = 10$  V and frequency 55 Hz, and output load resistance is  $R = 2.5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.4$  V.
  - (a) Calculate the DC value of the output voltage. [1]Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage  **$V_{out} = V_{DC} \pm 0.3$  V**.
  - (b) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor. [2]
  - (c) Draw the **Voltage Transfer Characteristic (VTC) curve** [2]
3. The input of a full-wave rectifier is expressed by,  $V_s(t) = 7\sin(400\pi t)$ , and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.3$  V.
  - (a) Calculate the input and output wave frequency. [2]
  - (b) Show the input and output waveforms.Now after connecting a capacitor,  $C = 100$   $\mu$ F in parallel with the load.
  - (c) Calculate the peak-to-peak ripple voltage,
  - (d) How can you provide better filtering for the output waves?
  - (e) What is the frequency of the Ripple voltage?
4. The input of a **Half-wave rectifier** is a **Square** wave voltage with peak  $V_M = 15$  V and frequency 0.5 Hz, and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
  - i. Show the input and output waveforms. [4]
  - ii. Draw the VTC curve [2]
5. The input of a **full-wave rectifier** is a **Square** wave voltage with peak  $V_M = 15$  V and frequency 0.5 Hz, and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
  - i. Show the input and output waveforms. [4]

ii. Draw the VTC curve [2]




(b) Input of the FW rectifier

6.

**Part 2:** A voltage waveform  $V_i = 15 \sin(2000\pi t)$  V is fed into a Half-wave rectifier with a load resistance  $R = 5 \text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D_0} = 0.7 \text{ V}$ .


- (a) **Illustrate** the input and output waveforms in separate graphs. Label the graph and **indicate** the voltage levels properly. [2]
- (b) **Calculate** the DC/Average value of the output. [1]
- (c) A capacitor is now added to reduce the fluctuation of the output voltage, which makes the peak to peak ripple voltage 4% of the maximum output voltage  $V_P$ . **Deduce** is the value of the capacitor from the given data.[2]
- (d) The input of a Full-wave rectifier is shown in Figure 1(b) above and output load resistance is  $R = 10 \text{ k}\Omega$ . Germanium diodes are used in this circuit for which the forward drop is  $V_{D_0} = 0.3 \text{ V}$ . **Show** the input and output waveforms [1]

7.

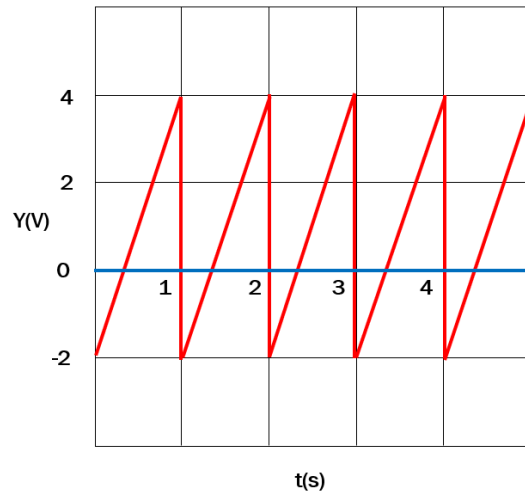


The input of a **Half-wave rectifier** is exhibited in the Figure above and output load resistance is  $R = 5 \text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7 \text{ V}$ .

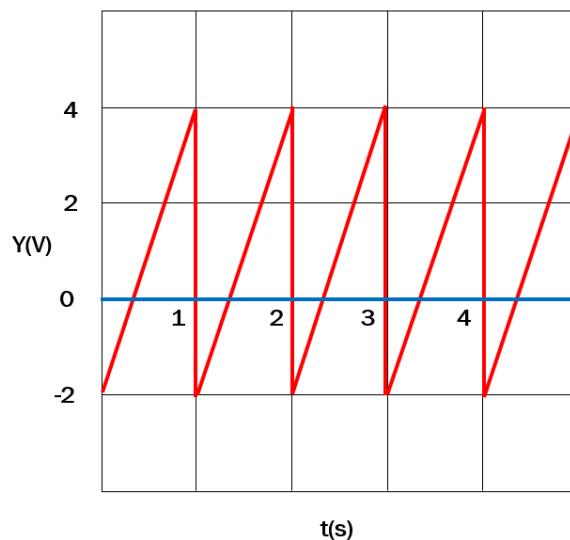- i. Show the input and output waveforms. [3]
- ii. Draw the VTC curve [2]
- iii. Calculate input and output frequency [3]



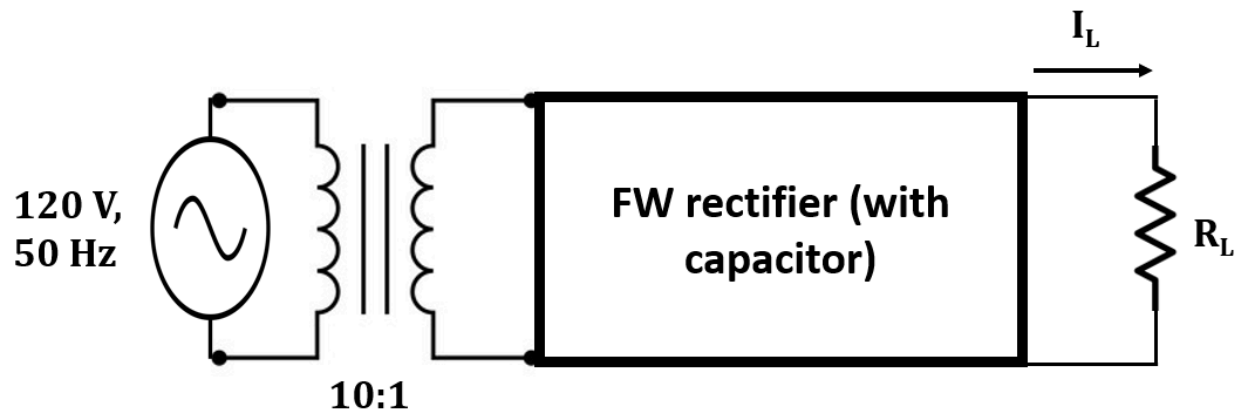
8. The input of a **full-wave rectifier** is exhibited in the Figure above and output load resistance is  $R = 5 \text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7 \text{ V}$ .
  - i. Show the input and output waveforms. [3]
  - ii. Draw the VTC curve [2]
  - iii. Calculate input and output frequency [3]
9. A full-wave rectifier is designed to deliver a maximum current  $I_L = 120 \text{ mA}$  to the load. The rectifier produces an output with a ripple of 5% of the peak output voltage. An input line voltage of 120 V (peak), 50 Hz is available. A 10:1 step-down transformer is used to transform the supply voltage to 12 V (peak).



- Draw** the Voltage Transfer Characteristics of the full-wave rectifier. [2]
- Calculate** the peak output voltage. [1]
- Determine** the value of the Load Resistor to deliver a maximum load current of 120mA. [2]
- Deduce** the value of the Capacitor and the DC average value. [1]
- Assume the transformer is removed and the rectifier is directly connected to the AC power supply line. **Discuss** the state of the diodes. [ Hint: use the Peak Input Value of the rectifier input] [3]

## Hybrid Problems


1.

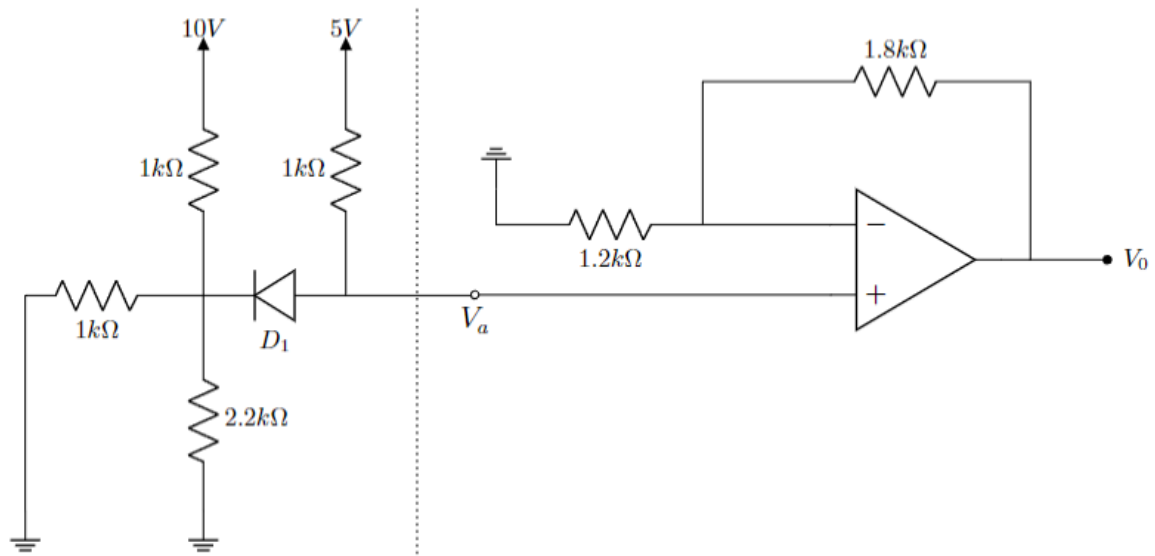

The saturation voltages of the Op-Amp are given as-  $V_{sat}^+ = +10V$  and  $V_{sat}^- = -10V$ . The forward voltage drop of the diode,  $V_D$  is 0.7V.

- Determine** the operating mode diode,  $D_1$ . Verify your assumption with necessary calculations.
- Calculate** the voltage at - (i) node 'Va', (ii) non-inverting terminal of the Op-Amp, (iii) inverting terminal of the Op-Amp.
- Find out the output voltage,  $V_o$  of the Op-Amp.

2.

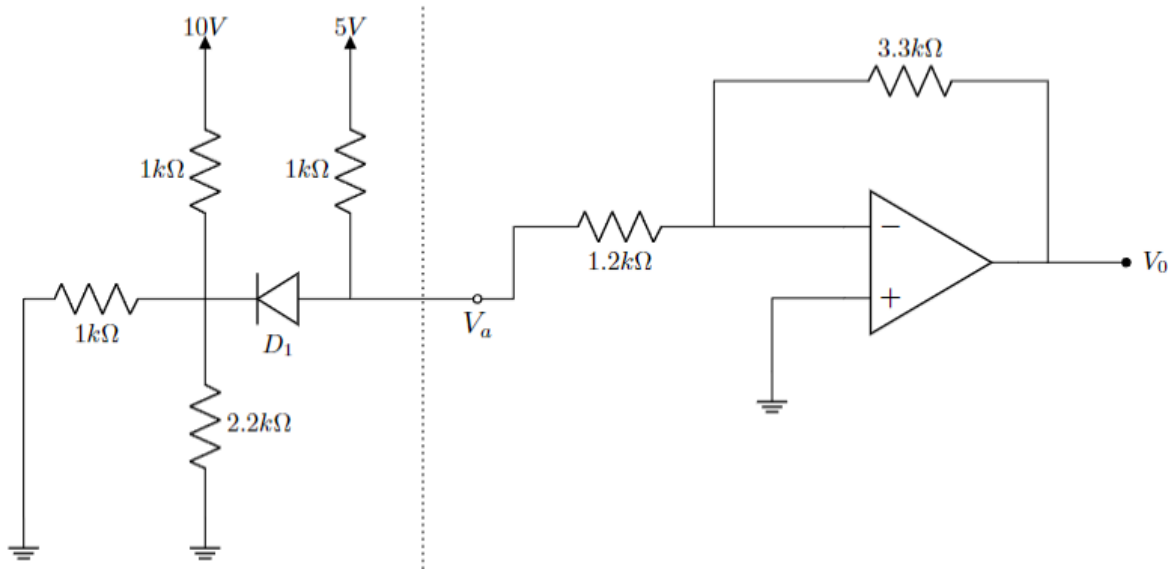


The saturation voltages of the Op-Amp are given as-  $V_{sat}^+ = +10V$  and  $V_{sat}^- = -10V$ . The forward voltage drop of the diode,  $V_D$  is  $0.7V$ .

- Determine** the operating mode diode,  $D_1$ . Verify your assumption with necessary calculations.
- Calculate** the voltage at - (i) node 'Va', (ii) non-inverting terminal of the Op-Amp, (iii) inverting terminal of the Op-Amp.
- Find out the output voltage,  $V_o$  of the Op-Amp.

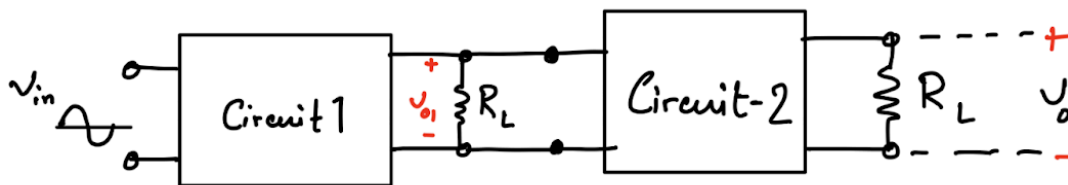3.

You are provided with the diagram below as a starting point for designing an AC to DC converter. Input voltage source is an sinusoidal voltage source ( $V_{in}$ ), with  $2V$  peak to peak voltage (i.e.  $1V$  amplitude) and the DC voltage is around  $10V$  (with ripple) at the output terminals ( $v_o$ ).



So, in order to solve this problem, you are provided with a single diode (with  $V_{D0} = 0.7V$ ), two resistors ( $R_1$  and  $R_2$ , excluding the load resistors  $R_L$ ) and an UA741 op-amp.

- Design **circuit-1** with the single diode and  $R_L = 10k\Omega$  ( $R_L$  is already provided in the diagram as output terminals of **circuit-1**) to get a rectified voltage and determine the DC value of the output voltage ( $v_{o1}$ ) of the circuit. [1+2]

- (b) Determine the ripple voltage of  $v_{o1}$ . [Ripple voltage is defined as the difference between the maximum and minimum value of a DC voltage.] [2]
- (c) What should be the value of a capacitor used at the output end of **circuit-1** with  $R_L$  to reduce the ripple voltage of  $v_{o1}$  to 1 V. How should the capacitor be connected with  $R_L$  in the diagram? [4+1]
- (d) Design an amplifier using an operational amplifier as **circuit-2** to increase the DC voltage level of the output voltage of the circuit designed in (c) to 10 V. Find the ripple voltage of the amplified voltage signal. [4+1]