
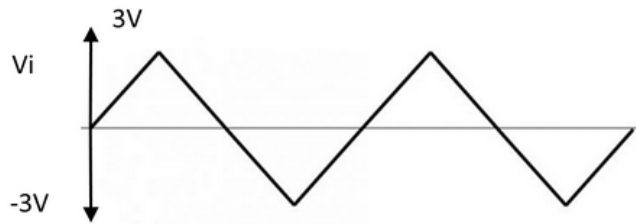


Question: 01: [CO3]

(5 marks)

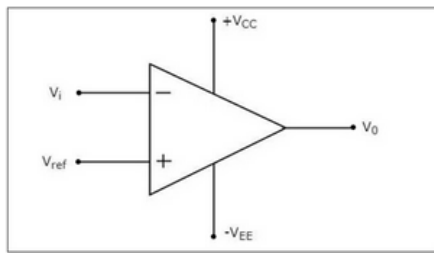

$V_{CC} = 15V = -V_{EE}$, $V_{ref} = 1.5V$, V_i is a 6V p-p triangular signal as shown below.

Question: 02: [CO3]

(5+5 marks)

A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure in a water tank. The valve operates on **ACTIVE LOW** logic. (i.e., the valve is OPENED when given a LOW voltage of 1 V, but remains CLOSED when provided a HIGH voltage of 6 V.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.

| At 0.5 atm pressure | At 1 atm pressure | At 1.5 atm pressure |
|-------------------------------|---------------------------|-------------------------------|
| $v_{0.5 \text{ atm}} = 0.5 V$ | $v_{1 \text{ atm}} = 3 V$ | $v_{1.5 \text{ atm}} = 5.5 V$ |

The pressure in the water tank can be measured by the formula $P = h\rho g$, where P , (in **Pascals (Pa)** unit) is the water pressure, h is the height of water in the tank (in *metres*), $\rho (= 1000 \text{ kgm}^{-3})$ is the density of water and g is the acceleration due to gravity (in ms^{-2}).

[1 atm = 101325 Pa]

- Design a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds 10 m.
- Draw the voltage transfer characteristics (VTC) of the designed Op-Amp.

Question: 03: [CO3]

(10 marks)

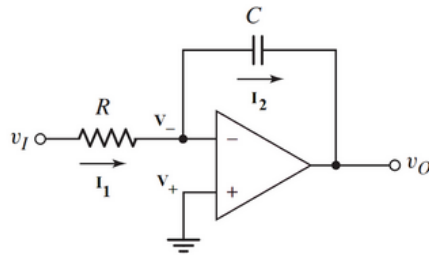


Figure 1 (a)

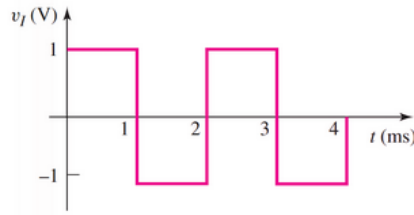



Figure 1 (b)

- Analyze** the circuit drawn in Fig. 1(a) and **determine** the voltage values at the inverting and non-inverting nodes (V_- and V_+). [0.5+0.5] [1]
- Identify** the relation between I_1 and I_2 . [1]
- Analyze** the circuit to derive the expression of output voltage V_O . You have to **show** all the steps. [3]
- Now consider the input wave v_1 given in Fig. 1(b). For circuit parameters $R = 10 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$, **determine** the output voltage at $t = 1 \text{ ms}$. [1]
- Design** a circuit using Op-Amps to implement the following expression: [4]

$$f = \frac{1}{4}x + 7y - \frac{d}{dt}z$$

Question: 04: [CO3]

(10 marks)

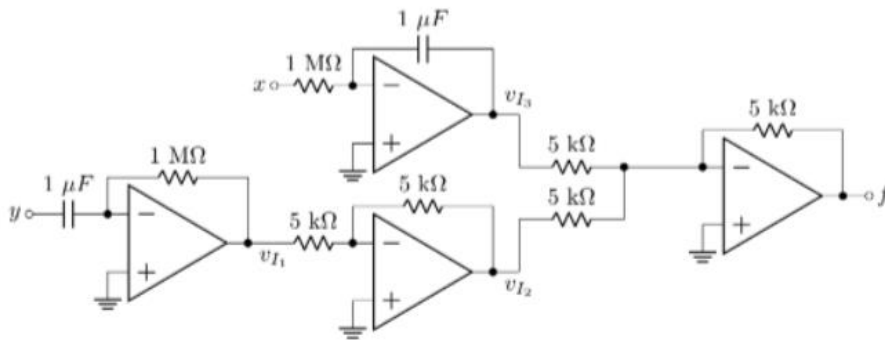


- Analyze** the circuit above to find an expression of f in terms of inputs x and y . Also, **determine** the intermediate outputs v_{I1} , v_{I2} , and v_{I3} as denoted in the circuit. [4]
- Draw the circuit of an inverting amplifier and **design** it in such a way that the voltage gain, $k = -4$. (i.e., find the values of R_1 and R_2). [3]
- Show** the input and output waveforms of the inverting amplifier of part (b) assuming a sinusoidal input of 0.5 V amplitude. **Calculate** the amplitude of the output. [2]
- Consider the inverting amplifier of part (b) again. Assume the input voltage can provide a maximum current of $0.5 \mu\text{A}$. **Determine** the design changes required, if any, for the circuit to work. [1]

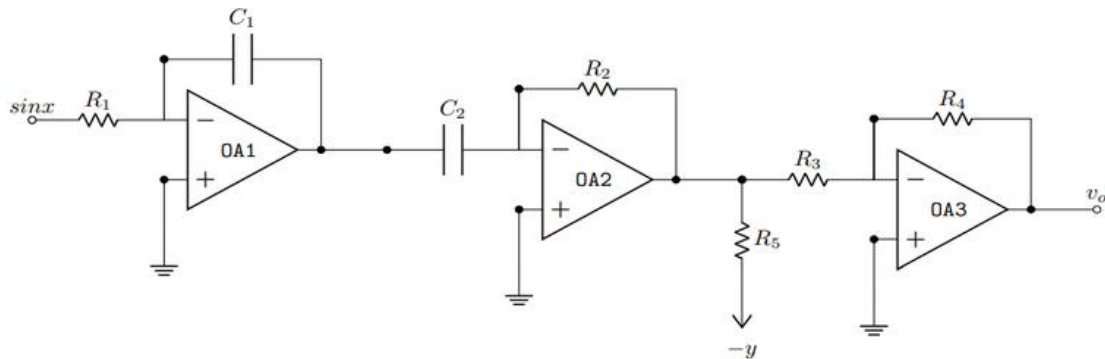Question: 05: [CO3]

(5 marks)

Deduce the output wave expression for the following circuit:



Question: 06: [CO3]

(2.5+2.5 marks)

Design a circuit using op-amps to implement $y=7x$ by an

- Inverting amplifier
- Non-inverting amplifier

Question: 07: [CO3]

(10 marks)

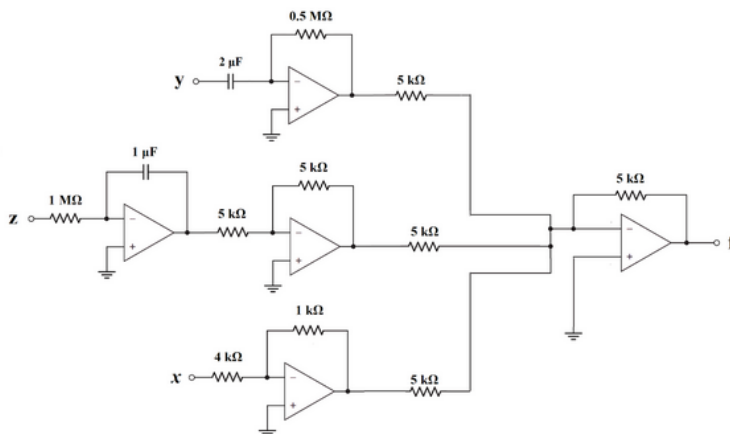


Figure 3(a)

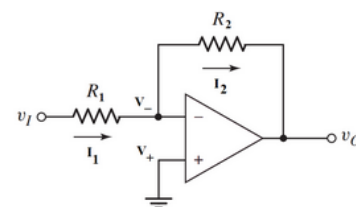
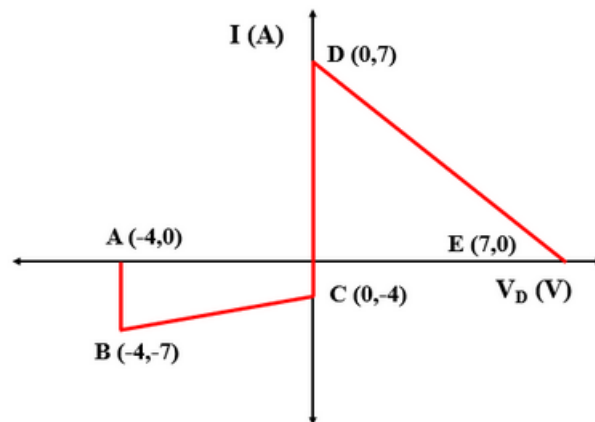


Figure 3(b)

- Analyze the circuit in Fig 3(a) to find an expression of f in terms of x , y , and z . [4]
- Design an inverting amplifier (i.e., find the values of R_1 and R_2 of the circuit shown in Fig. 3(b)) in such a way that the voltage gain is -4 . [3]
- Draw the input and output waveforms of the circuit you designed in (b). [2]
- Consider the circuit in Figure 3(b) again. Assume the input $v_i = 0.1 \sin \omega t$ (V) has a maximum current rating of $4 \mu\text{A}$. What design changes, if any, is required for this input, if the voltage gain remains the same?


Question: 08: [CO2]**(5 marks)**

Find out the slope of the following curves


**Question: 09: [CO3]****(5 marks)**

An automatic AC switching system using an Op-Amp comparator that will turn on automatically whenever the temperature is higher than 20° Celsius. The output waveform of an Op-Amp comparator should be between the voltage range of $[-4V\ 5V]$. The temperature sensor used with the circuit produces a voltage signal of $1.5V$ for a temperature value of 20° Celsius.

- Design and draw the comparator circuit with the required inputs. [3]
- Draw the VTC curve for your designed comparator. [2]

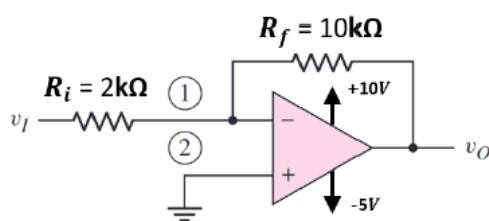Question: 10: [Part 01] [CO3]**(5 marks)**

(i)

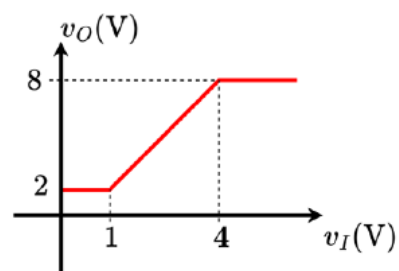

(ii)

- Draw the VTC curve for the circuit in Fig. (i). [3]
- Assume that the input signal for the circuit of Fig. (i) is $v_I = 0.1 \sin(\omega t)$ (V). Find out the output. [2]

[Part 02] [CO3]**(5 marks)**

- (a) Draw an Op-Amp circuit having the VTC shown in Fig. (ii). [2]
- (b) Deduce the close loop gain for that Op-Amp circuit. [1]
- (c) Determine the modification of this Op-Amp circuit which is required to implement a voltage-follower circuit and also draw the circuit. [2]

Question: 11: [CO3]**(5 marks)**

A Voltage Source, $V_o = 10\text{ V}$ in series with a resistor of $R = 3\text{ k}\Omega$.

- i. Write down the equation representing this curve
- ii. Determine the unknown parameters
- iii. Label the I-V curve


Question: 12: [CO3]**(5 marks)**

A Current Source, $I_o = 5\text{ mA}$ in parallel with a resistor of $R = 5\text{ k}\Omega$.


- i. Write down the equation representing this curve
- ii. Determine the unknown parameters
- iii. Label the I-V curve

Question: 13: [CO3]**(5 marks)**

Find out the output waveform of this differentiator circuit:

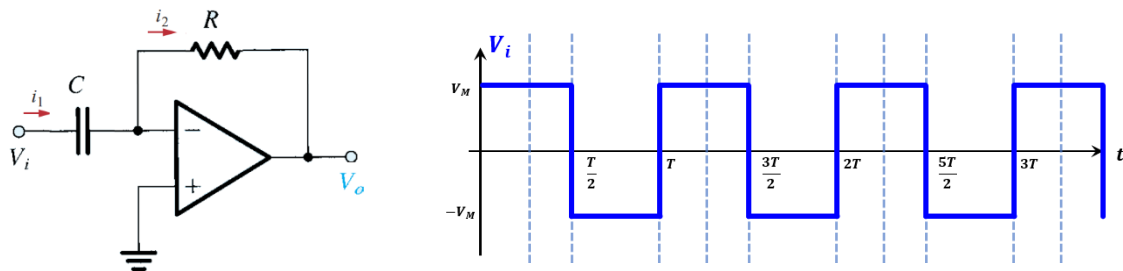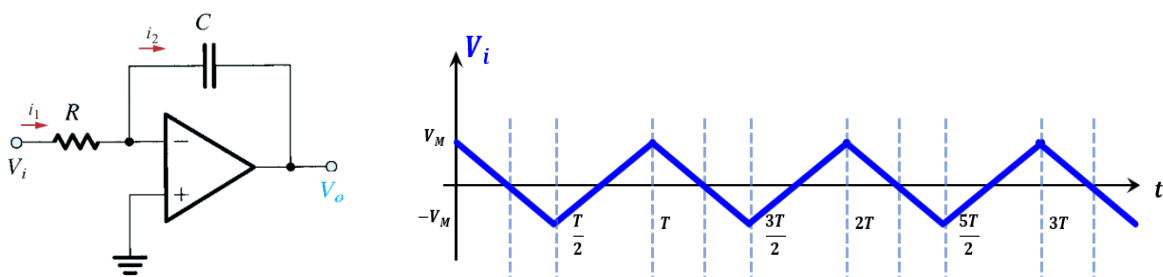**Question: 14: [CO3]****(5 marks)**

Find the output waveform of the following Op-Amp circuit:



Question: 15: [CO3]

(5 marks)

Design an Op-Amp circuit with inputs V_1 , V_2 , and V_3 to implement the following operational function: $V_o = 6V_1 - 10V_2 + 4V_3$