

CSE 251: Electronic Devices & Circuits

Lecture 2:



KCL, KVL, Nodal Analysis & Line diagram


Alternative Circuit Representation: Line diagrams


Goal: representing circuits using Short hand notations

Steps

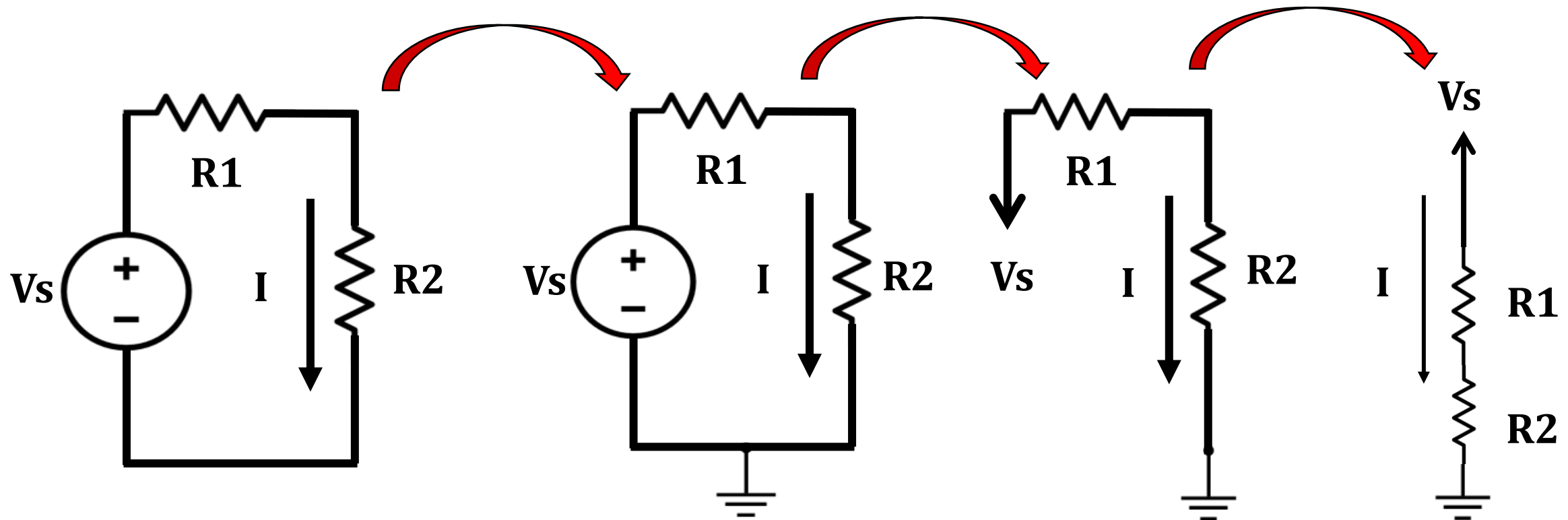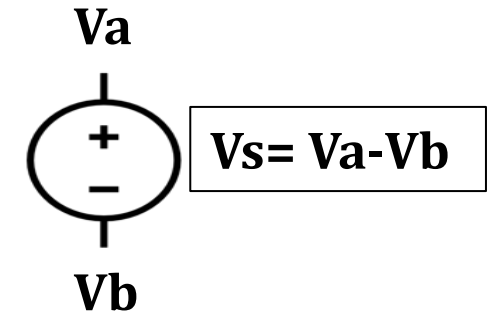
- Identify the 'Nodes'
- Select one node as 'Ground'
- Replace the other known voltage nodes with an arrow



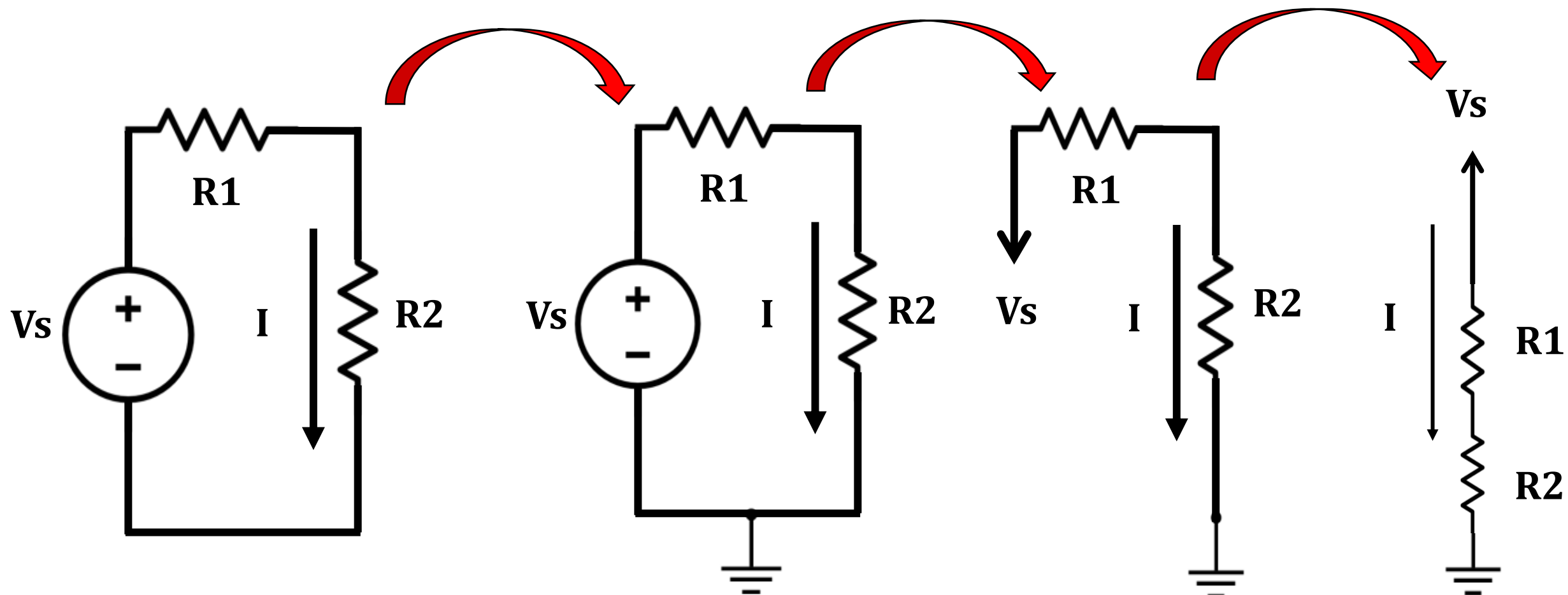

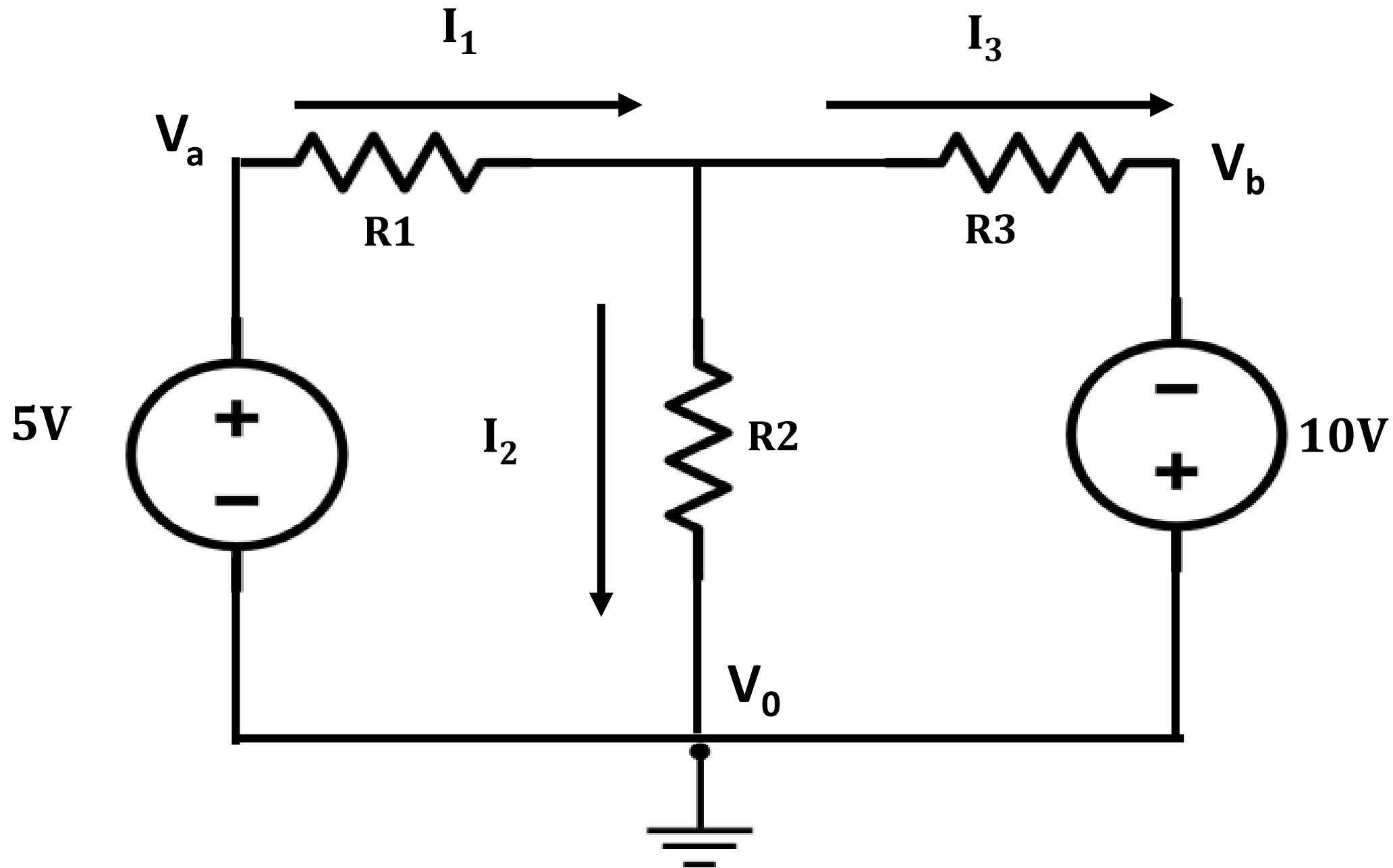

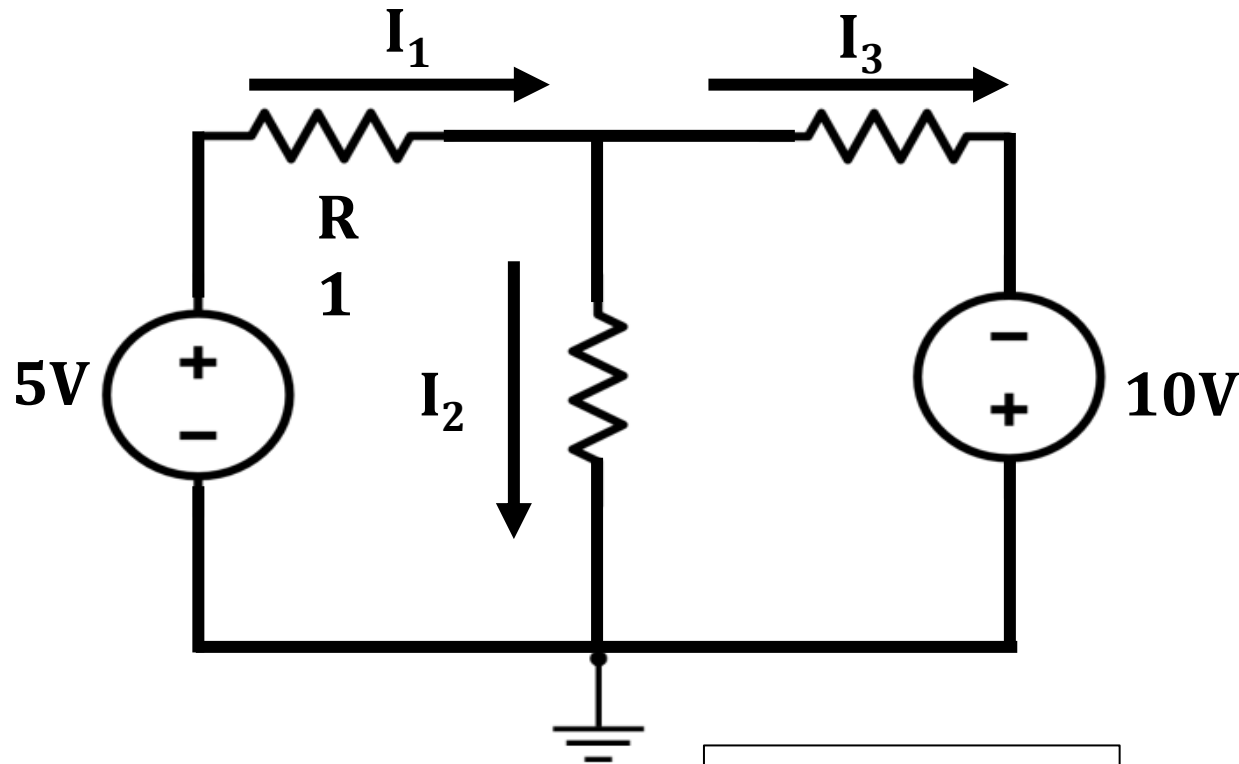- Circuits with voltage sources of opposite polarities



$V_o = 0V$ [Ground]

For 5V :



$V_a - V_o = (5 - 0) V$

$\Rightarrow V_a = 5V$


For 10V :

$V_o - V_b = (0 - 10) V$

$\Rightarrow V_b = -10V$

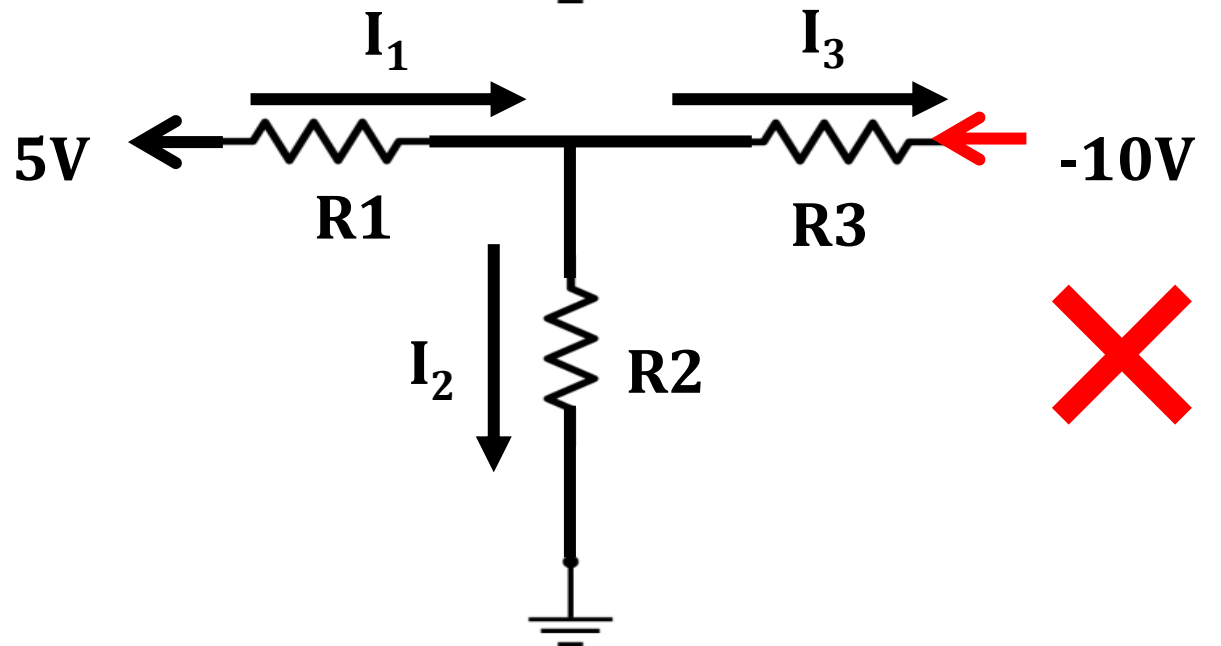
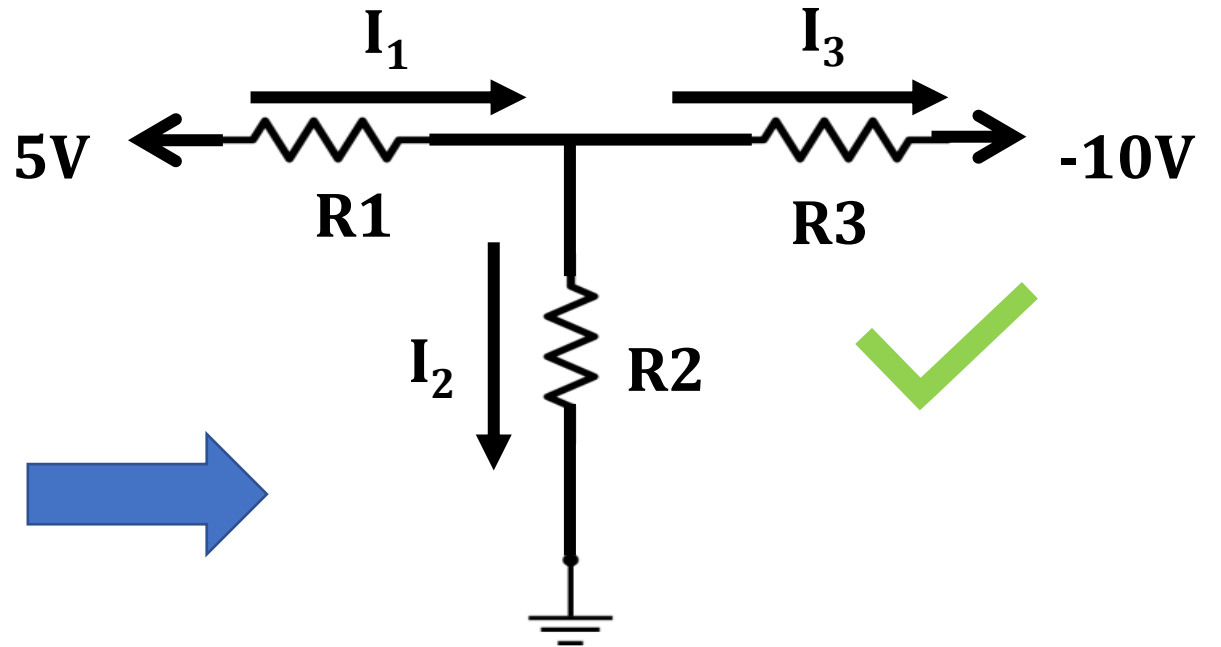


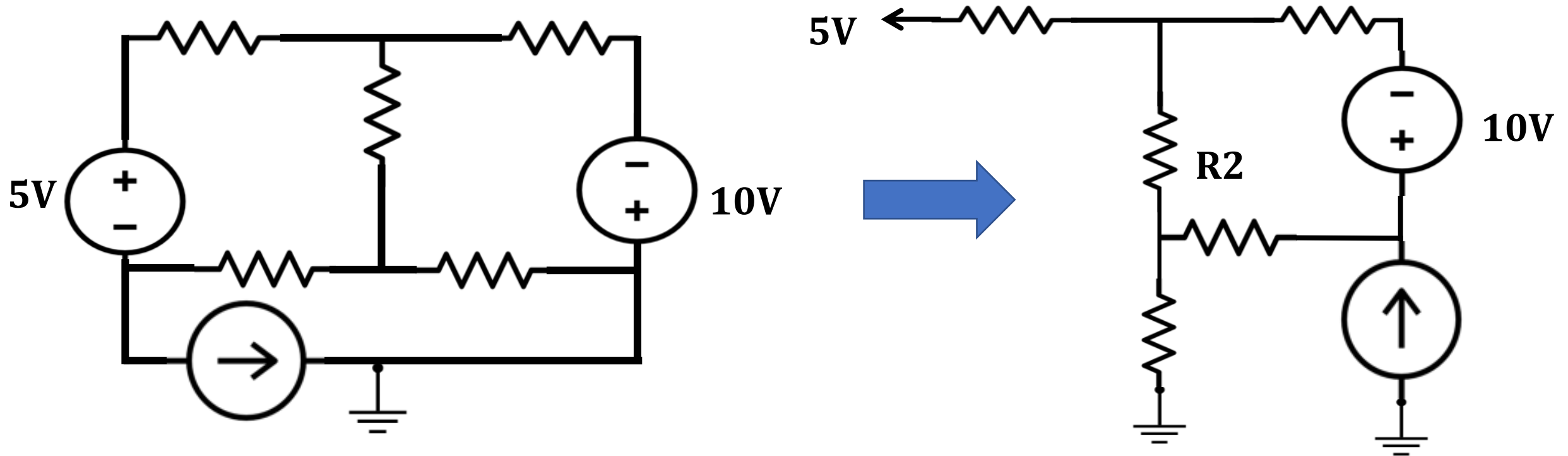- Circuit with a current source/ floating voltage source: Keep them as they are!



- **Floating voltage sources:** None of the terminals of the voltage source is connected to the reference i.e. ground node

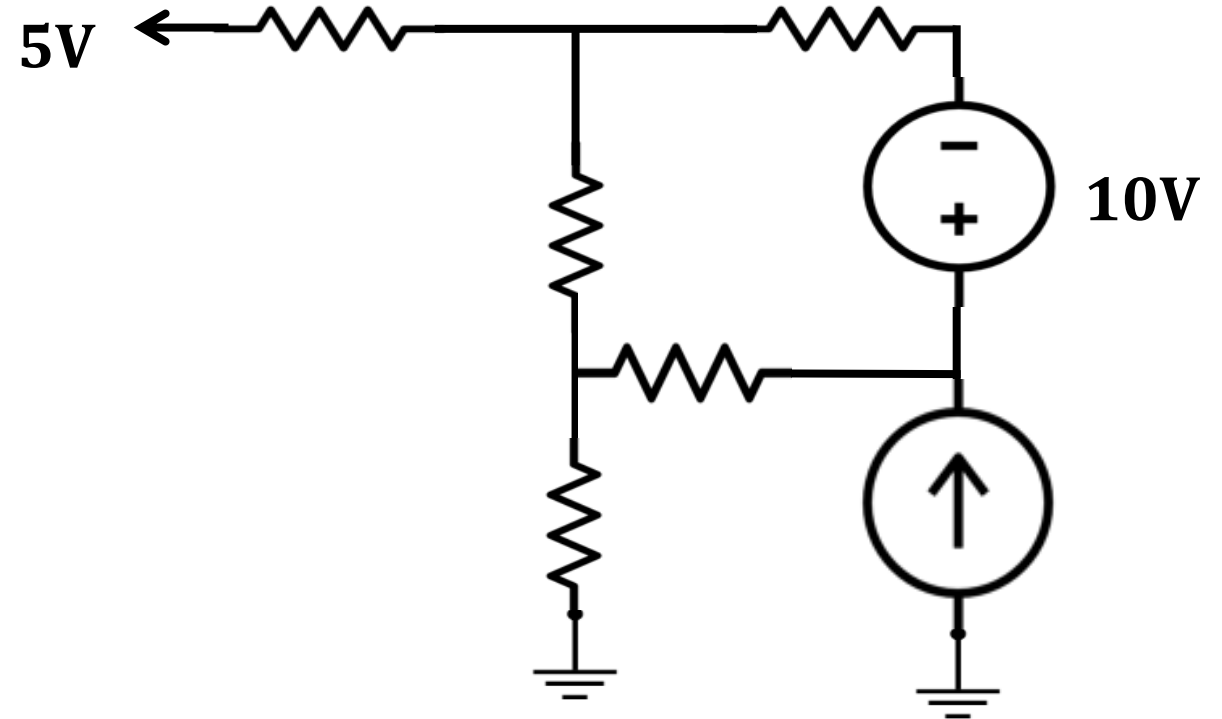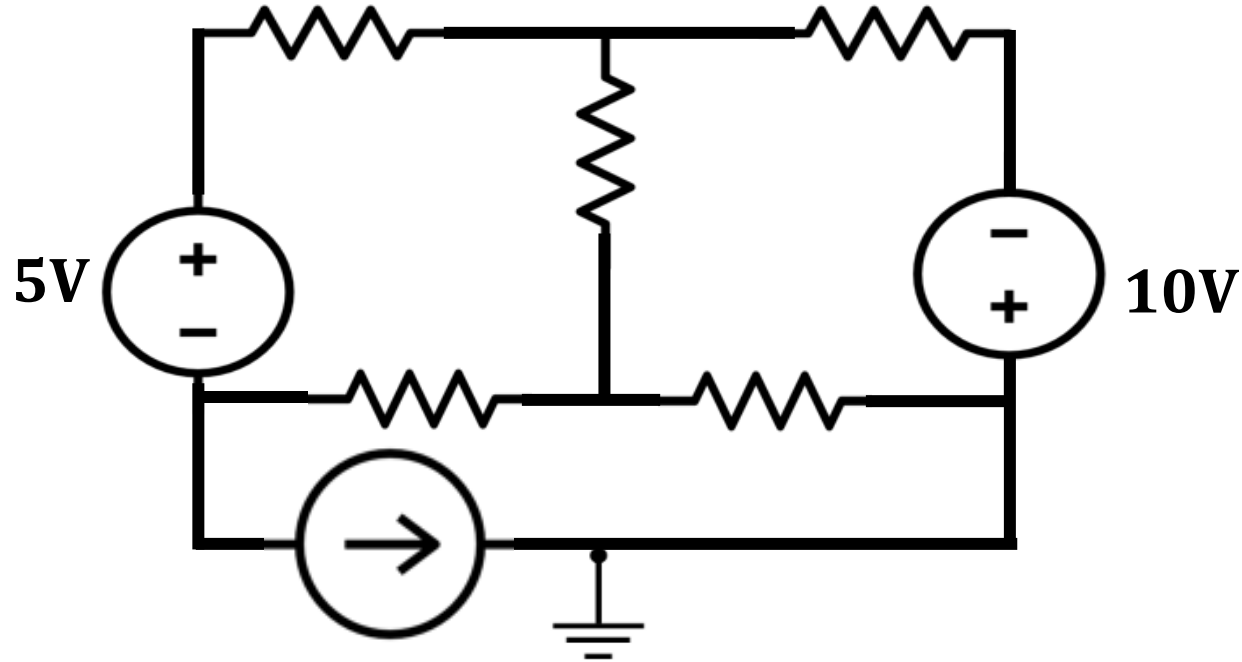
- Circuit with a current source/ floating voltage source: Keep them as they are!



- **Floating voltage sources:** None of the terminals of the voltage source is connected to the reference i.e. ground node

Kirchhoff's Current Law (KCL):

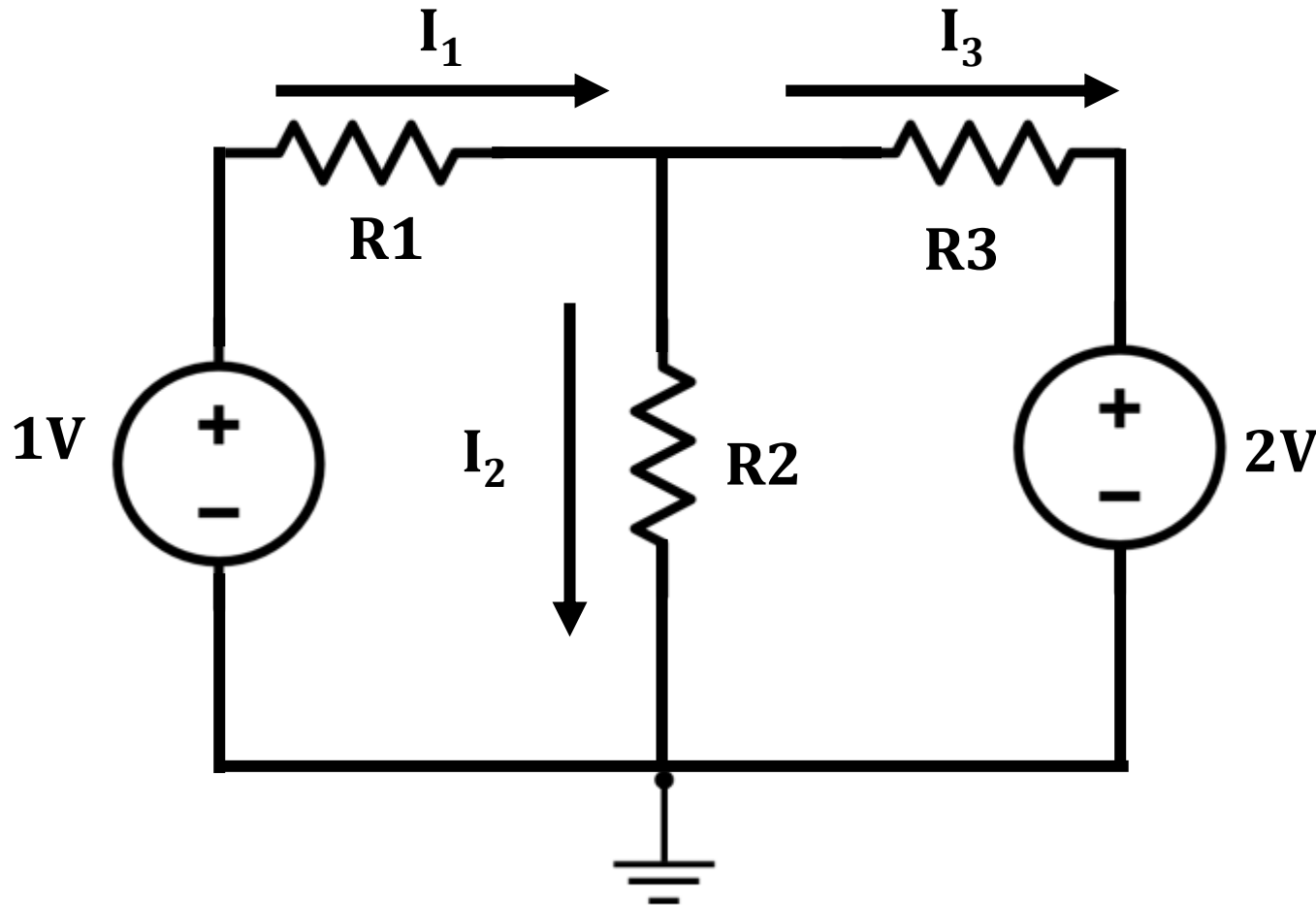
- “The algebraic sum of all currents entering and exiting a node must equal zero.”
- “Currents flowing into a node (or a junction) must be equal to the currents flowing out of it.”



$$I_1 = I_2 + I_3$$

Kirchhoff's Current Law (KCL):

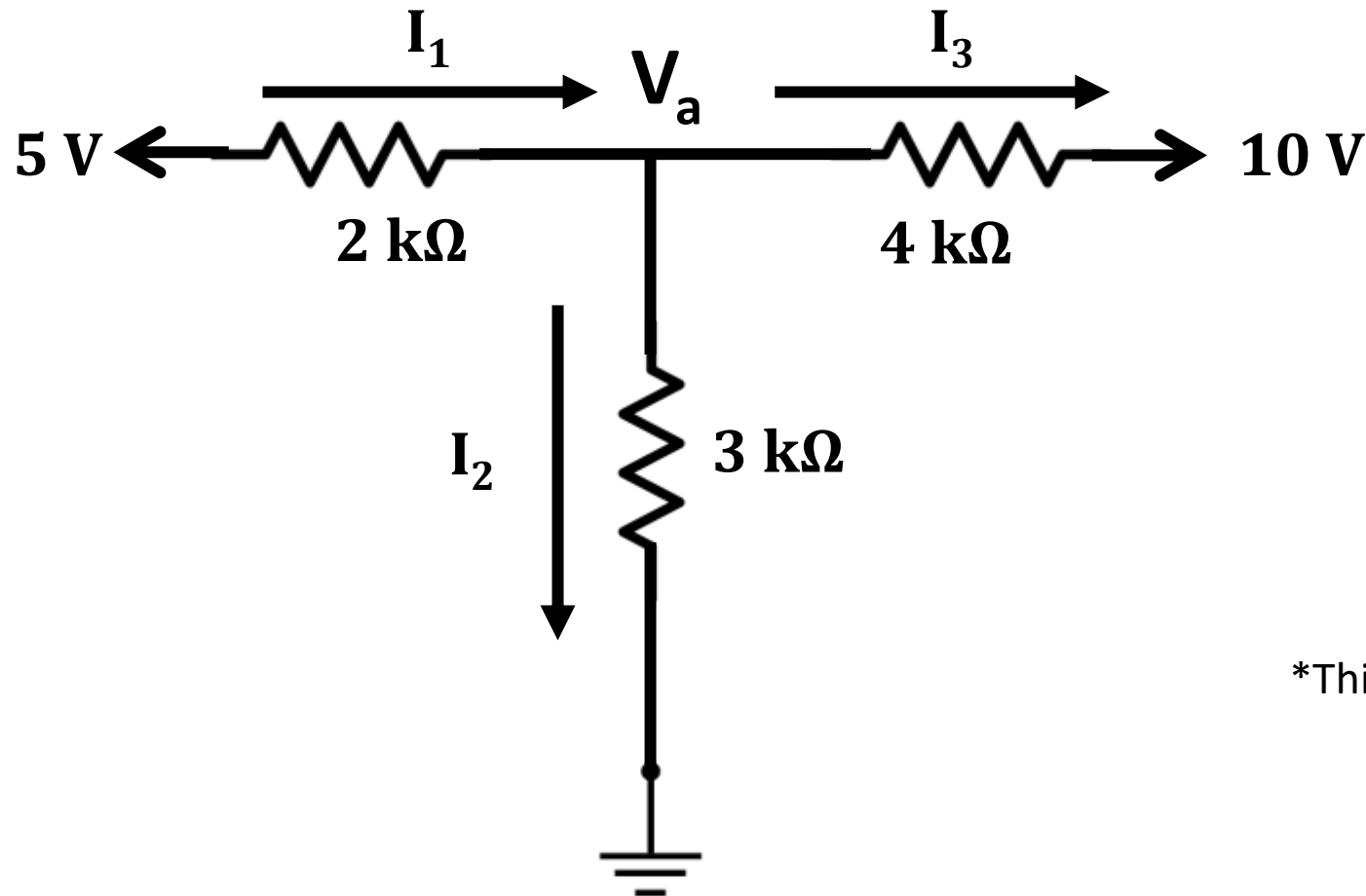- “The algebraic sum of all currents entering and exiting a node must equal zero.”
- “Currents flowing into a node (or a junction) must be equal to the currents flowing out of it.”




$$I_1 = I_2 + I_3$$


*This is also applicable for supernodes!


Kirchhoff's Voltage Law (KVL): The algebraic sum of all voltages in a loop must equal zero

Loop 1: $5 - I_1 R_1 - I_2 R_2 = 0$
Loop 2: $10 + I_2 R_2 - I_3 R_3 = 0$


$$\sum V = 0$$

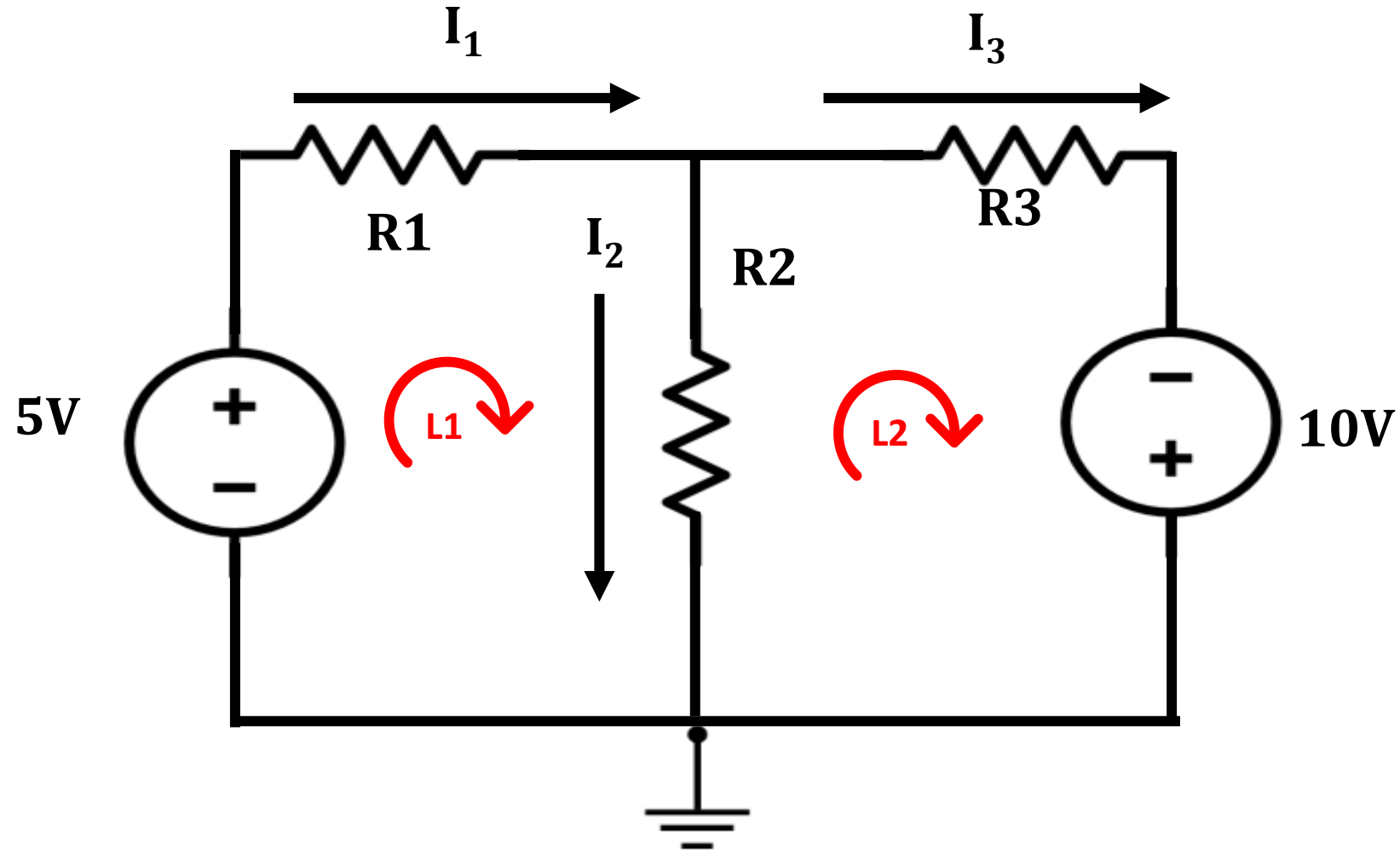

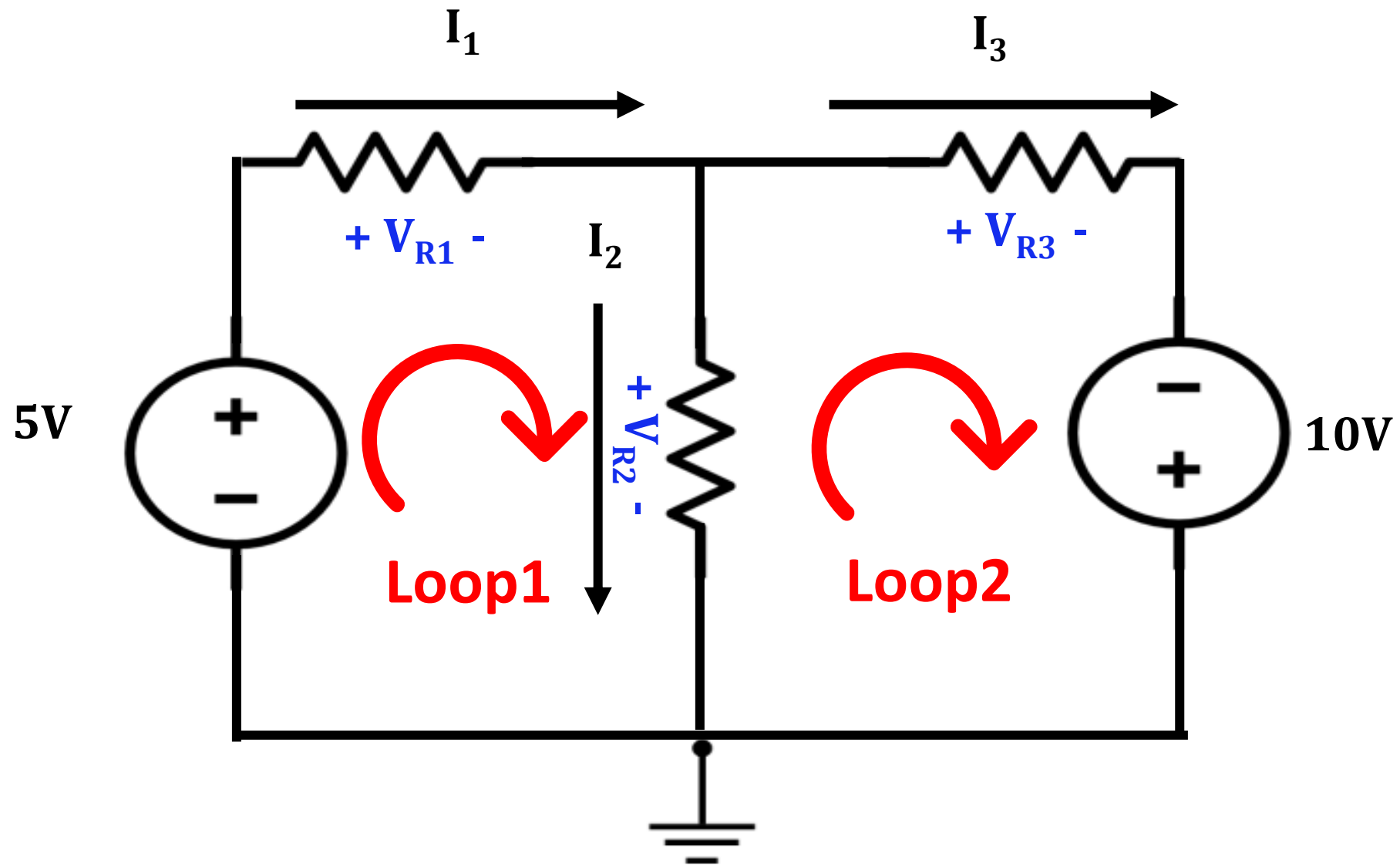

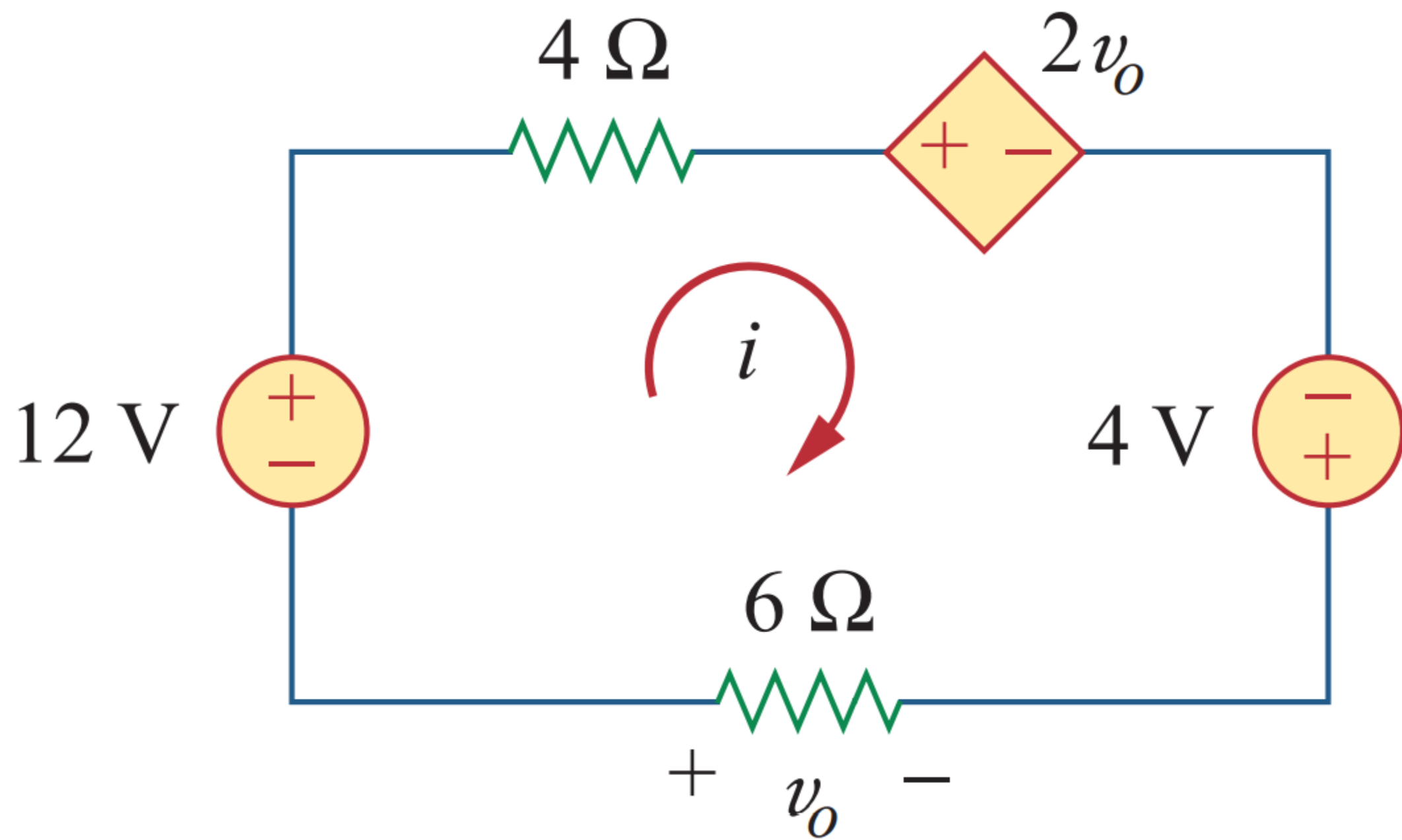


$$\sum V [\text{along line}] = \text{Voltage at the starting of the node} - \text{Voltage at the ending of the node}$$

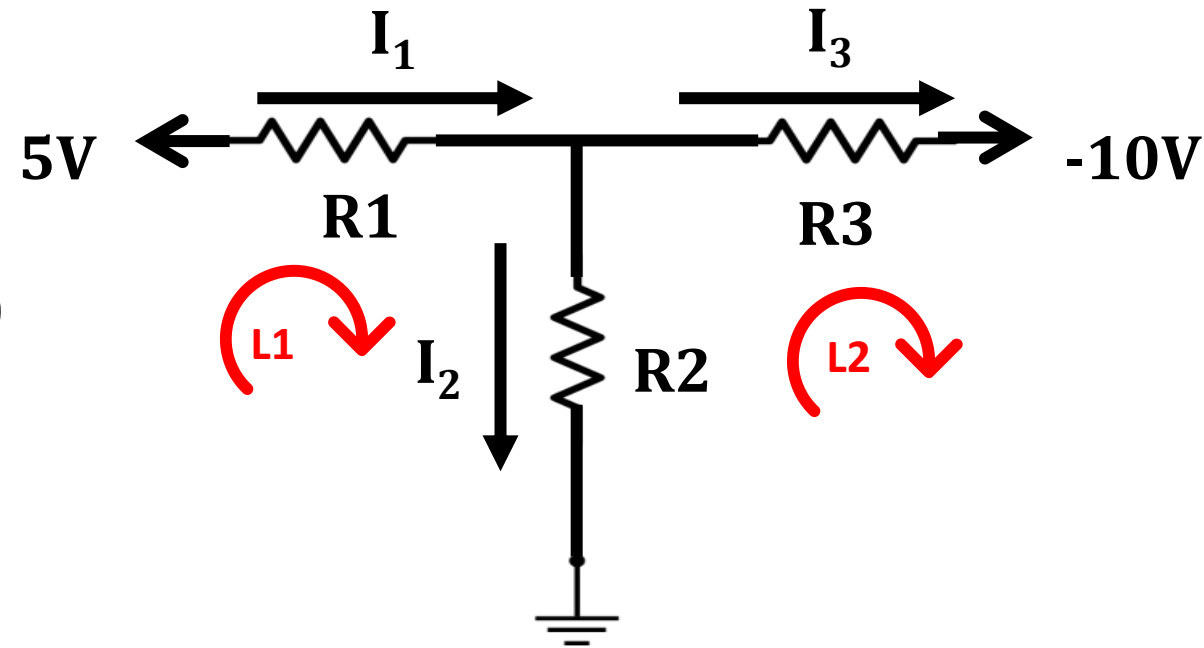


Line 1: $5 - 0 = I_1 R_1 + I_2 R_2 = 0$

Line 2: $0 - 10 = -I_2 R_2 + I_3 R_3$

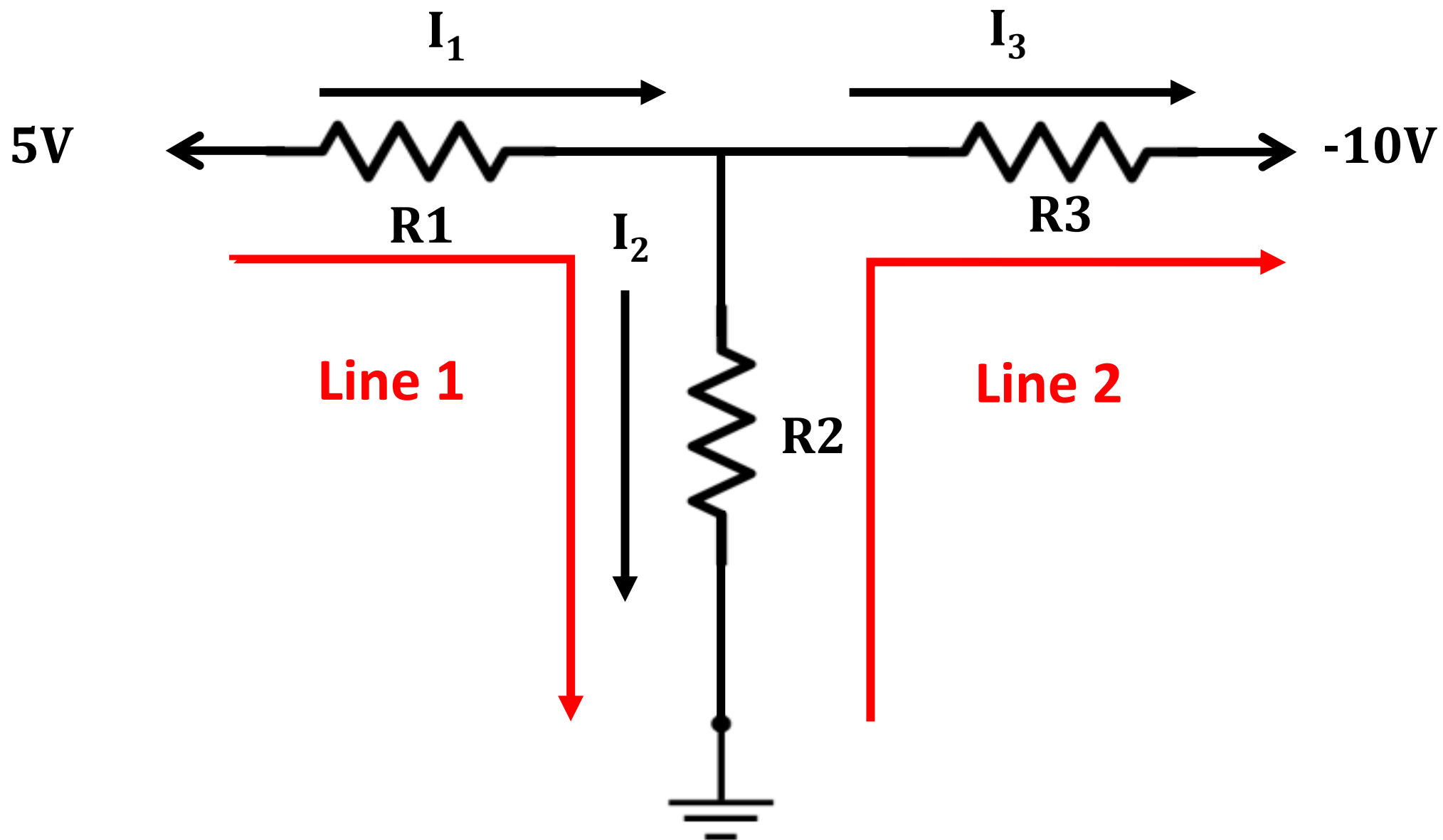


$$\sum V [\text{along line}] = \text{Voltage at the starting of the node} - \text{Voltage at the ending of the node}$$

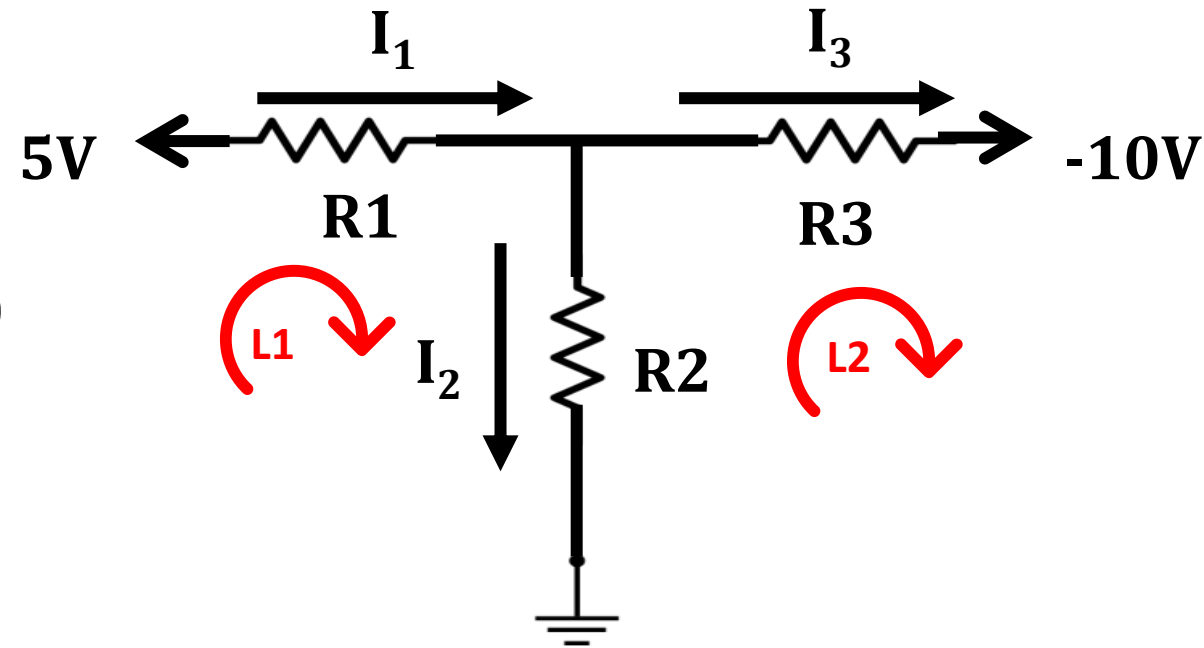

Line 1: $5 - 0 = I_1 R_1 + I_2 R_2 = 0$


Line 2: $0 + 10 = -I_2 R_2 + I_3 R_3$

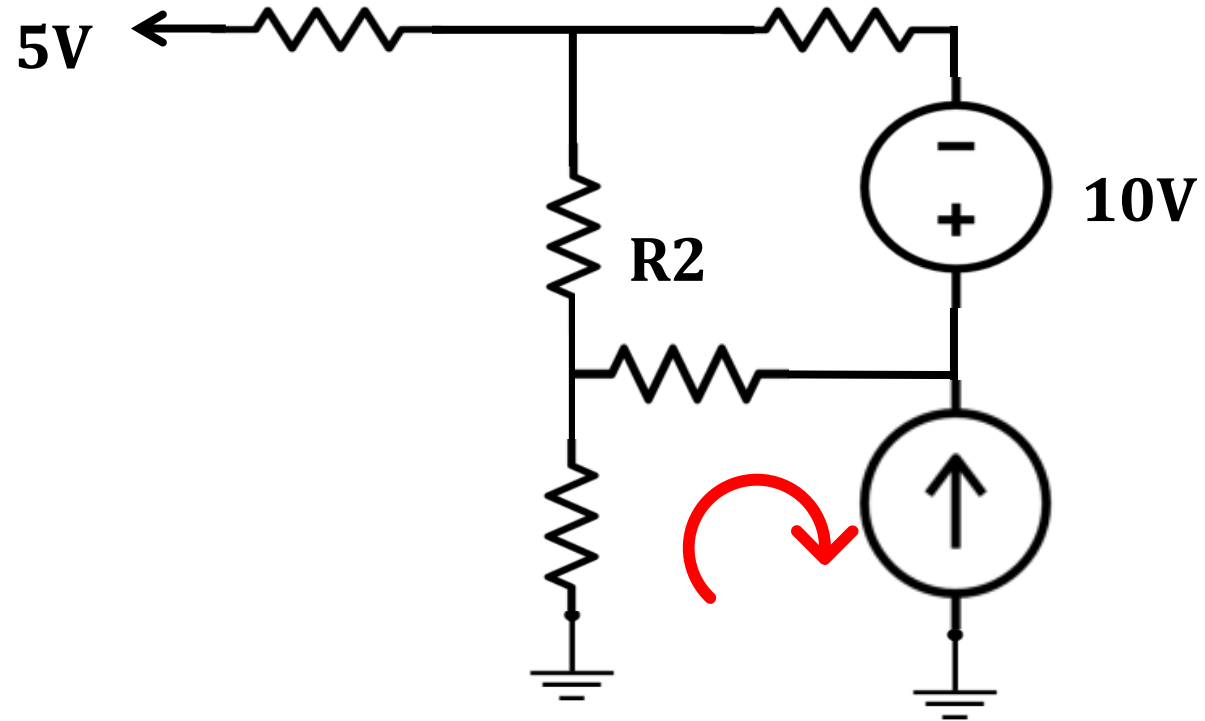


Can you write a KVL equation along this line?

Nodal analysis:

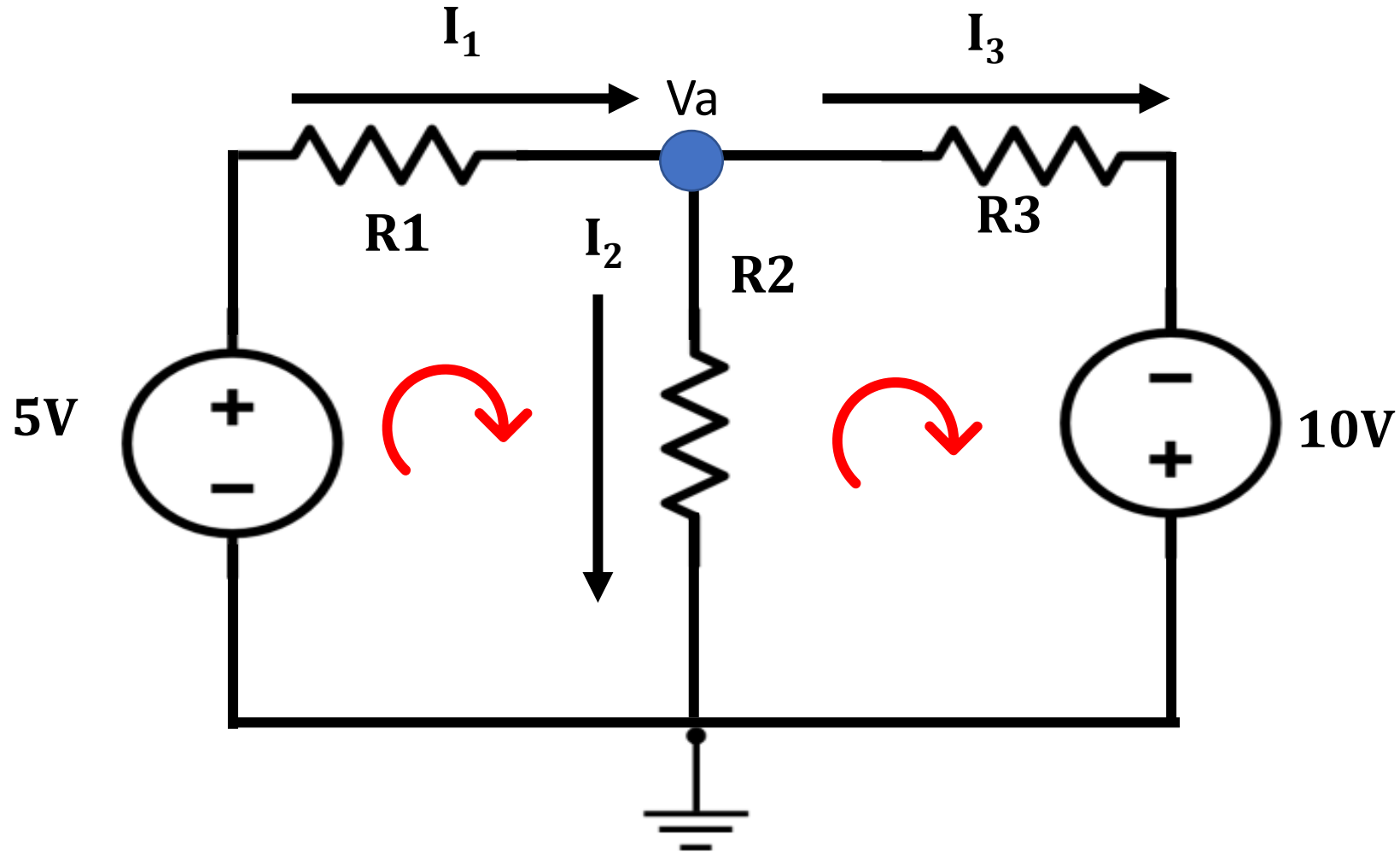
$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{5}{R_1} - \frac{0}{R_2} - \frac{-10}{R_3} = 0 ; \text{Derived from applying KCL at node } V_a$$



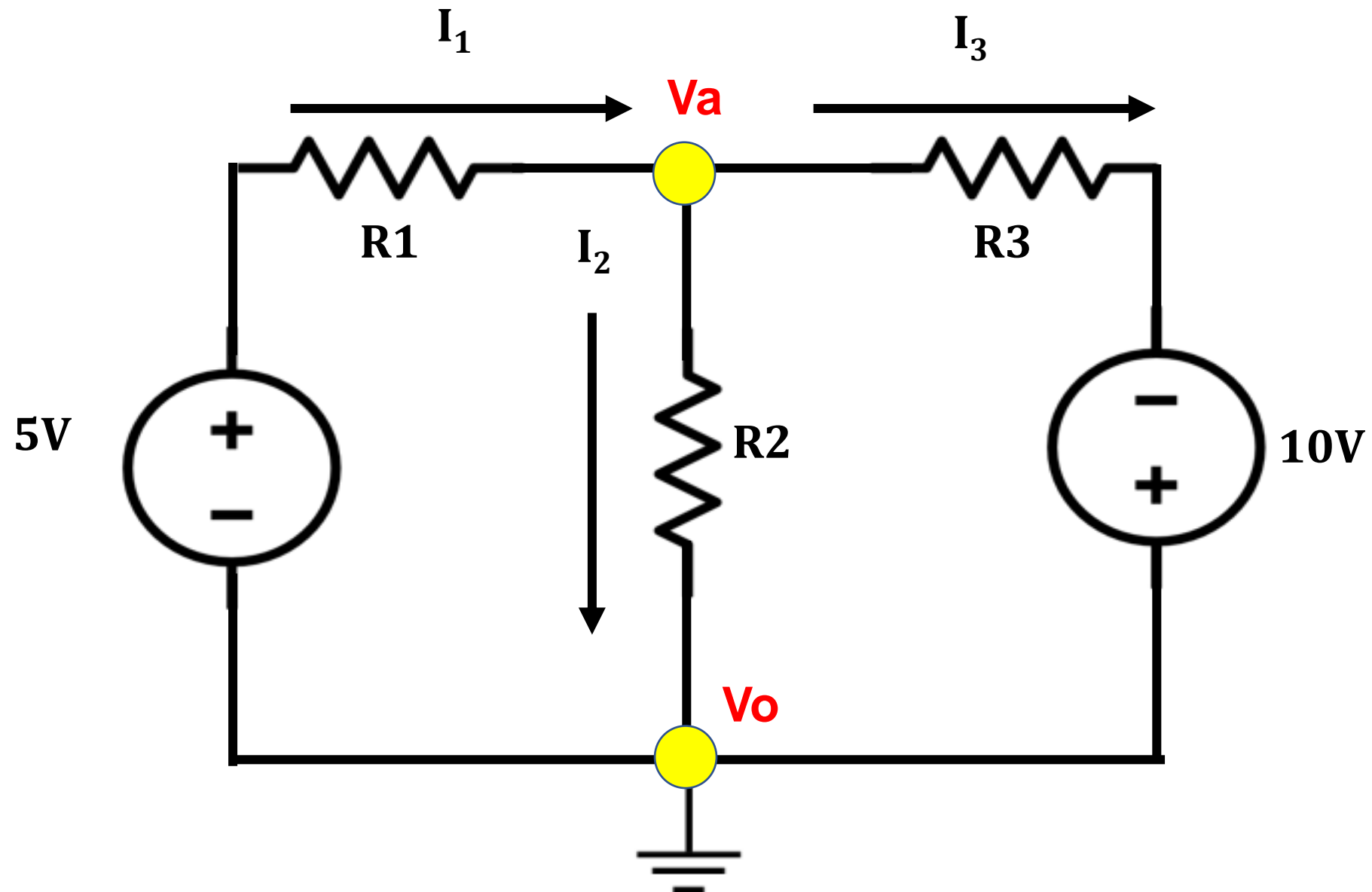

Nodal analysis:
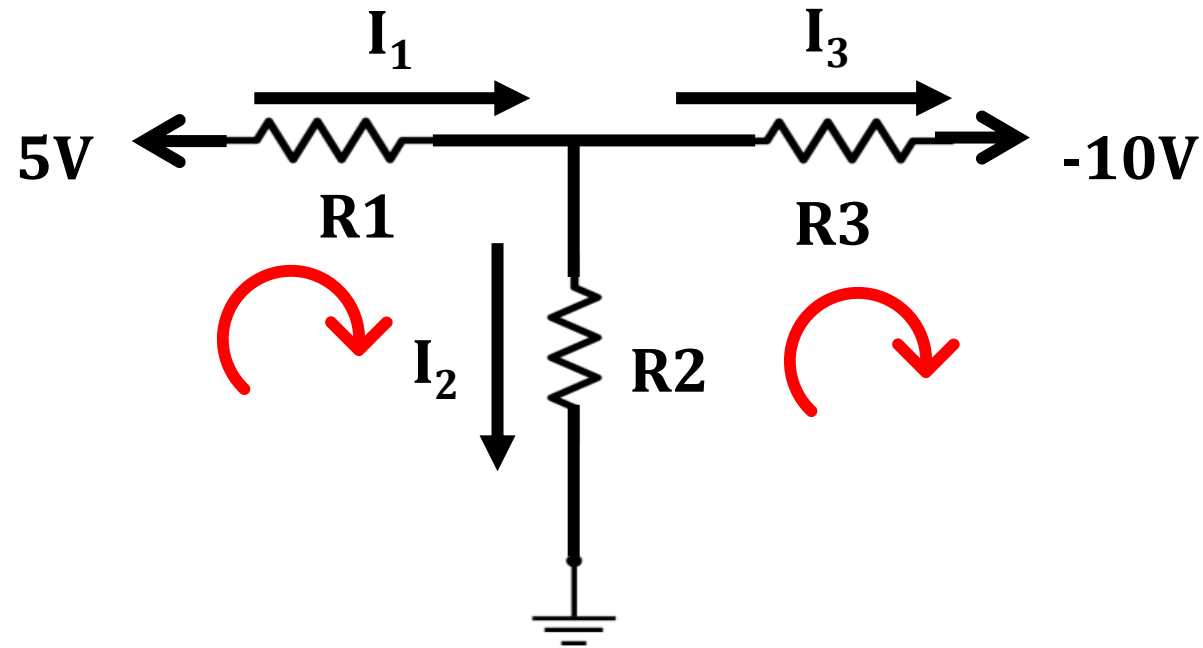
$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{5}{R_1} - \frac{0}{R_2} - \frac{-10}{R_3} = 0$$



Practice Problems: i) Draw Alternative Circuit Diagrams , ii) Write down KCL equations, iii) Write down KVL equations and iv) Nodal equation

