

Name:	ID:	Section:
-------	-----	----------


Assignment 3

BRAC Unniversity


Semester: Fall 20023

Course No.: CSE251	Marks:
Course title: Electronic Devices and Circuits	Submission Date: 24/10/2023
Faculty: TMT	

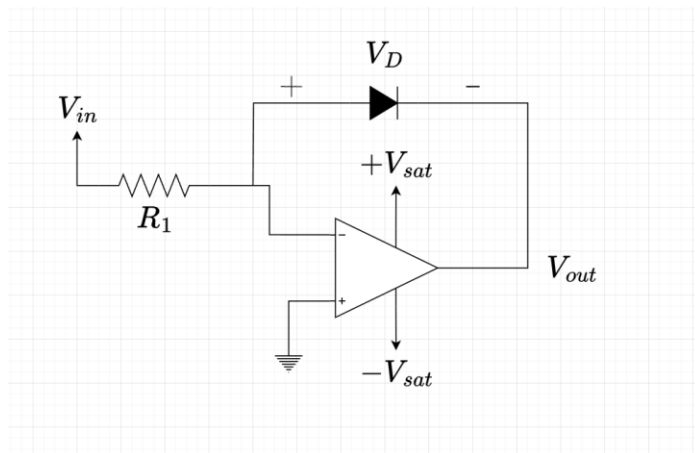1. Consider the following two circuits given below:



Circuit – 1

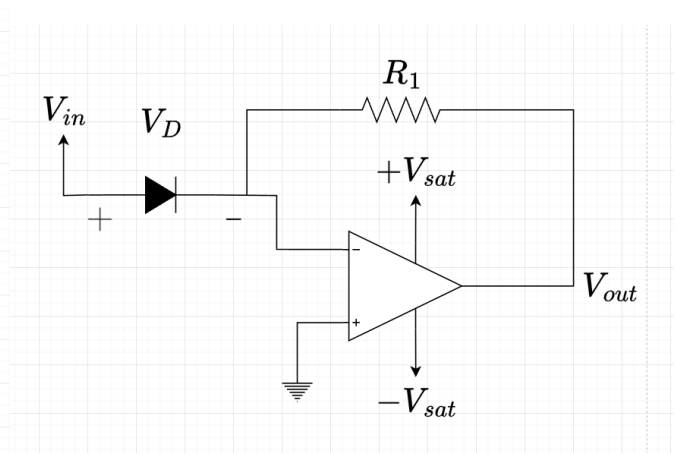

Circuit – 2

a) Solve both circuits and find their expressions of V_{out} . What mathematical operations are the two circuits performing on the input voltages? [CO1] [10]

b) Find the output values of the two circuits with $V_{in} = 0.01V, 0.02V, 0.05V$ and $0.1V$. Draw a table with two columns, one for output of Circuit-1 and one for Circuit-2, and enter 3 entries for the three input voltages above. [CO1] [4]

c) From the table obtained from (b), which of the outputs of the two circuits seem to grow faster? Explain your reasoning from the expressions obtained in (a) and tabular values from (b). [CO2] [6]

d) Now connect the output of the first circuit with the input of the second circuit. Draw the connected circuit and find the output voltage expression from an arbitrary input, V_{in} . [CO2] [10]

Given that, $I_s = 10^{-9} A$, $R_1 = 10 M\Omega$ and $V_T = 0.0259 V$. Also, the diode shockley equation that relates the current through it to the voltage across the diode is given by: $I_D = I_s \cdot \exp[(V_D/V_T)-1]$ where $\exp()$ is the exponential function.

